



TECHNICAL UNIVERISTRY OF MOMBASA

Faculty of Engineering & Technology

DEPARTMENT OF MECHANICAL & AUTOMOTIVE ENGINEERING

CERTIFICATE IN MECHANICAL ENGINEERING (Y1, S2)

EEE 1105: ELECTRICAL ENGINEERING SCIENCE II

END OF SEMESTER EXAMINATION

SERIES: DECEMBER 2014

TIME: 2 HOURS

Instructions to Candidates:

You should have the following for this examination

- *Answer Booklet*

This paper consists of **FIVE** questions. Answer any **THREE** questions

Maximum marks for each part of a question are as shown

This paper consists of **THREE** printed pages

Question One (Compulsory)

- a) What does it mean for an object to have an electric charge? Give an example of an object receiving an electric charge and describe how that charged object might behave. **(4 marks)**
- b) Given two lengths of a solid metal wire with round cross-sections which one will have the least electrical resistance; one that is small-diameter, or the one that is large-diameter? Assume all other factors are equal (same metal type, same wire length, etc) **(3 marks)**
- c) Label the direction of both electron flow and conventional flow in this simple circuit: **(3 marks)**
- Lamp

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

- d) (i) Show that for four resistors connected in series **(5 marks)**
- $$R_T = R_1 + R_2 + R_3 + R_4$$
- (ii) Show that for four resistors connected in parallel **(5 marks)**

Question Two

- a) (I) Define the following magnetic quantities:
- (i) Magnetic field
 - (ii) Magnetic flux Q
 - (iii) Magnetic flux density (B)
 - (iv) Magnetomotive force (mmf)
 - (v) Reluctance (S) **(5 marks)**
- (II) With an aid of sketches describe interaction of magnetic fields on current carrying conductors:
- (i) In the same direction
 - (ii) In opposite direction **(8 marks)**
- b) (I) A magnetic pole face has a rectangular section having dimensions 200mm by 100mm. If the total flux emerging from the pole is 150μWb, determine the flux density. **(4 marks)**
- (II) A flux of 300μ webers passing through a 150 turns coil is reversed in 40ms. Determine the average induced Emf. **(3 marks)**

Question Three

- a) Explain the meaning of a series circuit. **(2 marks)**

- b) Two resistors of values 10Ω and 20Ω are connected in parallel with one another, the combination draws a current of 10A from the supply. Calculate:
- (i) Current in each resistor
 - (ii) P.D across parallel circuit **(8 marks)**
- c) A battery of e.m.f 48V and internal resistance 3Ω is charged on a 110V d.c. supply, using the constant current method. If the cost of energy is shs 0.95 per kwh, calculate:
- (i) The series resistance required to give a current of 4A
 - (ii) The cost of charge the battery for 18 hours **(5 marks)**

Question Four

- a) (i) State THREE types of single phase motors and explain which type is best to be used in light office work **(5 marks)**
- (ii) Explain briefly why a single phase motor is not self-starting **(4 marks)**
- b) (i) State how the direction of rotation of a single phase induction motor can be changed. **(3 marks)**
- (ii) With aid of a circuit diagram, explain the principle of operation of a capacitor start single phase induction motor. **(5 marks)**
- c) Explain the term “Slip” in reference to induction motors **(3 marks)**

Question Five

- a) (i) State the losses that occur in a transformer. **(4 marks)**
- (ii) Explain using a diagram TWO methods by which transformer windings are wound around the iron core. **(8 marks)**
- b) (i) State the effect of the losses in transformer when it is on full load **(4 marks)**
- (ii) Explain briefly the principle of operation for a single phase transformer **(4 marks)**