



TECHNICAL UNIVERSITY OF MOMBASA

**Faculty of Engineering & Technology
in Conjunction with
Kenya Institute of Highways and
Building & Technology (KIHBT)**

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

HIGHER DIPLOMA IN TECHNOLOGY

EEP 3107: ELECTRICAL TECHNOLOGY I

END OF SEMESTER EXAMINATION

SERIES: MAY 2015

TIME ALLOWED: 2 HOURS

Instructions to Candidates:

You should have the following for this examination

- *Answer Booklet*

This paper consists of **FIVE** questions. Answer any **THREE** questions
This paper consists of **FOUR** printed pages

Question One

- a) Explain the main advantages of connecting the secondary windings of a three-phase distribution transformers in star **(6 marks)**
- b) A three phase system supplies a balanced load of 25KW at a p.f. of 0.8, the line voltage being 440V. Calculate:
(i) The line current
(ii) The phase current, when the load is connected either in star or in delta **(8 marks)**
- c) With the aid of a diagram, show the connection of three waltmeters for 2-phase balanced star connected load and derive the formula for total power **(6 marks)**

Question Two

- a) State:
(i) TWO causes of Harmonics
(ii) TWO methods of minimizing Harmonics **(4 marks)**
- b) A complex voltage wave form is made of two sinusoidal wave forms as follows:
- A fundamental wave of peak value 10V and frequency 50Hz
 - A second harmonic wave of peak value A volts and frequency 100Hz all waves starting at the same time as the fundamental wave
- (i) Draw a scale on the same axis the two waves with only one cycle of the fundamental **(10 marks)**
- (ii) Derive the complex waveform form the two waves **(4 marks)**
- (iii) State the maximum or peak value of the complex wave **(2 marks)**

Question Three

- a) (i) Give the expression for the R.M.S value of a complex wave with the fundamental and 2nd, 3rd and 5th harmonics **(5 marks)**
(ii) Also show graphically how the R.M.S value of the complex wave in a(i) above with 50% 2nd and 3rd Harmonics and 25% 5th harmonic **(7 marks)**
- b) A coil has a reactance of 15Ω and a resistance of 10Ω when connected across a 200V, 50Hz a.c. supply. Calculate:
(i) The current
(ii) The average power consumed
(iii) The phase angle between the voltage and the current
(iv) Draw both the circuit and the phasor diagram for this connection **(8 marks)**

Question Four

- a) State:

- (i) Norton's theorem
- (ii) Thevenin's theorem

Find the current flowing in the 5Ω resistor of the network shown in figure 4(a) above **(8 marks)**

Using THEVENIN theorem, calculate the current and power (W) across the $1K\Omega$ load resistor RL in figure 4(b)

Question Five

- a) A capacitor of $100\mu\text{F}$ is connected in series with a pure resistor of 50Ω across a 15V, 50Hz supply:
- (i) Capacitive reactance
 - (ii) Total impedance of the circuit
 - (iii) The current in the circuit
 - (iv) The phase angle
 - (v) The voltage across the capacitor
 - (vi) The KVA power in the circuit **(10 marks)**
- b) If a resistance of 100Ω an inductance of 0.2H and a capacitor of $20\mu\text{F}$ are connected in parallel across a 240V supply, calculate:
- (i) The current through each component

- (ii) Total circuit current
- (iii) Power factor of circuit, state whether leading or lagging
- (iv) The power absorbed by the circuit

(10 marks)