



TECHNICAL UNIVERSITY OF MOMBASA

**Faculty of Engineering &
Technology in Conjunction with
Kenya Institute of Highways and
Building Technology (KIHBT)**

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

HIGHER DIPLOMA IN ELECTRICAL & ELECTRONIC ENGINEERING

EEA 3163: ELECTRICAL TECHNOLOGY II

SPECIAL/SUPPLEMENTARY EXAMINATION

SERIES: AUGUST 2014

TIME: 2 HOURS

Instructions to Candidates:

You should have the following for this examination

- *Answer Booklet*
- *A non-programmable Scientific Calculator*

This paper consists of **FIVE** questions. Answer any **THREE** questions

All questions carry equal marks

Maximum marks for each part of a question are as shown
 This paper consists of **FOUR** printed pages

Question One

- a) With regard to mutually coupled coils, explain:
 (i) The maximum possible coefficient coupling
 (ii) How can such coupling be obtained
 (iii) Typical value of this coefficient between two air cored RF coils. **(6 marks)**
- b) Derive the necessary expression for calculating the inductance of a coil. **(6 marks)**
- c) (I) A ring of stalloy stampings having a mean circumference of 400mm and a cross-sectional area 500mm² has 200turns. Determine the inductance of coil corresponding to the reversal of current of:
 (i) 1A
 (ii) 5A
- (II) If the core is non-magnetic determine inductance of coil tube the following B-H curve:

B	1.2	1.3	1.4	1.5	1.55	1.6
H	400	500	650	900	1300	2500

(8 marks)

Question Two

- a) (i) State the maximum power transfer theorem.
 (ii) Derive the condition for maximum power transfer in a.c. circuits. **(6 marks)**
- b) A circuit has a resistance of 6Ω and a capacitance reactance of 8Ω in series. A voltage $V = 141 \sin 314t$ is applied. Determine:
 (i) Value of complex impedance
 (ii) Expression for current
 (iii) Power factor
 (iv) r.m.s values of voltage and current
 (v) Real power
 (vi) Reactive power draw the phasor diagram. **(7 marks)**
- c) A voltage 10V(rms) at a frequency of $10^6 \pi$ Hz is applied to points AB of the circuit shown in figure 1. Determine current I_1 in steady state conditions. $L_1 = 5mH$. $L_2 = 1mH$, $M_{12} = 2mH$, $R_1 = 10K$, $R_2 = 5K$ **(7 marks)**

R_1

Question Three

- a) Define the term “bandwidth” (2 marks)
- b) Derive the expressions for resonance frequency. (4 marks)
- c) A constant voltage at a frequency of 1MHz is applied to a choke coil in series with a variable capacitor. When the capacitor is set at 500pF, the current in the circuit is maximum. When the capacitance is 600pF, the current is half the maximum value. Determine:
- (i) Resistance
 - (ii) Inductance
 - (iii) Factor of the choke coil (7 marks)

- d) A voltage $V = 10 \sin \omega t$ is applied to a series RLC circuit. At resonance the voltage across capacitor is 500V. The band width is 400rad/s and impedance at resonance is 100Ω . Determine:
- (i) ω_r , lower and upper half power frequencies.
 - (ii) L and C (7 marks)

Question Four

- a) For the network of figure 2, determine:
- (i) I^1 , I^2 and I_3 with switch S at A
 - (ii) I_1 , I_2 and I_3 with switch S at B
- Using the principle of super position. (7 marks)

- b) In the circuit of figure 3 the resistance have the following values in ohms $R_a = 20 \Omega$, $R_b = 30 \Omega$, $R_c = 50 \Omega$, $R_d = 24 \Omega$, $R_e = 5 \Omega$. Determine the current supplied by the battery. **(6 marks)**
- c) Determine the currents through the different branches of the network shown in figure 4. **(7 marks)**

Question Five

- a) Derive the necessary equation for:
- Rise of current in an inductance circuit when it is connected to a dc source.
 - Decay of current in an inductance circuit when it is disconnected from the source.
- (8 marks)**
- b) In the circuit of figure 5, the switch is put on position 'a':
- Find expression for charging current.
 - After a long time the switch is put on position 'b'. Determine expression for current through $0.1m \Omega$ resistor.
 - Determine time constant of current in part (ii)
- (12 marks)**

