



# TECHNICAL UNIVERSITY OF MOMBASA

## Faculty of Applied & Health Sciences

DEPARTMENT OF MATHEMATICS & PHYSICS

UNIVERSITY EXAMINATION FOR:

**BACHELOR OF SCIENCE IN MATHEMATICS & COMPUTER SCIENCE**

APS 4112: ELECTRONICS

**END OF SEMESTER EXAMINATION**

SERIES: APRIL 2014

**TIME ALLOWED: 2 HOURS**

**Instructions to Candidates:**

You should have the following for this examination

- *Mathematical tables*
- *Scientific Calculator*

This paper consist of **FIVE** questions

Answer question **ONE (COMPULSORY)** and any other **TWO** questions

Maximum marks for each part of a question are as shown

This paper consists of **FOUR** printed pages

---

**Question One (Compulsory)**

a) Define the following terms:

- |                                       |           |
|---------------------------------------|-----------|
| (i) Doping                            | (1 mark)  |
| (ii) A hole                           | (1 mark)  |
| (iii) n-type and p-type semiconductor | (2 marks) |
| (iv) Intrinsic semi-conductor         | (1marks)  |

b) Explain why the conductivity of a metallic conductor decreases with increasing temperature while that of a semiconductor increases with increasing temperature. (3 marks)

- c) A crystal diode having internal resistance of  $= 30 \Omega$  is used for half wave rectification. If the applied voltage is 54V and load resistance  $R_L = 770 \Omega$ , find:
- (i)  $I_m$  (2 marks)
  - (ii)  $I_{dc}$  (2 marks)
  - (iii)  $I_{r.m.s}$  (2 marks)
  - (iv) ac power input and dc power output (4 marks)
  - (v) d.c. output voltage (2 marks)
  - (vi) efficiency of the rectification (2 marks)
- d) Explain briefly SIX types of diodes. (6 marks)
- e) In a common base connection current amplification factor is 0.9. If the emitter current is 1mA, determine the base current. (2 marks)

### Question Two

- a) Explain what happens to the depletion layer when a diode is.
- (i) Forward biased (2 marks)
  - (ii) Reverse biased (2 marks)
- b) State THREE ways in which a transistor can be connected in a circuit. (3 marks)
- c) The collector leakage current in a transistor is  $400 \mu A$  in common emitter arrangement. If the transistor is now connected in CB arrangement, what will be leakage current? Given that  $\beta = 100$  (4 marks)
- d) For a certain transistor,  $I_B = 30 \mu A$ ,  $I_C = 3mA$  and  $\beta = 60$ . Calculate  $I_{CBO}$  (4 marks)
- e) Name the current carriers in a:
- (i) pnp transistor (1 mark)
  - (ii) npn transistor (1 mark)
- f) (i) What is transistor biasing (2 marks)
- (ii) What is the importance of biasing (1 mark)

### Question Three

- a) State THREE methods of transistor biasing. (3 marks)
- b) For the circuit shown below, find the operating point given that  $\beta = 80$ . Neglect  $V_{BE}$ . (7 marks)

- c) Find the operating point in the circuit shown in the circuit below. Assume  $\beta = 80$  and  $V_{BE} = 0.7V$   
**(6 marks)**

d) What will result if biasing is not done in an amplifier circuit? **(2 marks)**

e) What biasing method provides the best stabilization of operating point? Explain? **(2 marks)**

#### Question Four

a) Draw a well labeled circuit of a transistor amplifier **(5 marks)**

b) In the transistor amplifier circuit shown below if  $R_C = 20K\Omega$ ,  $R_L = 20K\Omega$ ,  $R_{in} = 2k\Omega$ ,  $\beta = 100$  find the output voltage for an input voltage of 1mV r.m.s **(7 marks)**

c) State and explain FOUR factors used in the classification of transistor amplifiers **(8 marks)**

#### Question Five

a) Define the following terms:

(i) Filter circuit

(ii) Operating point

**(2 marks)**

b) A microphone delivers 72mV at 600  $\Omega$  into an amplifier which deliver 20 watts into a 16 – ohm speaker system at full power. Find the decibel gain of the amplifier. **(5 marks)**

- c) A single stage amplifier has a gain of 80. The collector load  $R_c = 2K \Omega$  and the input impedance is  $400 \Omega$ . Calculate the overall gain when two such stages are cascaded through R.C coupling. **(5 marks)**
- $i_{c \max} = 200mA$   $i_{c(\min)} = 20mA$ ,  $V_{CE(\max)} = 12V$
- d) In a certain transistor power amplifier,  $V_{CE(\min)} = 3V$  and  
. Calculate the a.c. output power. **(5 marks)**
- e) The voltage gain of an amplifier without feedback is 4000. Calculate the voltage gain of the amplifier if negative feedback is introduced in the circuit, given that feedback fraction  $m = 0.0.2$  **(3 marks)**