



TECHNICAL UNIVERSITY OF MOMBASA
Faculty of Applied & Health
Sciences

DEPARTMENT OF MATHEMATICS & PHYSICS

PRE-CERTIFICATE IN INFORMATION TECHNOLOGY (PCIT 13M)

APS 1003: FUNDAMENTALS OF PHYSICS

SPECIAL/SUPPLEMENTARY EXAMINATION

SERIES: OCTOBER 2013

TIME: 2 HOURS

Instructions to Candidates:

You should have the following for this examination

- Answer Booklet
- Mathematical Tables
- Scientific Calculator

This paper consist of **FIVE** questions in **TWO** sections **A & B**

Answer question **ONE (COMPULSORY)** and any other **TWO** questions
Maximum marks for each part of a question are as shown
This paper consists of **THREE** printed pages
SECTION A (COMPULSORY)

Question One

- a) Explain the following terms:
- (i) Doping (1 mark)
 - (ii) P.N. Junction (1 marks)
 - (iii) Barrier voltage (1 marks)
- b) With the aid of a circuit diagram, explain the operation of a full-wave bridge rectifier. (5 marks)
- c) Calculate the length of steel wire of 0.8mm diameter having resistance of $192 \times 10^{-6} \Omega$ (ρ for steel = $0.13 \times 10^{-6} \Omega \cdot \text{m}$) (4 marks)

SECTION B (Answer any TWO questions from this section)

Question Two

- a) Explain the following giving two (2) examples for each:
- (i) Intrinsic semiconductor
 - (ii) Extrinsic semiconductor (4 marks)
- b) With the aid of circuit diagrams show the following transistors configuration:
- (i) Common collector (2 marks)
 - (ii) Common emitter (2 marks)
 - (iii) Common base (2 marks)
- c) Differentiate between:
- (i) Polarized and Non-polarized capacitors
 - (ii) Fixed and variable capacitors (4 marks)

Question Three

- a) Explain the following terms:
- (i) Energy
 - (ii) Power
 - (iii) Charge
 - (iv) Capacitance (4 marks)
- b) With the aid of diagrams, explain how you would perform the following measurement.
- (i) Voltage in a circuit
 - (ii) Current in a circuit
 - (iii) Resistance in a circuit (9 marks)

- c) Differentiate between A.C and D.C. Energy (2 marks)

Question Four

- a) With the aid of a circuit diagram, show how a capacitor can be charged and discharged. (6 marks)
- b) Describe the construction of a transformer. Briefly explain its operation. (5 marks)
- c) Briefly explain how the following can be obtained:
- (i) P-type semiconductor
 - (ii) N-type semiconductor
- (4 marks)

Question Five

- a) Show that for temperature stabilized single stage class A transistor amplifier $V_{CC} = I_C R_C + V_{CE} + I_E R_E$ (5 marks)
- b) Explain the three (3) factor that affect the resistance (R) of a wire (6 marks)
- c) State at least **FOUR** disadvantages of using Zener diode as a voltage regulator. (4 marks)