



# TECHNICAL UNIVERSITY OF MOMBASA

## FACULTY OF ENGINEERING AND TECHNOLOGY

### DEPARTMENT OF MECHANICAL & AUTOMOTIVE ENGINEERING

#### UNIVERSITY EXAMINATION FOR:

DIPLOMA YEAR 3 SEMESTER 2

EPL 2306 : PLANT ELECTRICAL IV

END OF SEMESTER EXAMINATION

**SERIES:** APRIL 2016

**TIME:** 2 HOURS

**DATE:** Pick Date May 2016

#### Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of **FIVE** questions. Attempt any **THREE** questions.

**Do not write on the question paper.**

#### Question ONE

- State FOUR transformation processes of a transformer. (4 marks)
- State the difference between core type and shell type transformer. (4 marks)
- Using first principle, show that the transformation ratio  $K$  is given by:- (6 marks)
$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = K$$
- A 30kVA 2400/120V, 50 Hz transformer has a h.v. winding resistance of  $0.1\Omega$  and leakage reactance of  $0.22\Omega$ . The l.v. resistance is  $0.35\Omega$  and reactance is  $0.012\Omega$ . Calculate the equivalent impedance. (6 marks)

#### Question TWO

- State THREE reasons for conducting transformer test. (3 marks)
- Differentiate between no load test and impedance test of a transformer. (4 marks)
- Explain why transformers are rated in kVA. (3 marks)
- Obtain the equivalent circuit of a 200/400V, 50Hz single phase transformer from the following test data.  
O.C. test : 200V, 0.7A, 70W on l.v. side  
S.C. test: 15V, 10A, 85W on h.v. side  
Calculate the secondary voltage when delivering 5kW, 0.8 power factor lagging, the primary voltage being 200V. (10 marks)

### Question THREE

- State FOUR conditions for parallel operation of 3-phase transformer which does not apply to running of 1-phase transformer. (4 marks)
- State THREE advantages of Delta-Delta transformer configuration. (3 marks)
- Two transformers A and B are connected in parallel to a load of  $(2 + j1.5) \Omega$ . Their impedances in secondary are  $Z_A = (0.15 + j0.5)\Omega$  and  $Z_B = (0.1 + j0.6)\Omega$ . Their no-load terminal voltages are  $E_A = 207 \angle 0^\circ$  and  $E_B = 205 \angle 0^\circ$ . Calculate the power output and power factor of each transformer. (13 marks)

### Question FOUR

- State TWO main parts of an induction motor. (2 marks)
- Give an explanation for each of the following statements:-
  - Rotor slots are skewed
  - The brushes of a phase wound rotor are externally connected to a 3-phase star connected rheostat. (6 marks)
- State THREE differences between squirrel cage induction motors and phase wound induction motors. (3 marks)
- A 4-pole, 50Hz, 3-phase induction motor develops a maximum torque of 110Nm at 1360rpm. The resistance of a star connected rotor is  $0.25\Omega/\text{phase}$ . Calculate the value of resistance that must be inserted in series with each rotor phase to produce a starting torque equal to half-maximum torque. (9 marks)

### Question FIVE

- State THREE factors considered when choosing an electric motor. (3 marks)
- With reference to motor installation and operation, discuss the following requirements and methods:-
  - Location
  - Mounting
  - Alignment and Leveling (6 marks)
- Identify possible causes and corrective measures for each of the following abnormal situations:-
  - Motor starts bumping
  - Over-heating during operation
  - Brush sparking when speed increases excessively (6 marks)
- Calculate the theoretical continuous rating of a motor which has a duty cycle of 20 kW for 2 mins, 5 kW for 2 mins, 10 kW for 3 mins and stopped for three minutes. (5 marks)