



# TECHNICAL UNIVERSITY OF MOMBASA

**Faculty of Engineering and Technology**

**DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING**

**CERTIFICATE IN TECHNOLOGY**

**ELECTRICAL AND ELECTRONICS ENGINEERING (CEEE2)**

**EEE 1101**

**ANALOGUE ELECTRONICS**

**END OF SEMESTER EXAMINATIONS**

**SERIES: APRIL 2016**

**TIME: 2 HOURS**

## **INSTRUCTIONS TO CANDIDATES**

- 1) You should have the following for this examination;
  - Answer booklet
  - Non-programmable calculator
- 2) Answer any **THREE** Questions

#### QUESTION ONE

- a) 1 State three factors that affect the stability of a transistor amplifier  
2 Two possible effects of excessive shift of the Q-point of a Transistor amplifier. 6 Marks
- b) Sketch a labeled output Characteristics curves of a common emitter and show the cut off and Saturation regions 7 Marks
- c) A transistor amplifier operating in Class A mode has the following characteristics  $\Delta I_c = 2\text{mA}$ ,  $R_e = 12\text{K}\Omega$ ,  $I_b = 200\text{mA}$ ,  $V_{ce} = 10\text{V}$ , and  $V_{cc} = 24\text{ Volts}$ . Calculate the current Gain 'B' and the value of the Emitter Current ( $I_e$ ) 7 Marks

#### QUESTION TWO

- a) 1 Define the following as applied to Semi conductor theory  
1. Doping  
2. Extrinsic Semi conductor 3 Marks
- b) With the aid of diagrams, describe how a P-N Junction is formed. 6 Marks
- c) A crystal diode having internal resistance of  $150\Omega$ , is used for half wave rectification. If the applied Voltage is  $V = 50\sin\omega t$ , and the Load resistance is  $R_L = 800\Omega$ , Find  
1.  $I_m, I_{dc}, I_{rms}$   
2. Ac power input and dc power output  
3. Dc output Voltage  
4. Efficiency of rectification 11 Marks

#### QUESTION THREE

- a) Using sketches explain the operation of the following classes of Amplifiers  
Classes A, B, C. 9 Marks
- b) State any three comparisons between BJT and FET. 3 Marks
- c) With the aid of diagrams, describe the construction and operation of an enhancement mode MOSFET. 8 Marks

#### QUESTION FOUR

- a) With the aid of diagrams describe the construction and operation of a Cathode Ray tube employing Electric focussing and deflection system. 11 Marks
- b) 1 Explain the function of the Time base in a CRO.  
2 Explain how time base can be used to display an alternating waveform on an Oscilloscope. 9 Marks

#### QUESTION FIVE

- a) Draw a diagram of a Centre tap full wave rectifier and describe its operation. 10 Marks
- b) Explain the Principle of the following types of Filters  
1 Shunt Capacitor  
2  $\pi$ - Filter

QUESTION ONE

- d) 1 State four factors that affect the stability of a transistor amplifier  
2 Two possible effects of excessive shift of the Quescent point of a Transistor amplifier. 6 Marks
- e) Sketch a labbed output Characteristics curves of a common emitter and show the cut off and Saturation regions 7 Marks
- f) A transistor amplifier operating in Class A mode has the following characteristics  $\Delta I_c = 1\text{mA}$ ,  $R_e = 6\text{K}\Omega$ ,  $\Delta I_b = 100\text{mA}$ ,  $V_{ce} = 5\text{V}$ , and  $V_{cc} = 12\text{Volts}$ . Calculate the current Gain 'B' and the the value of the Emitter Current ( $I_e$ ) 7 Marks

QUESTION TWO

- d) 1 Define the following as applied to Semi conductor theory  
3. Doping  
4. Extrinsic Semi conductor 3 Marks
- e) With the aid of diagrams, describe how a P-N Junction is formed. 6 Marks
- f) A crystal diode having internal resistance of  $200\Omega$ , is used for half wave rectification. If the applied Voltage is  $V = 50\sin\omega t$ , and the Load resistance is  $R_L = 800\Omega$ , Find  
5.  $I_m, I_{dc}, I_{rms}$   
6. Ac power input and dc power output  
7. Dc output Voltage  
8. Efficiency of rectification 11 Marks

QUESTION THREE

- d) Using sketches explain the operation of the following classes of Amplifiers  
Classes A, B, C. 9 Marks
- e) State any three comparisons between BJT and FET. 3 Marks
- f) With the aid of diagrams, describe the construction and operation of an enhancement mode MOSFET. 8 Marks

QUESTION FOUR

- c) With the aid of diagrams describe the construction and operation of a Cathode Ray tube employing magnetic focussing and deflection system. 11 Marks
- d) 1 Explain the function of the Time base in a CRO.  
2 Explain how time base can be used to display an alternating waveform on an Oscilloscope. 9 Marks

QUESTION FIVE

- c) Draw a diagram of a full wave bridge rectifier and describe its operation. 10 Marks
- d) Explain the Principle of the following types of Filters  
1 Shunt Capacitor  
2  $\pi$ - Filter 10 Marks