



TECHNICAL UNIVERSITY OF MOMBASA

FACULTY OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

UNIVERSITY EXAMINATION FOR:

Bachelor of Science in Electrical and Electronic Engineering

EEE 2404: POWER ELECTRONICS II

END OF SEMESTER EXAMINATION

SERIES: MAY 2016

TIME: 2 HOURS

DATE: Pick Date Select Month Pick Year

Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of **five** Questions; Answer any **THREE** Questions.

Do not write on the question paper.

Question ONE

- a) Figure Q1 shows a circuit that is used to control the load power. Describe its operation. Include the waveforms of the six, voltages and currents indicated. **(8 marks)**

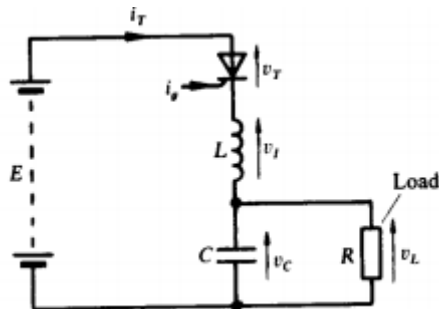


Figure Q1

- b) An ideal chopper operating at a frequency of 500 Hz supplies a load of 3Ω having an inductance of 9 mH from a 60 V battery. Assuming the load is shunted by a perfect commutating diode, and the battery is lossless,
- Determine the load current waveform for on/off ratios of:

I	1/1
II	4/1
III	1/4
 - Calculate the mean voltage and current at each setting in (i). **(12 marks)**

Question TWO

- Draw the circuit diagram of a buck converter using ideal switch and ideal diode and explain its operation. Sketch the equivalent circuit for the operational conditions assuming continuous conduction mode. **(9 marks)**
- Figure Q2 is a circuit diagram of an ideal synchronous buck regulator using ideal switches. Given that it is switching at 200 kHz, input voltage is **27.2V**, output voltage is **13.6V**, output load is 1.36Ω and peak to peak ripple current in inductor is 4A, determine:
 - Period, Duty cycle, T_{off} , T_{on} of the low side switch.
 - Output power, Average Input current.
 - The Value of the inductance, Average inductor current.
 - The value of the capacitance needed to obtain a 20mVpp ripple.
 - Draw the inductor current waveform for two periods.**(11 Marks)**

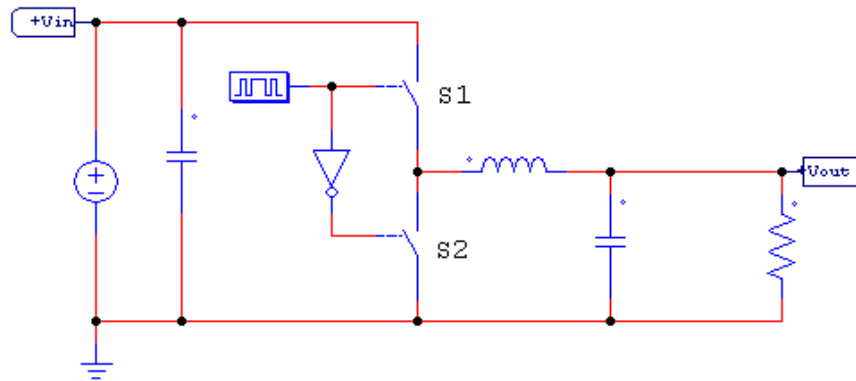


Figure Q2

Question THREE

- With reference to full bridge dc-dc converter,
 - differentiate between PWM with bipolar voltage switching and PWM with unipolar voltage switching.
 - Explain the term 'blanking time' **(3 marks)**
- In a full-bridge dc-dc converter utilizing PWM bipolar voltage switching, $v_{control} = 0.5 V_{tri}$. Obtain V_o and I_{d1} in terms of given V_d and I_o . By Fourier analysis, calculate the amplitudes of the switching-frequency harmonics in v_o and i_d . Assume that $i_o(t) = I_o$.

Question FOUR

- a) Give ONE disadvantage and TWO disadvantages of high switching frequency in inverters.
(3 marks)
- b) In the circuit of Figure Q4, $V_d = 300$, $m_a = 0.8$, $m_f = 39$, and fundamental frequency is 47 Hz. Use Table Q4 to calculate the rms voltage values at:
- the fundamental frequency
 - harmonic frequencies of 37, 77 and 115.
- (8 marks)

Table Q4: Generalized Harmonics of v_{Ao} for a Large m_f .

h \ m_a	0.2	0.4	0.6	0.8	1.0
1	0.2	0.4	0.6	0.8	1.0
<i>Fundamental</i>					
m_f	1.242	1.15	1.006	0.818	0.601
$m_f \pm 2$	0.016	0.061	0.131	0.220	0.318
$m_f \pm 4$					0.018
$2m_f \pm 1$	0.190	0.326	0.370	0.314	0.181
$2m_f \pm 3$		0.024	0.071	0.139	0.212
$2m_f \pm 5$				0.013	0.033
$3m_f$	0.335	0.123	0.083	0.171	0.113
$3m_f \pm 2$	0.044	0.139	0.203	0.176	0.062
$3m_f \pm 4$		0.012	0.047	0.104	0.157
$3m_f \pm 6$				0.016	0.044
$4m_f \pm 1$	0.163	0.157	0.008	0.105	0.068
$4m_f \pm 3$	0.012	0.070	0.132	0.115	0.009
$4m_f \pm 5$			0.034	0.084	0.119
$4m_f \pm 7$				0.017	0.050

Note: $(\hat{V}_{Ao})_{h/2} / V_d [= (\hat{V}_{AN})_{h/2} / V_d]$ is tabulated as a function of m_a .

- c) In a single-phase full-bridge PWM inverter, the input dc voltage varies in the range 295-325V. Due to low distortion requirements in the output voltage v_o , $m_a = 1.0$.
- Determine the highest V_{o1} that can be obtained and indicated on its nameplate as its voltage rating.
 - Its nameplate volt-ampere rating is specified as 2000 VA, that is $V_{o1max} \times I_{o1max}$, where i_o is assumed to be sinusoidal. Calculate the combined switch utilization ratio when the inverter is supplying its rated volt-ampere.
- (9 marks)

Question FIVE

- a) Differentiate between ;
- Equation solvers and circuit oriented simulations.
 - Differentiate between load – resonant and resonant – switch converters
- (4 marks)
- b) Draw a diagram of a half-bridge series loaded converter and explain its operation.
- (6 marks)

c) Explain the effects of the following disturbances:

- (i) Overvoltage
- (ii) Voltage spikes
- (iii) harmonics.

(3 marks)

d) A parallel capacitor chopper of Figure Q5(d) has a load of 5Ω supplied from a 24V battery. The required turn-off time for thyristor T_1 is $60\mu\text{s}$. Determine:

- (i) the size of capacitor.
- (ii) the appropriate minimum on-time for thyristor T_1 if $R_2 = 5R_1$

(7 marks)

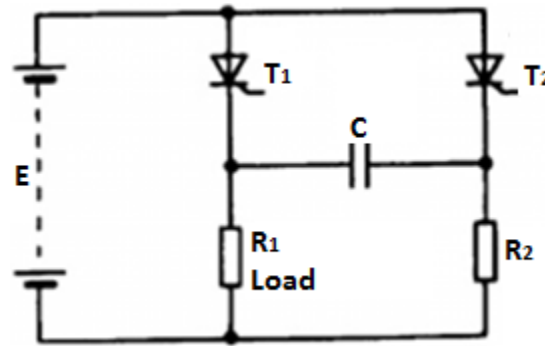


Figure Q5(d)