



# TECHNICAL UNIVERSITY OF MOMBASA

---

FACULTY OF ENGINEERING & TECHNOLOGY

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

## UNIVERSITY EXAMINATION FOR:

DIPLOMA IN TECHNOLOGY (ELECTRICAL POWER ENGINEERING)(DEPE2)

EEE 2101 : ANALOGUE ELECTRONICS 1.

## END OF SEMESTER EXAMINATION

**SERIES:** MAY 2016

**TIME:** 2 HOURS

**DATE:** MAY 2016

### Instructions to Candidates

You should have the following for this examination

*-Answer Booklet, examination pass and student ID*

This paper consists of FIVE questions. Attempt **ANY THREE Questions**

**Do not write on the question paper.**

---

### Question ONE

a) Explain the following terms as used in diodes

- i. Avalanche breakdown
- ii. Zener effect

(b) With the aid of a construction diagram explain the NPN transistor action (10 marks)

c) Distinguish between the following classes of amplifiers illustrating with waveforms:-

- i. class A
- ii. class B
- iii. class C

(6 marks)

(d)(i) With the aid of a circuit diagram explain the operation of a voltage doubler.

(ii) Explain the following terms as applied to cathode ray oscilloscope:-

- I. Time base
- II. Synchronization

(4marks)

## Question TWO

a)(i) Explain any TWO factors that affect the Q-point of an amplifier

(ii) State how the factors in a(i) can be minimized (6marks)

(b)(i) Explain the term “ Thermal runaway”

(ii) State any TWO effects of thermal runaway

(4marks)

c)(i) For figure 1 circuit determine the values of:-

I. Collector current  $I_C$

II.  $V_{CE}$

Take  $V_{BE} = 0.6V$  and  $h_{fe} = 100$

(ii) Determine the new values of c(i) if a resistor of  $1k\Omega$  is connected between emitter and ground

(6marks)

(d)(i) Explain how d.c stabilization is achieved in an emitter feedback biasing circuit.

(ii) State the effect of removing the emitter decoupling capacitor in the biasing circuit of d(i)

(6marks)

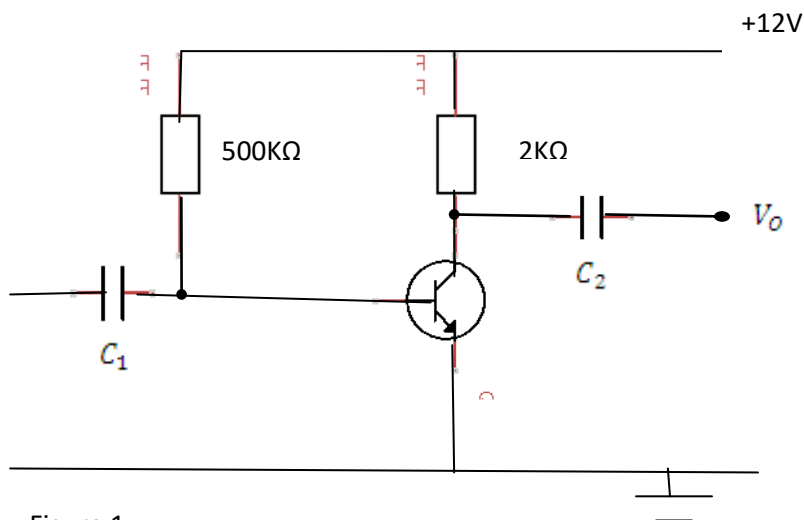


Figure 1

## Question THREE

(a)(i) State any THREE methods of biasing a transistor

(ii) Explain TWO purposes for each of the following

- I. d.c loadline
- II. a.c loadline

(b) The characteristics of a BJT are given in table 1 below

The transistor has a collector load of  $1500\Omega$ , a supply voltage of  $6V$  and a bias current of  $40\mu A$

- i. Plot the characteristics
- ii. Draw the d.c and a.c loadlines on the characteristics
- iii. Calculate the power dissipated in the transistor
- iv. Calculate the total voltage swing at the collector for an a.c input signal current of  $40\mu A$  peak in the base

| $V_{CE}$ | Collector Current $I_C$ (mA) |               |               |
|----------|------------------------------|---------------|---------------|
|          | $I_b=0$                      | $I_b=40\mu A$ | $I_b=80\mu A$ |
| 1        | 0.2                          | 1.90          | 3.7           |
| 4        | 0.3                          | 2.05          | 4.0           |
| 7        | 0.4                          | 2.20          | 4.3           |

Table 1

#### Question FOUR

(a) Define the following terms as applied to power supplies:-

- i. Ripple
- ii. Peak Inverse voltage

(b)(i) Draw a circuit diagram of a full wave bridge rectifier and explain its operation with the aid of waveforms.

(ii) State any TWO advantages of full wave bridge rectifier over the centre-tapped.

(iii) With the aid of a circuit diagram explain the operation of a zener diode regulator when:-

- I. The load varies
- II. The input voltage varies

(14marks)

c) A  $5.6V, 1W$  zener diode regulator having a minimum current of  $5mA$  is used in a shunt regulator to supply a constant load current of  $20mA$  from a supply voltage which varies between  $15V$  and  $24V$ . Calculate:-

- i. the suitable value of series resistor  $R_s$
- ii. the power rating of  $R_s$  in C(i) above
- iii. the power dissipated by the zener diode when the supply is at its maximum

(6marks)

### Question FIVE

(a)(i) With the aid of a construction diagram describe the operation of an n-channel JFET

(ii) State any TWO differences between  $FET_S$  and  $BJT_S$

(10 marks)

(b) For the JFET amplifier of figure 2  $g_m=2000\mu S$ , Determine:-

- i. Its input impedance
- ii. a.c output resistance
- iii. output voltage

(6marks)

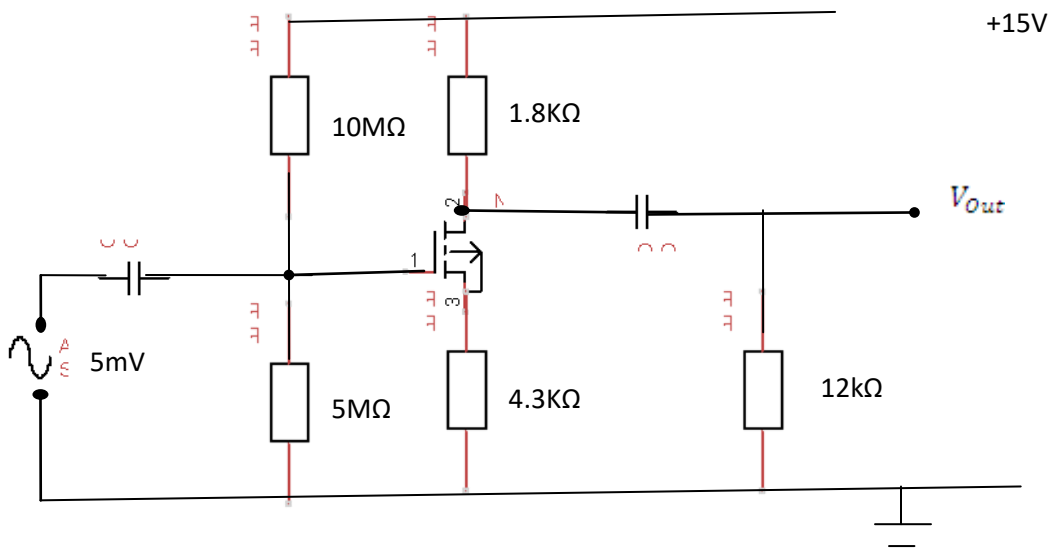


Figure 2:

c) Explain the following terms as applied in FETs

- i. pinch-off voltage
- ii. Transconductance

(4marks)