

TECHNICAL UNIVERSITY OF MOMBASA
FACULTY OF ENGINEERING AND TECHNOLOGY
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING
EEP 2104 CIRCUIT THEORY II

SERIES: MAY 2016

Instructions

- This paper consists of FIVE questions
- Answer any THREE questions
- All Questions carry equal marks

QUESTION ONE

- (a) A coil having resistance of 10Ω and inductance of 0.2H is connected in series with a capacitor of capacitance $80\mu\text{F}$ across a 240V , 50Hz supply. Draw the circuit diagram and calculate:
- The current in the circuit
 - Voltages V_R , V_L , and V_C
 - The phase angle and draw the phasor diagram (11 marks)
- (b) Distinguish between average value and instantaneous value (4 marks)
- (c) Explain the following terms and give their expressions.
- RMS value
 - Form factor (5 marks)

QUESTION TWO


- (a) With the aid of diagrams explain the functions of the following in analogue instruments
- Air current damping device
 - Control device (8 marks)
- (b) A coil of conductor is rotating within a magnetic field. Draw the sine wave and the generated emf is given by $e = 2\pi BANn\sin\theta$ (6 marks)
- (c) (i) Explain the importance of power factor improvement in ac circuits.
(ii) Draw the phasor diagrams for each of the following circuits:
- Ac circuit having resistance only
 - Ac circuit having inductance only
 - Ac circuit having capacitance only (7 marks)

QUESTION THREE

- (a) A resistance of 15Ω , an inductance of 0.18H and a capacitance of $60\mu\text{F}$ are connected in parallel across a 220V , 50Hz supply. Calculate:
- The current on each branch
 - The supply current
 - The phase angle and draw the phasor diagram (11 marks)
- (b) Explain the following terms:
- Admittance
 - Reluctance
 - Susceptance (3marks)
- (c) A resistance of 20Ω , an inductance of 0.12H and capacitance of $50\mu\text{F}$ are connected in series. Calculate the impedance using:
- Rectangular notation
 - Polar notation (6 marks)

QUESTION FOUR

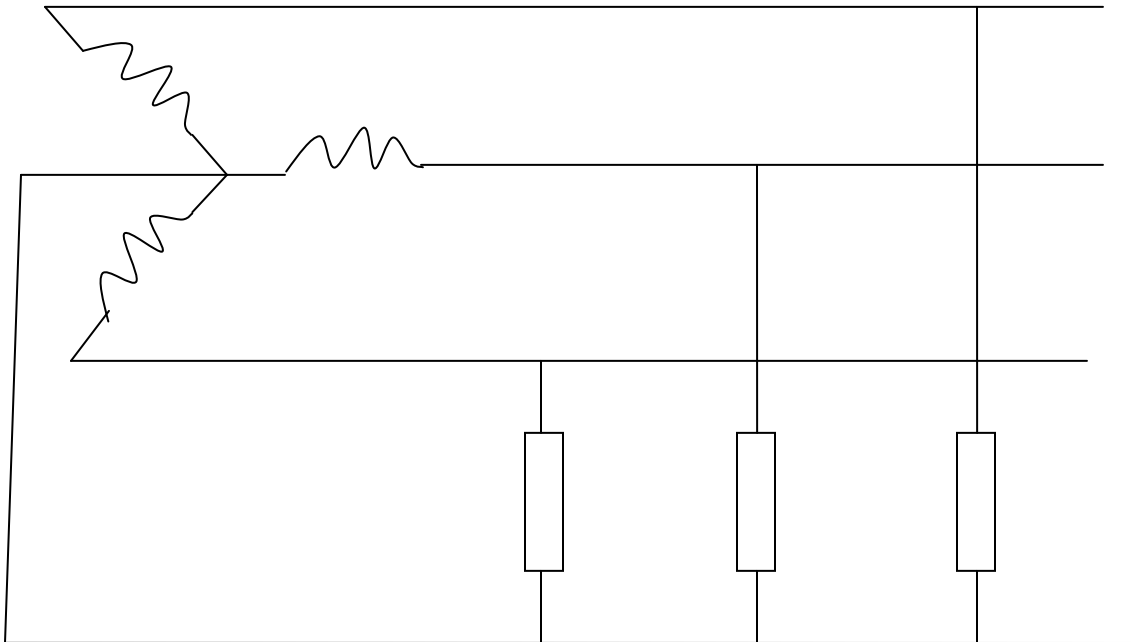- (a) For the circuit of figure Q4a, calculate
- Current in each line
 - The current in the neutral conductor
- (12 marks)



- (b) Draw the waveforms for three phase emfs and state expressions for line and phase currents in:
- Star-connected supply
 - Delta connected supply
- (8 marks)

QUESTION FIVE

- (a) (i) State the expression for power in a three phase system
- (ii) A three phase delta connected motor operating off a 415V system is developing 25kW at an efficiency of 0.95p.u. and a power factor of 0.9. Calculate:
- The line current
 - The phase current
- (6 marks)

- (b) With the aid of a diagram explain the operation of a permanent magnet moving coil instrument.
(7 marks)

- (c) With the aid of a diagram explain the two-meter method of power measurement in three phase systems.
(7 marks)

