



TECHNICAL UNIVERSITY OF MOMBASA

FACULTY OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF MEDICAL ENGINEERING

UNIVERSITY EXAMINATION FOR:

DIPLOMA IN MEDICAL ENGINEERING (DME 315)

EEP 2152: ELECTRICAL ENGINEERING SCIENCE

END OF SEMESTER EXAMINATION

SERIES: APRIL 2016

TIME: 2 HOURS

DATE: 9 May 2016

Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of **FOUR** questions. Attempt question ONE (Compulsory) and any other TWO questions.

Do not write on the question paper.

Question ONE (Compulsory)

(a) With reference to a simple cell, explain:

- (i). Polarisation
- (ii). Local action

(4 marks)

(b) (i) State Kirchhoff's laws.

(4 marks)

- (ii) Applying Kirchhoff's laws determine the currents flowing in each branch of the network given Figure Q1.

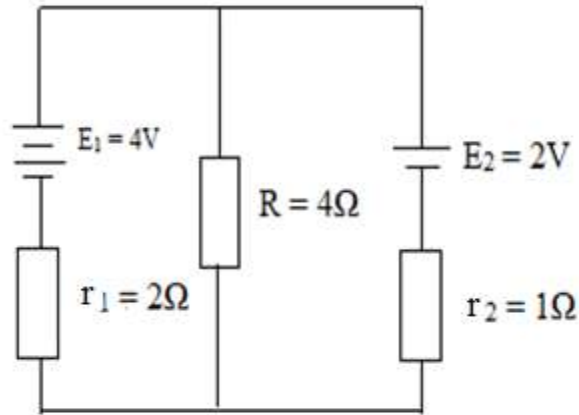


Fig. Q1

(10 marks)

- (c) (i) State any **FOUR** characteristics of magnetic flux lines. **(4 marks)**
- (ii) Describe the processes that occur when the cell is:
- (I) Charging
 - (II) Discharging

(8 marks)

Question TWO

- (a) (i) Define the capacitance of a capacitor. **(2 marks)**
- (ii) State superposition theorem. **(2 marks)**

- (b) Applying superposition theorem determine the current in each branch of the network given Fig. Q2(a).

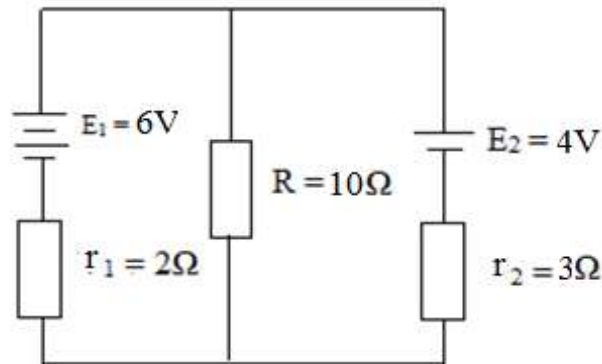


Fig. Q2(a)

(10 marks)

- (c) Applying current division principle for the circuit given Fig. Q2(b) show the relationship between the supply current and the branch currents.

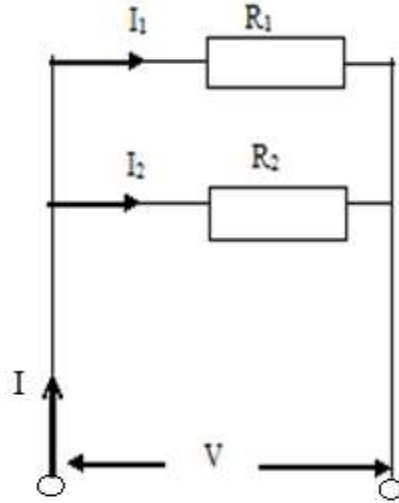


Fig. Q2(b)

(6 marks)

Question THREE

- (a) State the procedure followed to determine electrical quantities in active networks applying Thevenin's theorem. (4 marks)
- (b) (i) With the aid of a diagram describe the construction of primary cell. (8 marks)
(ii) State **THREE** applications of secondary cells. (3 marks)
- (c) Given that two parallel rectangular plates measuring 20cm by 40cm carrying an electric charge of $0.2\mu\text{C}$. Determine:
- (i) Electric flux density
(ii) Electric field strength if the plates are spaced 5mm apart and the voltage between them is 0.25KV.

(5 marks)

Question FOUR

- (a) (i) State the difference between ideal constant voltage generator to ideal constant current generator. (4 marks)
(ii) Describe **THREE** types of magnetic materials giving an example in each. (6 marks)
- (b) For the given circuits network Fig. Q4(b), determine:
- (I) Equivalent capacitance
(II) The voltage across AB
(III) The charge on each capacitor

(10 marks)

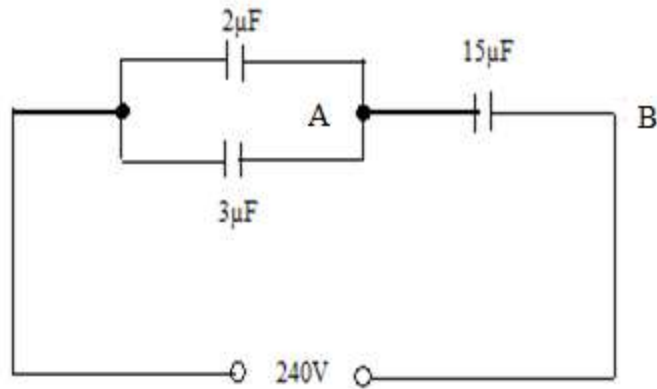


Fig. Q4(b)

Question FIVE

(a) With aid of a diagram describe hysteresis loop as exhibited in a ferromagnetic material. **(10 marks)**

(b) (i) Given that a 250-KVA, 11000V/415V, 50Hz single phase transformer has 80 turns on the secondary winding. Determine:

- (I) Primary and secondary currents
- (II) Primary turns
- (III) Maximum value of the flux

(5 marks)

(ii) Given that 12V battery is connected in a circuit having three series-connected resistors of 4Ω, 9Ω and 11Ω. Determine:

- (I) Current flowing through the circuit
- (II) Voltage across 9Ω resistor
- (III) Power dissipated in the 11Ω resistor

(5 marks)