



TECHNICAL UNIVERSITY OF MOMBASA

Faculty of Engineering and Technology

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING
UNIVERSITY EXAMINATIONS 2016/2017
FOR THE DEGREE OF BACHELOR OF SCIENCE IN ELECTRICAL AND ELECTRONIC
ENGINEERING

EEE 2210:ANALOGUE ELECTRONICS II

END OF SEMESTER EXAMINATIONS

SERIES: MAY, 2016

TIME: 2 HOURS

INSTRUCTIONS:

1. You should have the following for this examination:
 - Answer booklet
 - Non-Programmable Scientific calculator
 2. This paper consists of **FIVE** questions
 3. Answer **QUESTION ONE** and other **TWO** Questions.
 4. Do not write on the question paper.
 5. *This paper consists of FOUR printed pages.*
-

Question ONE

- (a) Consider Fig.Q1, CE circuit. Draw:
- (i) DC load line
 - (ii) AC load line
 - (iii) Determine the maximum peak-to-peak signal that can be obtained
- (14.5 marks)

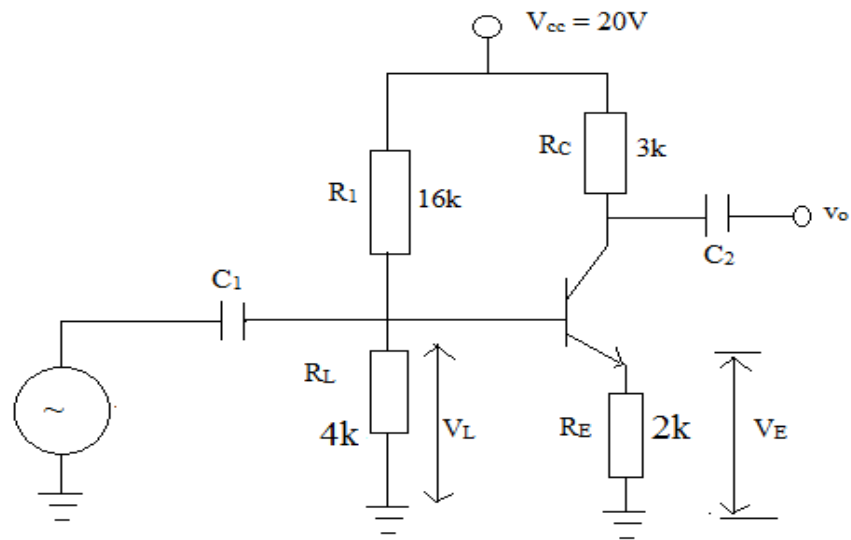


Fig. Q1

- (b) (i) State at least **THREE** reasons for the popular use of h-parameters.
(ii) A transistor used in CE arrangement had the following set of h-parameters when the d.c operating point is:
 $V_{CE} = 15V$ and $I_C = 1mA$.
 $H_{ie} = 2500\Omega$, $h_{oe} = 10^{-4}mho$, $h_{ie} = 10^{-3}$, $h_{fe} = 40$

The as load line seen by the transistor is $r_L = 500\Omega$. Determine the Approximate values using reasonable approximation of the following:

- (I) Input impedance
(II) Current gain
(III) Voltage gain and comment on its sign.
- (c) (i) Discuss negative feedback in amplifiers.
(ii) Consider an amplifier of 60dB gain, output impedance $f_o = 10k\Omega$. It is required to modify its output impedance to 500Ω by applying negative feedback. Calculate:
- (I) The value of the feedback.
(II) The percentage change in the overall gain for 10% change in the gain of the interval amplifier.

Question TWO

(a) For the transistor amplifier show in Fig. Q2, $h_{ie} = 1.5k\Omega$, $h_{fe} = 100$, $h_{re} = 3 \times 10^{-4}$,

$h_{oe} = 25\mu\text{hos} = \frac{1}{40k}$. Calculate:

- (i) A_i
- (ii) R_i
- (iii) A_v
- (iv) x/o

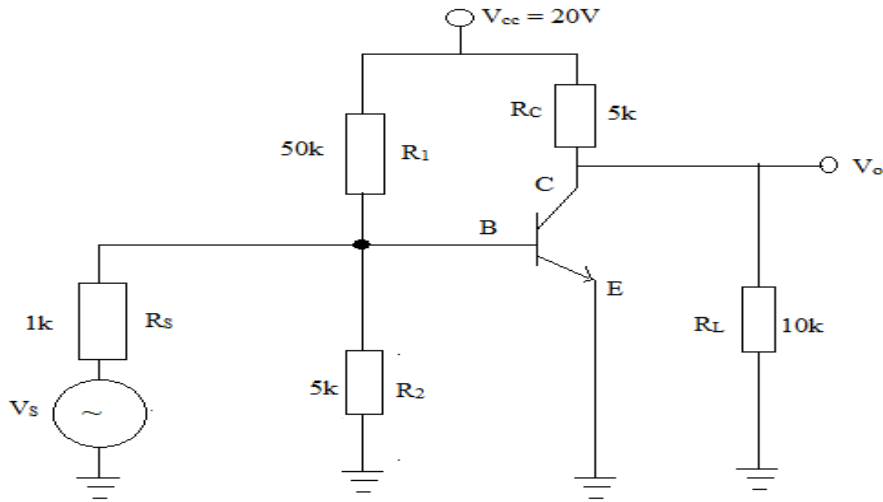


Fig. Q2

(c) Consider a Silicon Controlled Rectifier (SCR).

- (i) Draw the circuit symbol
- (ii) Briefly describe the principle of operation.

(3.5 marks)

Question THREE

(a) Name the **FOUR** basic arrangements for using negative feedback and the block diagrams to differentiate them.

(8 marks)

- (b) With the aid of a block diagram show how negative feedback can increase the input impedance of an amplifier.

(4 marks)

- (c) Consider the amplifier of 60dB. A negative feedback of $\beta = 0.005$ is applied. Determine the change in overall gain of the feedback amplifier if the interval amplifier is subjected to a gain reduction of 10%.

(8 marks)

Question FOUR

- (a) (i) Draw the circuit of a generalized FET amplifier with a source resistance R_s and a drain resistance R_d .
- (ii) Draw the small-signal equivalent circuit of (a)(i).
- (iii) Determine the Thevenin's equivalent circuit looking into the drain at low frequency.

(11.5 marks)

- (b) Define:

- (i) Transconductance, g_m
- (ii) Drain resistance, r_d
- (iii) Pinch off voltage
- (iv) Amplification factor, μ

(4 marks)

- (c) In an FET amplifier, the load resistance $R_L = 10k\Omega$, $R_G = 1m\Omega$, $R_s = 1k\Omega$, $C_s = 25\mu F$, $\mu = 25$, $r_d = 80k\Omega$. If the input signal voltage is 0.1V at a frequency of 1 μ Hz, find the output signal voltage of the amplifier.

(4.5 marks)

Question FIVE

- (a) Consider a triac:
- (i) Draw the basic structure diagram
- (ii) Draw the circuit symbol.
- (iii) I-V characteristics

- (iv) Briefly describe the principle of operation
- (v) State at least two applications

(14.5 marks)

(b) A given silicon UJT has an inter-base resistance of $8k\Omega$, $R_{BI} = 5k\Omega$, with $I_E = 0$, find:

- (i) UJT current if $V_{BB} = 30V$ V_E is less V_P
- (ii) Z and standoff voltage
- (iii) Peak point voltage, V_p

(5.5 marks)