



# TECHNICAL UNIVERSITY OF MOMBASA

FACULTY OF ENGINEERING AND TECHNOLOGY

ELECTRICAL ENGINEERING DEPARTMENT

## UNIVERSITY EXAMINATION FOR:

BACHELOR OF SCIENCE IN ELECTRICAL AND ELECTRONIC ENGINEERING

EEE2511: POWER SYSTEM ANALYSIS I

## END OF SEMESTER EXAMINATION

**SERIES: MAY 2016**

**TIME: 2 HOURS**

**DATE:** Pick Date Select Month Pick Year

### Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of **five** Questions; Question ONE is compulsory. In addition attempt any Other TWO Questions.

**Do not write on the question paper.**

### Question ONE (Compulsory 30 marks)

a)

- Explain with the aid a sketch the FOUR kinds of power injections to a given bus
- State the elements responsible for kinds of power injections above

**(6 Marks)**

b) Show that for a TWO bus system the power flow equation is given by:

$$P_p = |V_p|^2 G_{pp} + |V_p||V_q|G_{pq} \cos(\theta_p - \theta_q) + |V_p||V_q|B_{pq} \sin(\theta_p - \theta_q)$$

$$Q_p = -|V_p|^2 B_{pp} + |V_p||V_q|G_{pq} \sin(\theta_p - \theta_q) - |V_p||V_q|B_{pq} \cos(\theta_p - \theta_q)$$


**(8 Marks)**

c)

- Highlight any THREE challenges faced by power transmission planners in a developing country
- State THREE important stakeholders in power system planning

**(6 Marks)**

d) Determine the Y matrix for the Five Bus power system Figure 1 below:

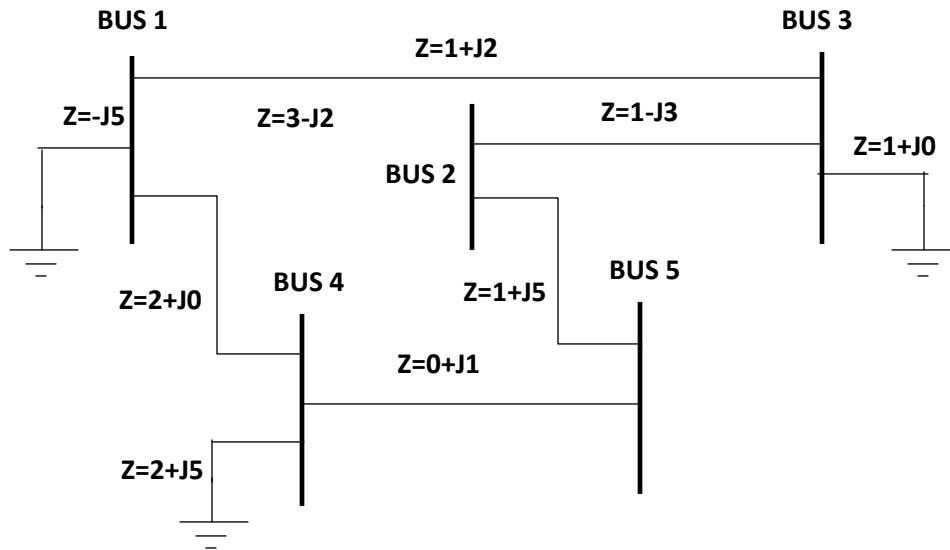

**Figure 1**

**(10 Marks)**

**Question TWO**

- a)
  - i. State any FOUR benefits provided by digital computer in load flow analyses
  - ii. Explain FOUR limitations of Fast Decoupled Load flow algorithms

**(8 Marks)**

b) Show that for Fast Decoupled Load Flow technique:-

$$\frac{\Delta P}{\Delta V} = [B'] \Delta \theta$$

hence determine voltage and angle after TWO iterations for a 3-bus system having Y matrix given by:

$$\begin{vmatrix} -34.43 & 14.3 & 20 \\ 14.3 & -24.3 & 10 \\ 20 & 10 & -30 \end{vmatrix}$$


**(12 Marks)**

**Question THREE**

- a) State any FOUR: -
  - i. inter-relationship between active power, reactive power, voltage and phase angle of a practical power system during steady state operation
  - ii. precautions taken while using Gauss-seidel technique in power flow analysis

**(8 Marks)**

b) A TWO bus system is shown in Fig 2 below:

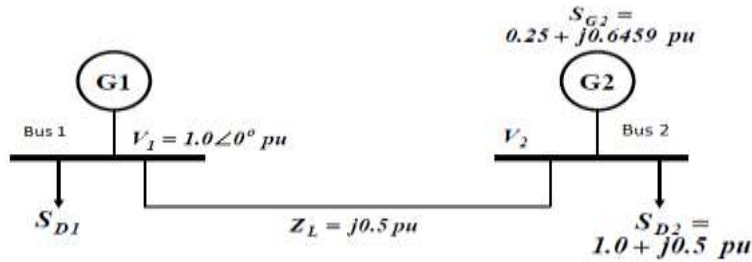

**Figure 2**

- c) The line impedances are as indicated in per unit on 100MVA base. Using Gauss-Seidel method:-
- Classify each bus
  - Find bus admittance matrix
  - Determine bus 2 voltage after FOUR iterations.
  - Estimate bus 1 real and reactive power.

**(12 Marks)**

#### Question FOUR

- a)
- Define load forecasting with respect to power systems
  - Highlight any FIVE factors causing load changes in a power system
  - Explain how load forecasting can be classified

**(11 Marks)**

b) The admittance matrix of a power system is given as:

$$Y_{bus} = j \begin{bmatrix} -13 & 5 & 4 & 0 \\ 5 & -13.5 & 2.5 & 2 \\ 4 & 2.5 & -9 & 2.5 \\ 0 & 2 & 2.5 & -4.5 \end{bmatrix} \text{ per unit}$$

- c) Given that current voltages  $V_1$ ,  $V_2$ ,  $V_3$  and  $V_4$  are 1 p.u each in magnitude and corresponding angles are  $0^\circ$ ,  $20^\circ$ ,  $30^\circ$  and  $-45^\circ$  respectively, estimate the load forecast in  $t = 10$  years assuming an exponential load growth given by  $I = ce^{dx}$  where constants  $c$  and  $d$  are 1.2, and 2 respectively


**(9 Marks)**

#### Question FIVE

- a)
- State any THREE assumptions made while using Newton Raphson algorithm for load flow analysis
  - State TWO advantages and TWO disadvantages of Newton Raphson Technique for power flows over Gauss Seidel

**(7 Marks)**

b) A THREE bus power system is as shown in Figure 3 below:

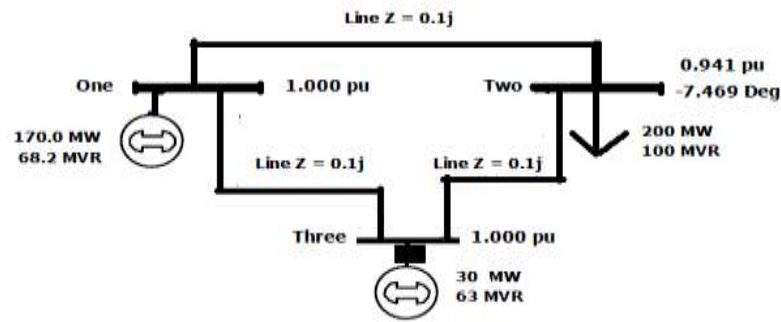

**Figure 3**

Apply the Newton- Raphson power flow to determine the voltage magnitude and angle at bus two. Assume that bus one is the slack and take base of 100 MVA

**(13 Marks)**