



TECHNICAL UNIVERSITY OF MOMBASA

FACULTY OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF MEDICAL ENGINEERING

UNIVERSITY EXAMINATION FOR:

DIPLOMA IN MEDICAL ENGINEERING

EHL 2301: MEDICAL ELECTRONICS III

END OF SEMESTER EXAMINATION

SERIES: APRIL 2016

TIME: 2 HOURS

DATE: 16 May 2016

Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of **FIVE** questions. Attempt question ONE (Compulsory) and any other TWO questions.

Do not write on the question paper.

QUESTION ONE

(a) With the aid of diagrams describe how a unijunction transistor (UJT) can be used in a relaxation oscillator. Show the output wave forms generated. **(8marks)**

(b)



A 250Ω resistor is connected in series with the gate of a thyristor as shown in fig.Q1 . The gate current required to fire the SCR is 8 Ma. Calculate the value of the input voltage V_{in} for causing the SCR to breakdown . **(4 marks)**

(c) State the nature of failures common with the following components.

(i) resistors

(ii) variable resistors

(iii) capacitors

(iv) semi conductors devices.

(8marks).

(d) (i) Using labelled diagrams explain the operation of a diac.

(4marks)

(ii) explain the construction of an SCR.

(6 marks)

QUESTION TWO

(a).Derive an expression to show that the average voltage through a reverse blocking thyristor is approximately $\frac{V_{MAX}}{\pi}$. **(6 marks)**

(b) A thyristor is used to control the voltage to a resistive load. If $240V_{RMS}$ is used to supply the circuit and the SCR fires 2.0msec after the commencement of every cycle,determine the average current to the load if it has a resistance of 500Ω . **(14 marks)**

QUESTION THREE

(a) Describe the construction and operation of a triac .

(10 marks)

(b) With the aid of a labelled diagram describe a circuit to control the brightness of an incandescent lamp using a triac.

(10 marks)

QUESTION FOUR

(a) Discuss the following methods of fault diagnosis

(i) half split

(ii) end to end

(6 marks)

(b) Briefly describe the following devices:-

(i) tunnel diode

(ii) UJT

(10 marks)

(c) Outline any four applications of thyristors.

(4 marks)

QUESTION FIVE

(a) Discuss the following as causes of failure in components.

(i) operating stress

(ii) Environmental stress

(9 marks)

(b) Explain the following terms as used in maintenance.

(i) Redundancy

(ii) availability

(iii) corrective maintenance

(6 marks)

(c) Discuss any two advantages of using a thyristor as a switch over mechanical switches.

(5marks).