



TECHNICAL UNIVERSITY OF MOMBASA

Faculty of Engineering and Technology

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

UNIVERSITY EXAMINATION FOR:

CERTIFICATE IN ELECTRICAL POWER ENGINEERING (CEPE 2) PP2

ELECTRICAL TECHNOLOGY

EEP1201

END OF SEMESTER EXAMINATION SERIES:

MAY 2016

TIME: HOURS

DATE:

Instructions to Candidates

You should have the following for this examination

Answer booklet, examination pass and student ID

This paper consists of five Questions; Attempt any THREE Questions.)

DO NOT WRITE ON THE QUESTION PAPER.

QUESTION ONE

(i) Define the following terms:-

- I. Transients
 - II. Time constant
 - III. Steady state current
- (6marks)

(ii) A coil of inductance 3H and resistance 10Ω is suddenly connected to a 50V a.c supply .
Determine :

- I. The time constant
 - II. The current after 0.5sec
 - III. Voltage across the resistor
 - IV. The current across the resistor
- (7marks)

(a) (i) Describe the transient response for current decay in an L-R Circuit .

(ii) State the effects of the following elements on an A.C . circuit:-

- (I)Resistor (II) Inductor (III) Capacitor (7marks)

QUESTION TWO

a) (i) Draw a diagram of a complex wave consisting of a fundamental and a third harmonic.

(ii) State three causes of harmonics
(8marks)

b) (i) Explain the three effects of harmonics

(ii) Draw a diagram of a complex wave consisting of a fundamental and second harmonic
(8marks)


c) State three effects of harmonics (4marks)

QUESTION THREE

(a) State the following theorems in relation to electrical network analysis:-

- I. Thevenin's theorem
 - II. Norton's theorem
- (6marks)

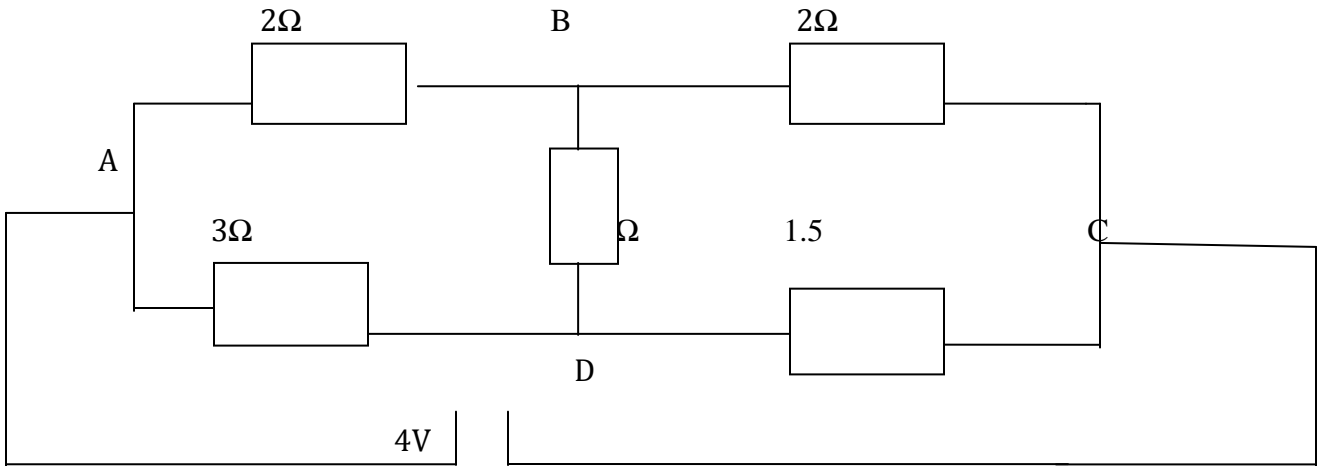(b) Determine the thevenin's equivalent circuit with respect to terminal BD of the circuit shown in figure 1



(C)

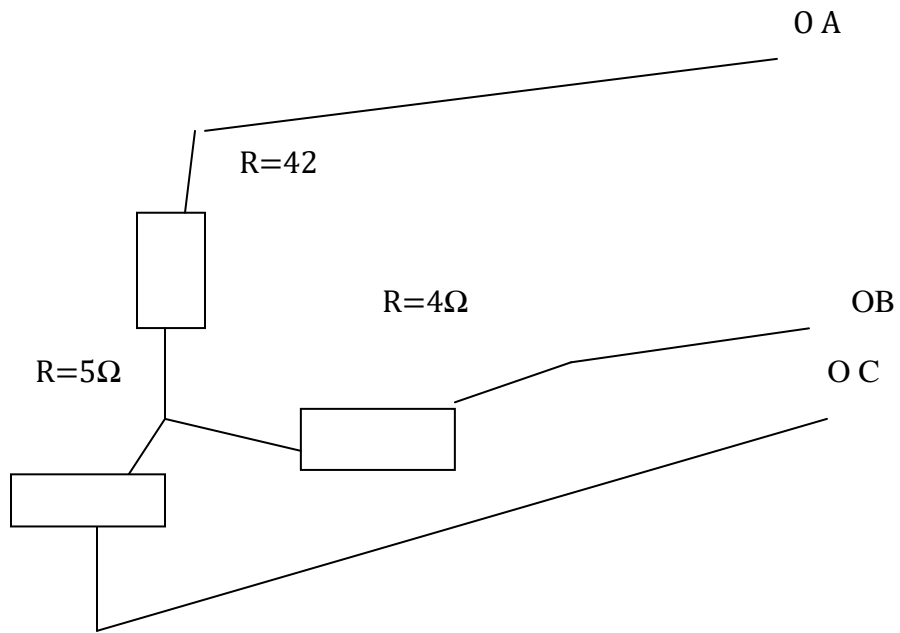


Fig 2

Three resistors 5Ω , 3Ω and 4Ω are connected star as shown in figure 2. Determine the equivalent delta connected networks showing resistances between corresponding pairs of terminals. (6 marks)

QUESTION FOUR

- (a) (i) With the aid of a diagram show the production of rotating magnetic field (6marks)
- (b) Explain :-
- I. Why an induction motor does not run as synchronous speed
 - II. Slip as applied to an induction motor
 - III. The production of torque in the rotor of a three-phase induction motor. (9marks)
- (c) State four reasons why we use starter three phase induction motors. (5marks)

QUESTION FIVE

a (i) State two methods of connecting the windings of a three phase generator and explain how they are carried out (5marks)

(ii) Describe what is meant by a three phase three wire supply and mention two advantages of such a system over a single phase (5marks)

b(i) Calculate total power taken from a three phase, 415 V(line) supply by three 50Ω resistor when they are connected (i) in star (ii) In delta

(ii) State two methods of power measurements in a three phase supply and explain how they are connected to the supply. (4marks)

