



# TECHNICAL UNIVERSITY OF MOMBASA

FACULTY OF ENGINEERING & TECHNOLOGY

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

## UNIVERSITY EXAMINATION 2016/2017

THIRD YEAR SECOND SEMESTER EXAMINATION FOR THE  
DEGREE OF BACHELOR OF TECHNOLOGY AND APPLIED PHYSICS

### EEE 4350: DIGITAL ELECTRONICS & DEVICES

END OF SEMESTER EXAMINATION

**SERIES: DECEMBER 2016**

**TIME: 2 HOURS**

**DATE:** Pick DateSelect MonthPick Year

#### Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of FIVE questions. Attempt **Question ONE (Compulsory)** and any other **TWO Questions**


**Do not write on the question paper.**

#### Question ONE

- a. De-Morganize the Boolean expression below and implement the simplified expression using a minimum number of NAND gates.

$$Y = \overline{(A \cdot B + C)} \cdot \overline{(A + B \cdot C)} \quad (8 \text{ marks})$$

- b. With the aid of a block diagram, XOR implementation and truth table describe the operation of a full-adder. (9 marks)
- c. In a 4-stage ripple counter, the propagation delay of a Flip-flop is 50 ns. If the pulse width of the strobe is 30 ns, find the maximum frequency at which the counter operates reliably. (2 marks)
- d. For the circuit given in **Figure Q1**, sketch the output signal at  $Q_2$  for five clock periods. Assume that the two flip-flops are initially cleared. (5 marks)

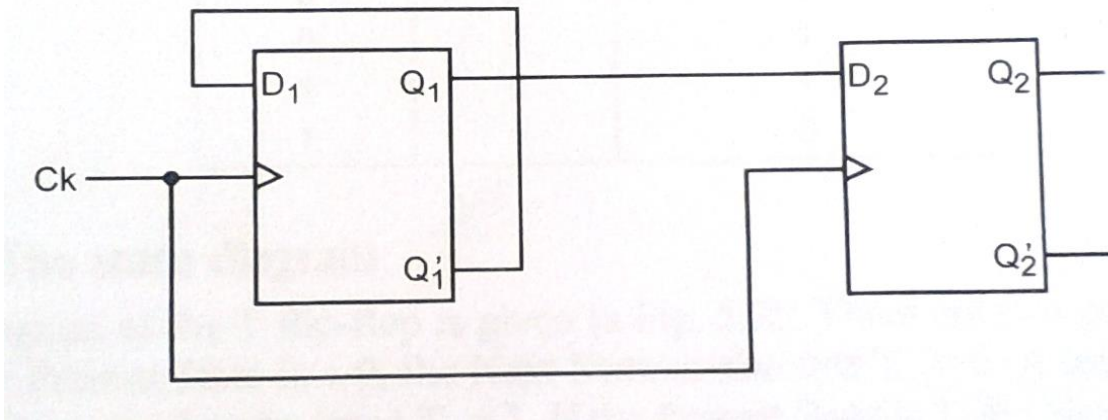

**Figure Q1**

e. Tyrone Shoelaces has invested a huge amount of money into the stock market and doesn't trust just anyone to give him buying and selling information. Before he will buy a certain stock, he must get input from three sources. His first source is Pain Webster, a famous stock broker. His second source is Meg A. Cash, a self-made millionaire in the stock market, and his third source is Madame LaZora, a world-famous psychic. After several months of receiving advice from all three, he has come to the following conclusions:

- i. Buy if Pain and Meg both say yes and the psychic says no.
- ii. Buy if the psychic says yes.
- iii. Don't buy otherwise.

Construct a truth table and find the minimized Boolean function to implement the logic telling Tyrone when to buy. Implement the minimized Boolean function.

(6 marks)

**Question TWO**

- a. Prove that  $B \oplus (B \oplus A.C) = AC$  (5 marks)
- b. Use a Karnaugh Map to simplify the following Boolean expression:

$$F(w, x, y, z) = \sum m(1,5,6,9,13)$$

that has the don't care conditions


$$d(w, x, y, z) = \sum m(4,7,12) \quad (5 \text{ marks})$$

- c. Show the states of a 4-bit SISO register for data input 1101 using a block diagram, waveforms and transition table. Assume the registers contain ones initially. Use positive-edge triggered D-flip-flops (10 marks)

**Question THREE**


- a. Define the term race around as used in flip-flops. (2 marks)

- b. In the flip-flop circuit of **Figure Q3.1** show that if:
- $P_r = 0$  and  $C_r = 1$ , then  $Q = 1$  (independent of  $S$ ,  $R$ , and  $CK$ )
  - $P_r = 1$  and  $C_r = 0$ , then  $Q = 0$  (independent of  $S$ ,  $R$ , and  $CK$ )
  - $P_r = C_r = 1$ , then it functions as a clocked SR flip-flop
- (10 marks)

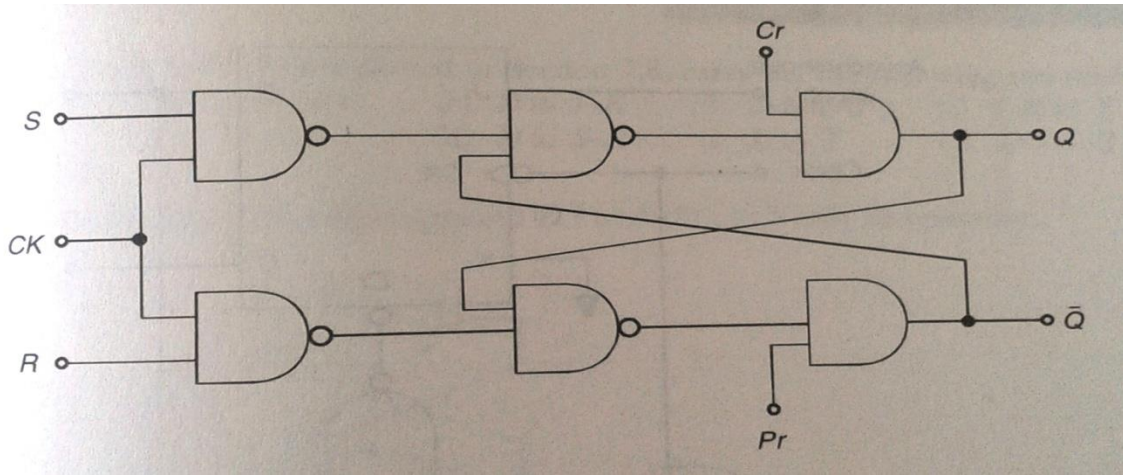

**Figure Q3.1**

- c. **Figure Q3.2** shows a positive edge-triggered D-type flip-flop. Verify its operation. (8 marks)

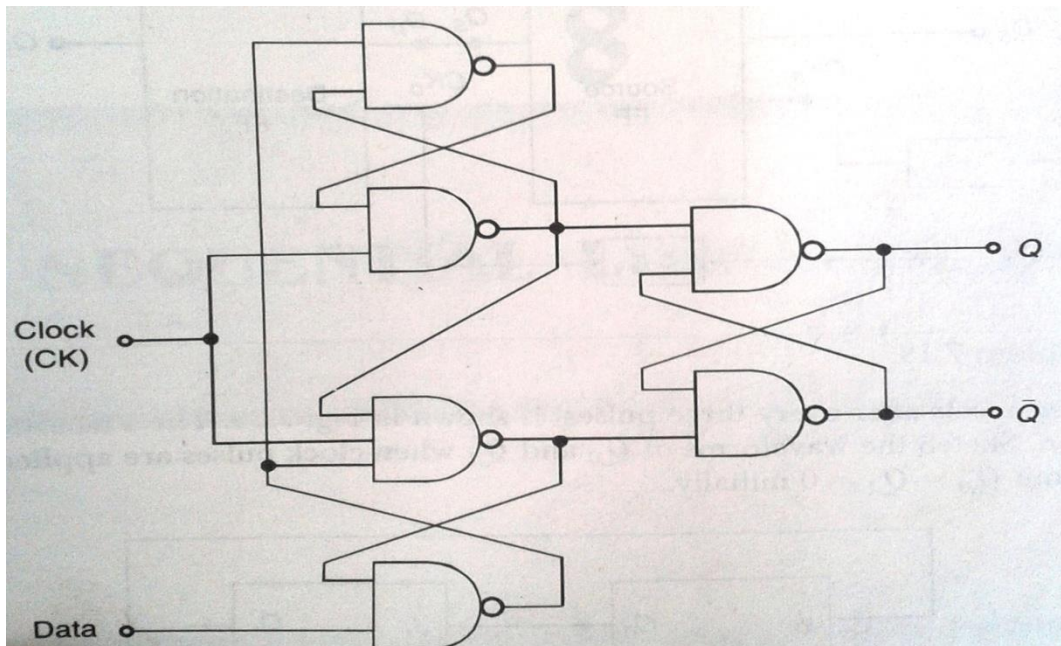

**Figure Q3.2**

**Question FOUR**


- Design a J-K counter that goes through states 2, 4, 5, 7, 2, 4..... (14 marks)
- Differentiate between combinational and sequential logic circuits. (6 marks)

**Question FIVE**

- Perform the following operations:

- i.  $D3F_{16} - 75C_{16}$  (using 2's complement)
  - ii.  $396_{10} + 863_{10}$  (using Excess-3 code)
  - iii.  $10101100111_2$  to Gray
- (5 marks)

- b. i. Find the Boolean expression and Truth Table that describes the circuit of **Figure Q5**.
  - ii. Design the circuit in (i) using minimum number of NOR gates
- (15 marks)

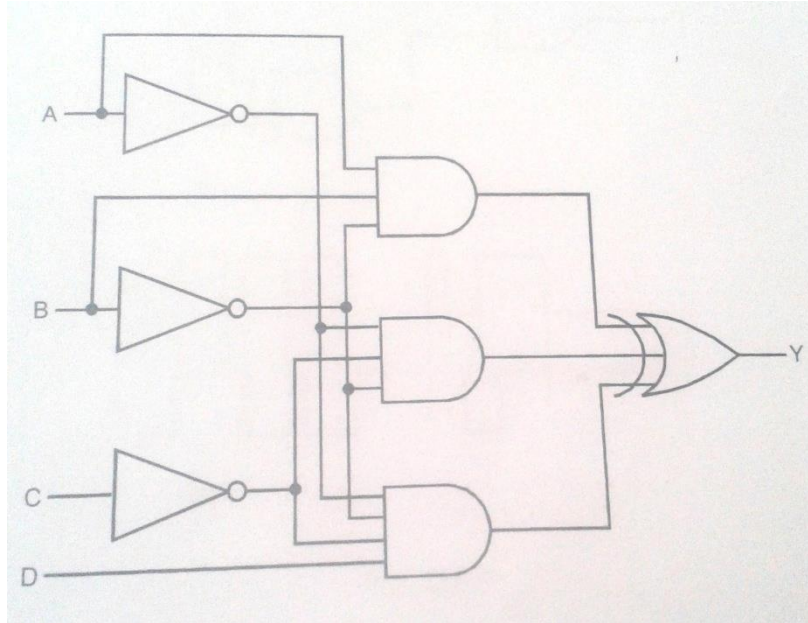

**Figure Q5**