



**TECHNICAL UNIVERSITY OF MOMBASA**

---

**FACULTY OF ENGINEERING AND TECHNOLOGY**

**DEPARTMENT ELECTRICAL AND ELECTRONICS ENGINEERING**

**UNIVERSITY EXAMINATION FOR:**

CERTIFICATE IN TECHNOLOGY

EEP 1101: ENGINEERING SCIENCE 1

**END OF SEMESTER EXAMINATION**

**SERIES: DECEMBER 2016**

**TIME: 2HOURS**

**DATE:**

**Instructions to Candidates**

*You should have the following for this examination*

-Answer Booklet, examination pass and student ID

*This paper consists of five questions. Answer **ANY THREE QUESTIONS**.*

***Do not write on the question paper.***

### QUESTION ONE

- a) i. Explain the term ‘polarization’ as applied to batteries (3 marks)
- ii. A battery is made up of four individual cells of which has an open circuit terminal voltage of 2V and an internal resistance of  $0.1 \Omega$ , calculate;
- I) Terminal voltage of the battery under no load condition
- II) Current that flows when the battery terminals are short circuited (7 marks)
- b) A battery of e.m.f 48V and internal resistance  $3\Omega$  is charged on a 110 v.d.c supply, using the current method. If the lost of energy is sha. 0.95 per kwh, calculate;
- I) The series resistance required to give a current of 4A
- II) The cost of charge the battery for 18 hours. (10 marks)

### QUESTION TWO

- a) i. Define work
- ii. Calculate the work done in raising a 2kg mass of metal through a height of 20 meters, take  $g = 9.81\text{m/s}^2$  (5 marks)
- b (i) A vehicle which has a mass of 10 kg is moving at a velocity of 60km/h, calculate its kinetic energy.
- ii. Explain the terms vector and scalar quantities (7 marks)
- c) With the aid of a diagram,; Describe briefly the changes in the potential and kinetic energies of the bob of a simple pendulum as it goes from one side of its swing to the other. (8 marks)

### QUESTION THREE

- a) i. Define the following terms as applied in magnetism;
- I) Magnetic motive force
- II) Reluctance
- III) Magnetic flux
- IV) Magnetic flux density
- ii. Draw a diagram of the magnetic field produced by a current flowing in a long straight wire in a plane at right angles to the wire. (9 marks)
- b) i. State a rule that gives the relation between the direction of the current and that of the field
- ii. State four useful machines whose operation depends on the principle of a force in a current carrying conductor. (8 marks)
- c) A flux of  $300\mu\text{webers}$  passing through a 150 turns coil is reversed in 40 ms. Determine the average induced e.m.f (3marks)

**QUESTION FOUR**

- a. (i) State Kirchoff's laws  
 (ii) From the circuit of figure 1 below, calculate;  
 (I) Total resistance  
 (II) Power dissipated by the 10 Ω resistors  
 (III) Potential drop across R5 (12Ω)  
 (IV) Total power

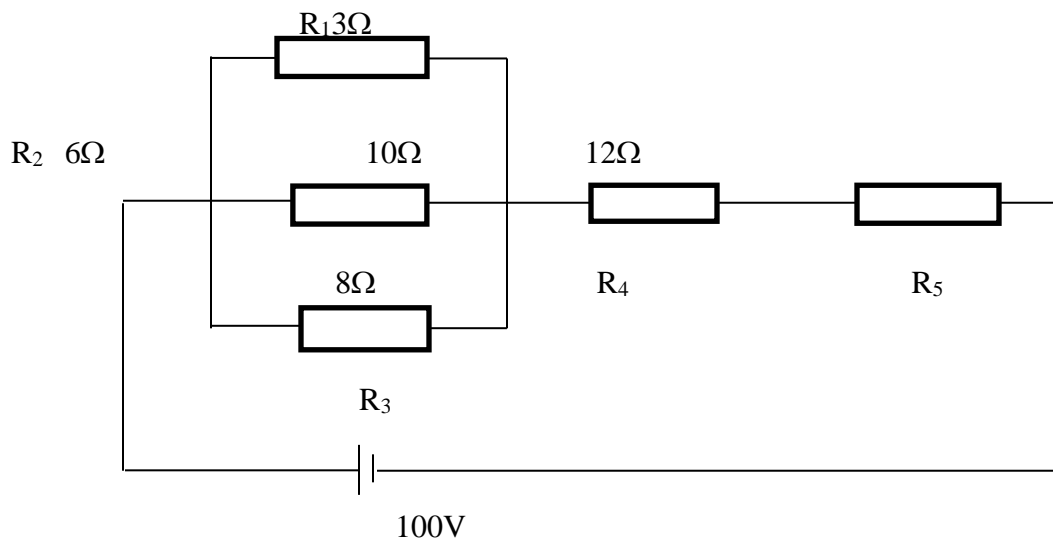


Figure 1

(10 marks)

- b. i) State Ohm's law  
 ii) Define the following electrical quantities and state their units:-  
 (I) Voltage  
 (II) Current  
 (III) Conductance  
 (IV) Conductivity  
 (V) Power

(10 marks)

**QUESTION FIVE**

- a (i) Determine the Thevenin equivalent for the circuit in figure II between terminals 'a' and 'b'  
 (5 marks)

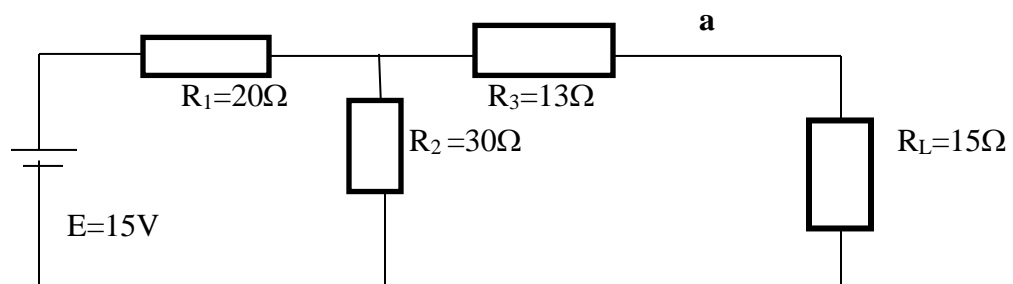


Figure ii

- (ii) Calculate (I) Current (II) Voltage across the  $15\Omega$  load resistor
  - (iii) If  $R_L$  is a variable load resistor, calculate its value to develop maximum power across it. ( 9marks)
- b. Obtain norton's equivalent circuit of figure II above (6 marks)