

TECHNICAL UNIVERSITY OF MOMBASA  
FACULTY OF ENGINEERING AND TECHNOLOGY  
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING  
EEP 2103 CIRCUIT THEORY II  
DEEE2  
SERIES:           MAY 2016

Instructions

- This paper consists of FIVE questions
- Answer any THREE questions
- All Questions carry equal marks

### QUESTION ONE

- (a) Explain the following terms:
- Average value
  - Instantaneous value
  - RMS value
  - Form factor (7 marks)
- (b) A coil of conductor is rotating within a magnetic field. Draw the sine wave and derive the equation of the generated emf. (6 marks)
- (c) (i) Explain the term 'power factor'
- (ii) Draw the phasor diagrams for each of the following circuits:
- Ac circuit having resistance only
  - Ac circuit having inductance only
  - Ac circuit having capacitance only (7 marks)

### QUESTION TWO

- (a) A coil having resistance of  $8\Omega$  and inductance of  $0.18\text{H}$  is connected in series with a capacitor of capacitance  $80\mu\text{F}$  across a  $200\text{V}$ ,  $50\text{Hz}$  supply. Draw the circuit diagram and calculate:
- The current in the circuit
  - Voltages  $V_R$ ,  $V_L$ , and  $V_C$
  - The phase angle and draw the phasor diagram (12 marks)
- (b) With the aid of diagrams explain the functions of the following in analogue instruments
- Control device
  - Eddy current damping device (8 marks)

### QUESTION THREE


- (a) A resistance of  $25\Omega$ , an inductance of  $0.18\text{H}$  and a capacitance of  $40\mu\text{F}$  are connected in parallel across a  $200\text{V}$ ,  $50\text{Hz}$  supply. Calculate:
- The current on each branch
  - The supply current
  - The phase angle and draw the phasor diagram (10 marks)
- (b)(i) Distinguish between admittance and susceptance
- (ii) Explain the condition for resonance (4 marks)
- (c) A resistance of  $20\Omega$ , an inductance of  $0.12\text{H}$  and capacitance of  $50\mu\text{F}$  are connected in series. Calculate the impedance using:
- Rectangular notation
  - Polar notation (6 marks)

QUESTION FOUR

(a) For the circuit of figure Q4a, calculate

- i. Current in each line
- ii. The current in the neutral conductor

(12 marks)

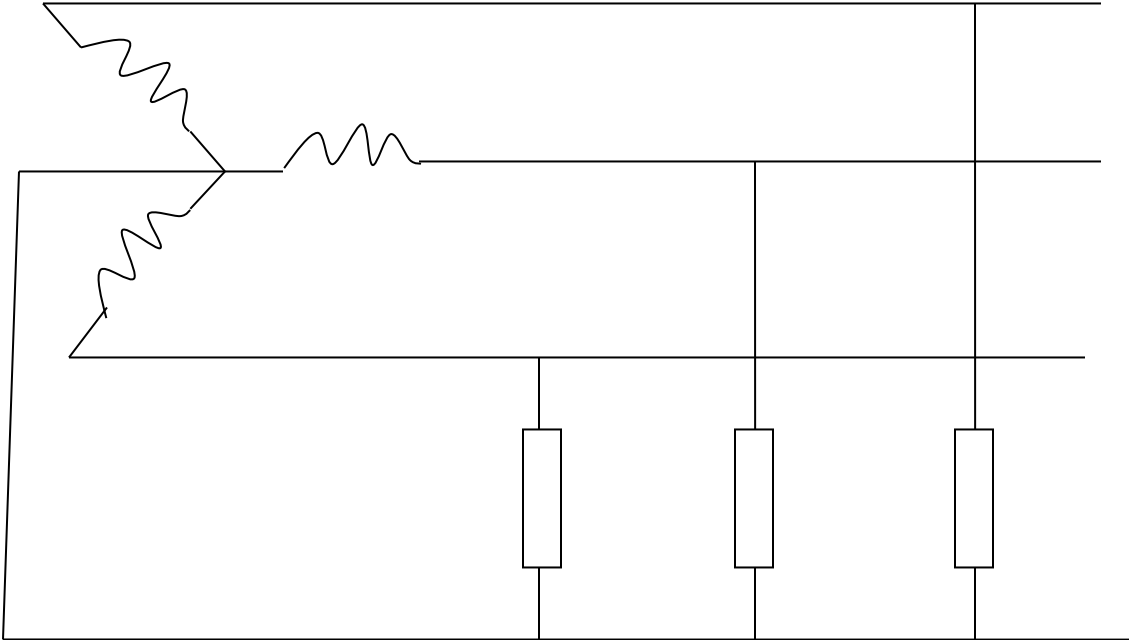

(b) Draw the waveforms for three phase emfs and state expressions for line and phase currents in:

- i. Star- connected supply
- ii. Delta connected supply

(8 marks)

QUESTION FIVE

(a) With the aid of a diagram explain how deflection is achieved in a permanent magnet moving coil instrument. (7 marks)

(b) (i) State the expression for power in a three phase system

(ii) A three phase delta connected motor operating off a 415V system is developing 25kW at an efficiency of 0.9p.u. and a power factor of 0.88. Calculate:

- I. The line current
- II. The phase current

(6 marks)

(c) With the aid of a diagram explain the two-meter method of power measurement in three phase systems. (7 marks)