



TECHNICAL UNIVERSITY OF MOMBASA

FACULTY OF ENGINEERING & TECHNOLOGY

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

UNIVERSITY EXAMINATION FOR:

DIPLOMA IN TECHNOLOGY (ELECTRICAL POWER ENGINEERING) (DEPE5)

EEE 2303 : POWER ELECTRONICS 11

END OF SEMESTER EXAMINATION

SERIES: DECEMBER 2016

TIME: 2 HOURS

DATE: DECEMBER 2016

Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of FIVE questions. Attempt **ANY THREE Questions**

Do not write on the question paper.

Question ONE


(a)(i) Explain the importance of free wheeling diode in controlled rectification

(ii) With the aid of a diagram and waveform explain how the speed of a d.c motor can be varied using a thyristor. **(8marks)**

(b (i) Explain the principles of operation of an inverter by use of basic circuit.

(ii) Explain the operation of figure 1 circuit below:

(12marks)

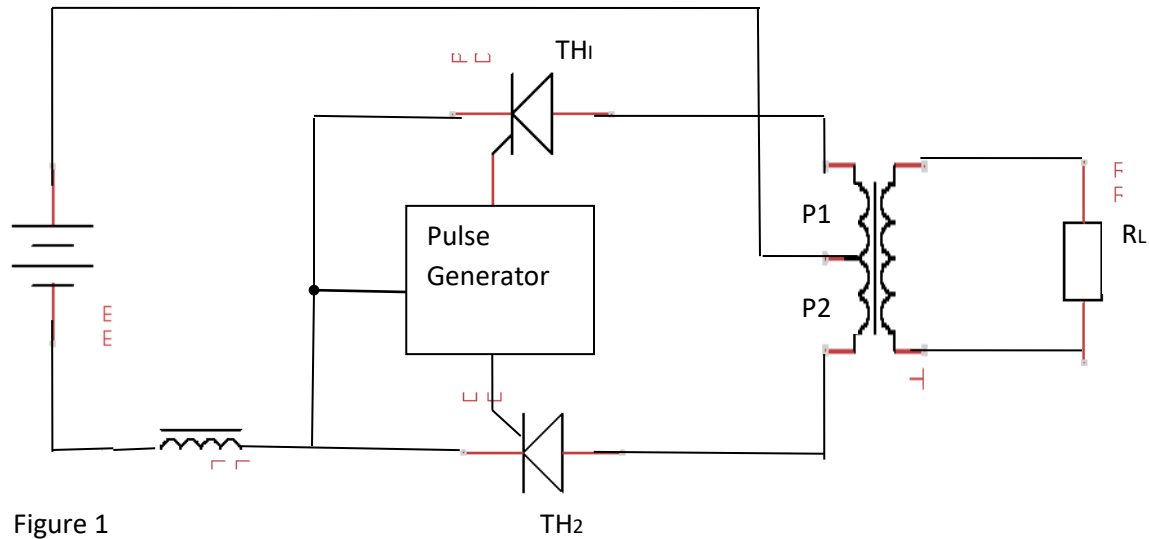

Question TWO

(a)(i) State any TWO advantages of using thyristor for motor speed control.


(ii) Draw a three phase controlled converter circuit diagram and explain the process of regenerative braking of a d.c motor. **(8marks)**

(b)(i) Explain the principle of operation of a basic D.C chopper circuit.

(ii) For the chopper circuit of figure 2 employing parallel-capacitor commutation and operating at 200Hz, determine:-

- I the thyristors T1 and T2 ratings
- II its capacitor value
- III the value of the inductance

(12marks)

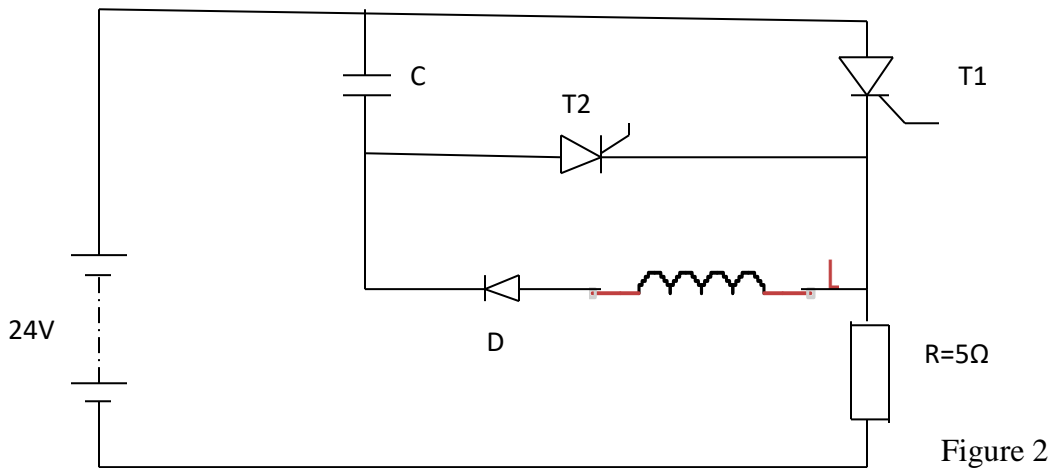

Question THREE

(a)(i) With the aid of a block diagram explain the structure of computer Aided Part Programming(CAPP) software in a manufacturing industry.

(ii) Explain the following types of robots

I Manufacturing robots

II Handling

(10marks)

(b) Explain the following CNC program features

(i) canned cycles


(ii) CNC program macro

c) With the aid of a labelled block diagram explain the operation of a numerically controlled machine.

(10marks)

Question FOUR

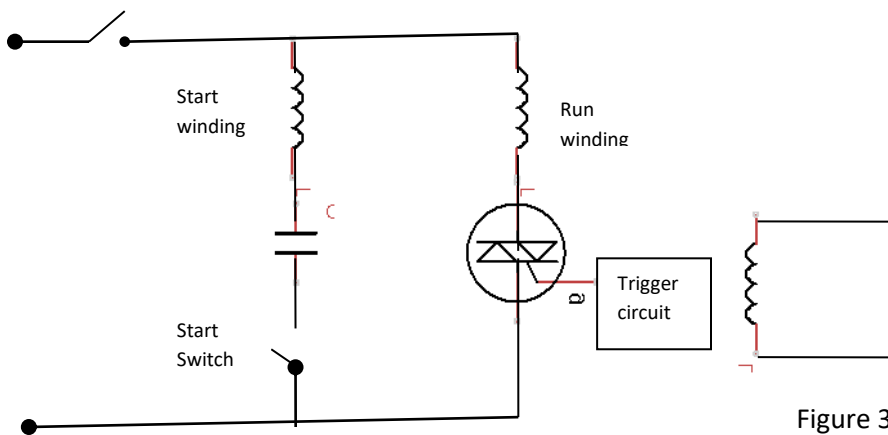(a) (i) Explain the operation of the induction-motor speed control of figure 3 below.



(ii) With the aid of a block diagram explain the operation of a variable d.c speed drive

(9marks)

(b)(i) With the aid of a block diagram explain the speed control of an induction motor or synchronous motor by use of a cycloconverter.

(ii) Explain the major limitation of using a cycloconverter in speed control of motors in (b)(i) above

(7marks)

(c) An inverter supplies a 4-pole cage induction motor rated at 240V, 50Hz. If the motor speed is 900rev/s, Determine the inverter output frequency

(4marks)

Question FIVE

(a)(i) With the aid of a low pass T-filter section derive its characteristic impedance expression

(ii) Deduce the relationship between the impedances of a symmetrical π network and that of an equivalent T-network
(9marks)

(b)(i) (i) Define the term “Insertion loss” for a filter transmission network

(ii) A constant K T-section filter consists of two series elements each of 60mH and a shunt capacitor of 0.1 μ F, Determine:-

I Its cut-off frequency

II Iterative impedance at 2kHz

(11marks)