



TECHNICAL UNIVERSITY OF MOMBASA

FACULTY OF ENGINEERING & TECHNOLOGY

DEPARTMENT OF MECHANICAL & AUTOMOTIVE ENGINEERING

UNIVERSITY EXAMINATION FOR:

DIPLOMA IN MARINE ENGINEERING) (DMAE3)

EMR 2204 : MARINE ELECTRONICS 1

END OF SEMESTER EXAMINATION

SERIES: DECEMBER 2016

TIME: 2 HOURS

DATE: DECEMBER 2016

Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of FIVE questions. Attempt **ANY THREE Questions**

Do not write on the question paper.

Question ONE

(a) Define the following terms:

(i) intrinsic semiconductor

(ii) extrinsic semiconductor (4marks)

(b) With the aid of a diagram, explain the formation of a P-type extrinsic material (5marks)

(c) (i) State any TWO advantages of ICs over discrete circuits

(ii) Define the following terms as used in the manufacture of monolithic integrated circuits:

(I) metallization

(II) wafer

(III) encapsulation

(IV) Diffusion mask (11marks)

Question TWO

(a)(i) State any TWO factors that distinguish a zener diode from a rectifier diode

(ii) Using a schematic diagram and waveforms explain the operation of a full wave bridge rectifier.

(8marks)

(b)(i) Explain the formation of a P-N junction

(ii) Sketch the silicon diode forward and reverse characteristics and explain its shape (8marks)

(c) Explain any TWO applications of LEDs

(4marks)

Question THREE

(a)(i) State any THREE methods of biasing a transistor

b) Distinguish between the following classes of amplifiers illustrating with waveforms:-

i. class A

ii. class B

iii. class C

(12marks)

(c) (i) Give any THREE reasons why the Common Emitter (C-E) connection is preferred over the other configurations

(ii) With the aid of a construction diagram explain the NPN transistor action

(8marks)

Question FOUR

(a)(i) State any THREE advantages of a Transistor as an electronic switch over mechanical switches

(ii) Draw the common emitter output characteristics and explain under which conditions a transistor may be used as a switch rather than an amplifier. (8marks)

(b) With the aid of a two-diode representation of both an NPN and PNP transistor explain how you can determine the serviceability of these transistors by use of an ohmmeter. (8marks)

(c) Calculate the value R_B of figure 1 below (Take $I_B = 7.5\mu A$ and $V_{BE} = 0.6V$)

(4marks)


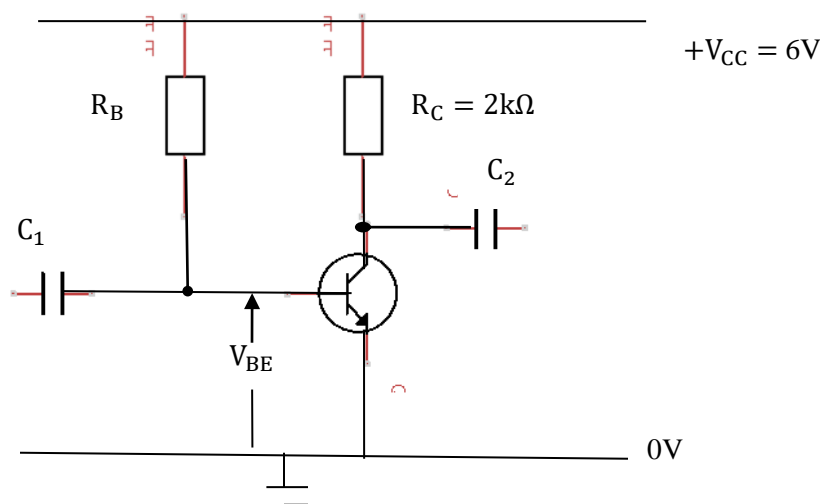


Figure 1

Question FIVE

- (a)(i) Derive the expression of the voltage gain when an OPAMP is connected as a non-inverting amplifier
- (ii) For the circuit of the summing amplifier of figure 3 determine the value of the output voltage

(11marks)

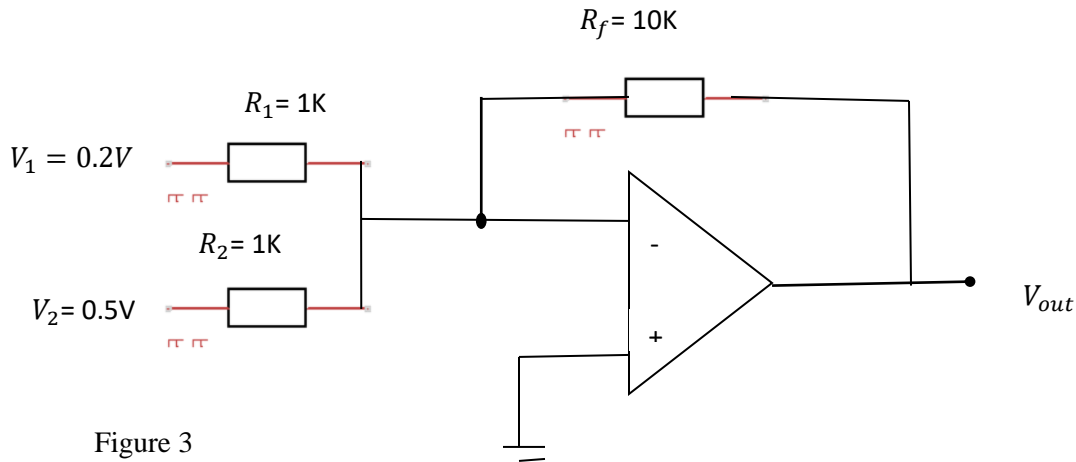

- (b)(i) With the aid of a diagram explain the operation of an OPAMP as an integrator
- (ii) Explain the following parameters as applied to OPAMPS

- I Slew rate
- II Input offset voltage
- III Common mode rejection ratio

(9marks)