



TECHNICAL UNIVERSITY OF MOMBASA

Faculty of Engineering & Technology

DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

SPECIAL/SUPPLEMENTARY UNIVERSITY EXAMINATION 2017/2018

THE DEGREE OF BACHELOR OF SCIENCE IN ELECTRICAL AND ELECTRONIC
ENGINEERING

EEE 2302: ANALOGUE ELECTRONICS III

TIME: 2 HOURS

DATE: SEPTEMBER, 2018 SERIES

INSTRUCTIONS

This paper has five Questions.

Answer any **THREE** Questions.

Question ONE

- (a) Consider an ideal operational amplifier.
- (i) Name **TWO** primary assumptions used in the analysis of its circuits.
 - (ii) Name any **TWO** additional implicit assumptions or characteristics.
(4 marks)
- (b)
- (i) Draw the equivalent circuit of a low frequency operational amplifier circuit as a voltage controlled voltage source.
 - (ii) Using a suitable circuit diagram, derive an expression for the overall gain of the ideal inverting configuration amplifier.
 - (iii) Design an inverting amplifier to have an input resistance of $20\text{k}\Omega$ and a gain of 40dB.
(11½ marks)
- (c) Consider the amplifier given in Fig. Q1(c). The passive components are $R_1 = 3\text{k}\Omega$ and $R_2 = 43\text{k}\Omega$. If the input signal $V_s = +0.1\text{V}$. Calculate:
- (i) Voltage gain, A_v
 - (ii) Output voltage, V_o
 - (iii) Output current, i_o

Assume that the op amp is ideal.

(4½ marks)

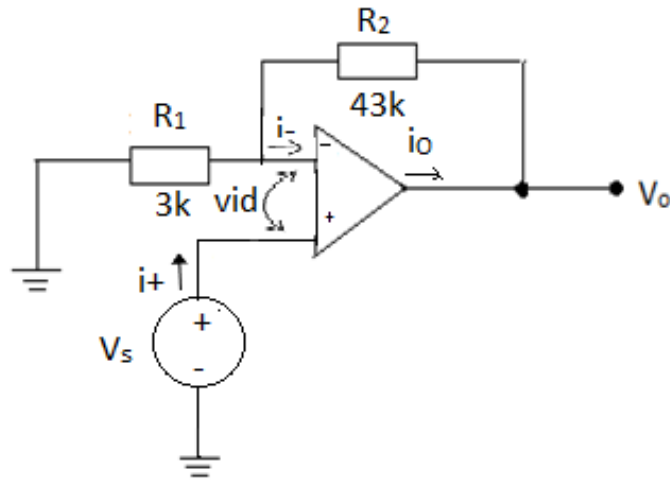


Fig. Q1(c)

Question TWO

(a) State any **TWO** advantages of an instrumentation amplifier over a differential amplifier. **(2 marks)**

(b) An instrumentation amplifier is implemented using the 3-opamp configuration of Fig. Q2(b). The inputs are:

$$V_2 = 2080\text{mV and } V_1 = 2100\text{mV}$$

The passive components are:

$$R_1 = 25\text{k}\Omega, R_x = 50\text{k}\Omega, R_{1A} = R_{2A} = 25\text{k}\Omega, R_{2A} = R_{2B} = 50\text{k}\Omega \text{ and } R_G = 400\Omega$$

Assuming that the opamps are ideal, determine the following:

- (i) The voltage V_{01} and V_{02}
- (ii) The current I_G through R_G
- (iii) The current J_R through R_{2B}
- (iv) The output voltage V_o

(9 marks)

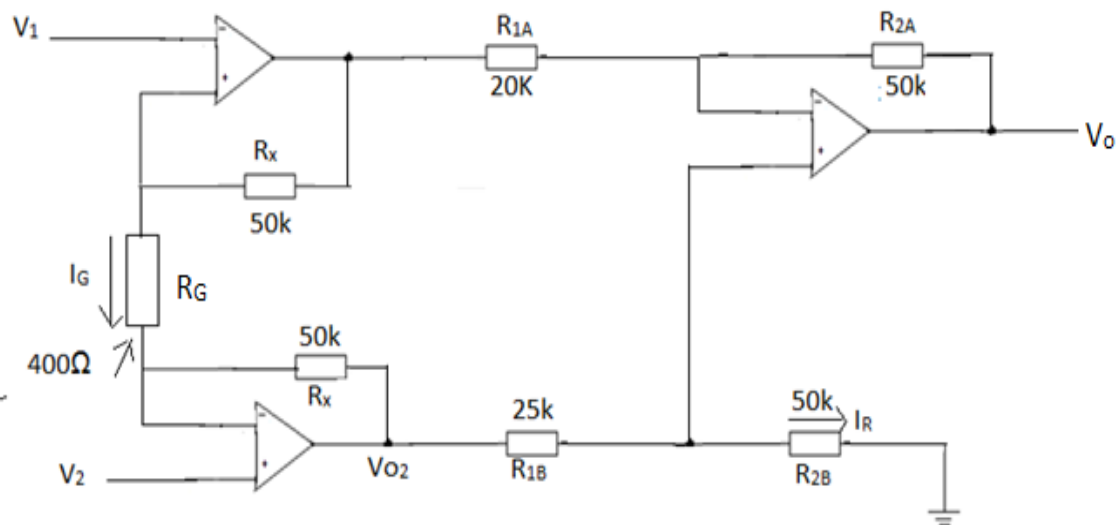


Fig. Q2(b)

(9 marks)

(c) In the circuit given in Fig. Q2(c), the opamp has the following parameters:

$$V_{10} = 4\text{mV}, I_B = 180\text{nA} \text{ and } I_{10} = 40\text{nA}$$

Where V_{10} is the input offset voltage, I_B is the bias current, and I_{10} is the input offset current.

Determine the largest error or “worst case” output voltage V_o due to the input offset effects. The input $V_1 = 20\text{mV}$.

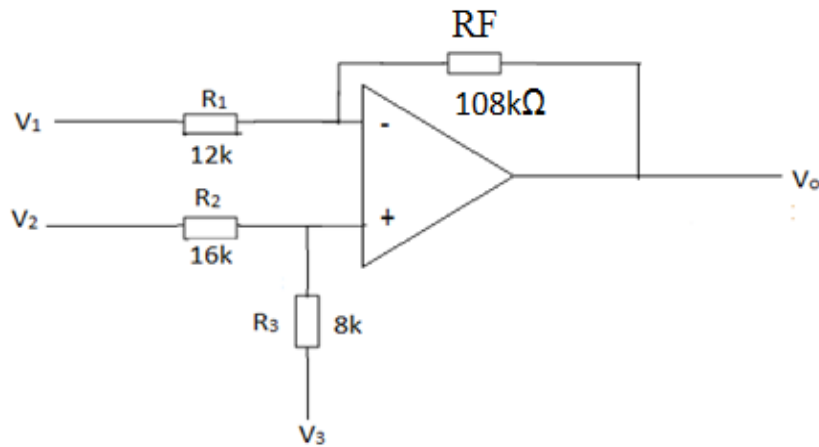


Fig.Q2(c)

Question THREE

- (a)
 - (i) Describe an oscillator.
 - (ii) Discuss briefly the classification of diverse oscillators.
 - (iii) Using a suitable block diagram, derive the condition for oscillation.

(6 marks)

- (b) With the aid of a diagram, briefly describe the principles of operation of mono-stable multivibrator.

(8 marks)

- (c) Consider the Wien bridge oscillator circuit given in Fig. Q3(c).
 - (i) Determine the frequency of oscillation.
 - (ii) Calculate the value of R_1 necessary to maintain oscillation.

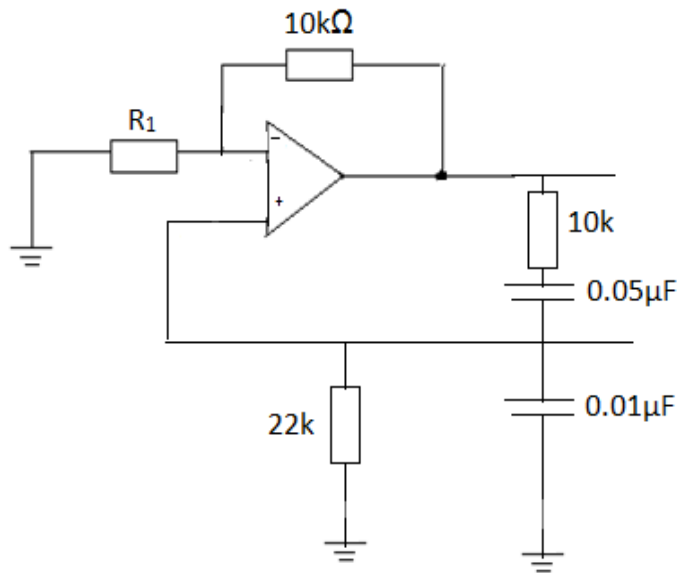


Fig. Q3(c)

(6 marks)

Question FOUR

- (a) (i) With aid of a suitable diagram explain the principles of operation of a precision rectifier.
- (ii) State any **THREE** limitations of a precision rectifier.

(8 marks)

- (b) A differential amplifier with a nominal gain of 10 is illustrated in Fig. Q4(b) tolerances in the resistors result in the actual values shown. Determine:

- (i) The output voltage V_o
- (ii) The common mode gain
- (iii) The Common Mode Rejection Ratio (CMRR)
- (iv) The differential input impedance.

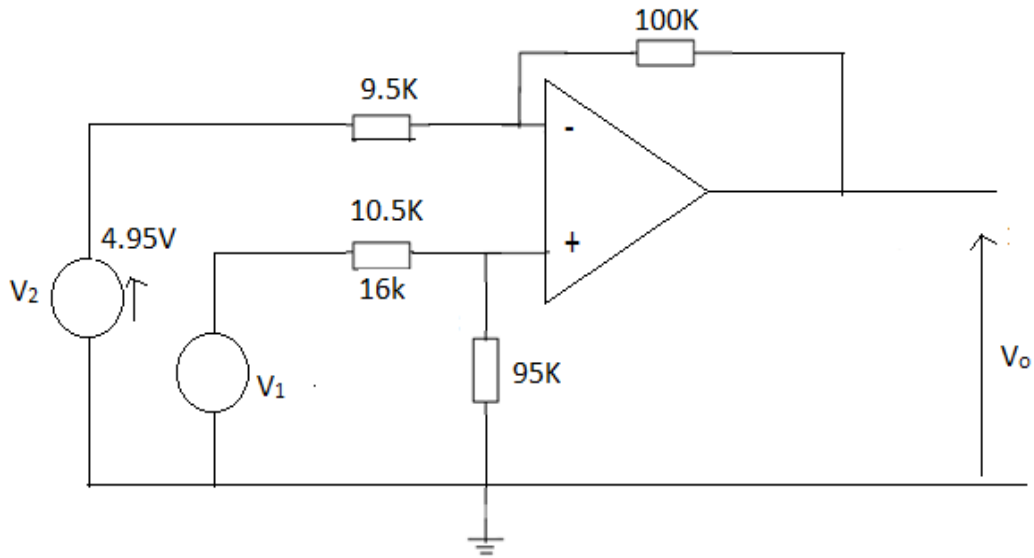


Fig. Q4(b)

(9 marks)

- (c) State the **THREE** sources of unwanted offset voltages in an operational amplifier.

(3 marks)

Question FIVE

- (a) The operational amplifier given in Fig. Q5(a) is ideal. If the input voltages are:

$$V_1 = 60mV, \quad V_2 = 48mV \text{ and } V_3 = (24 \cos \omega t)mV \text{ and the resistances in the circuit are,}$$

$$R_1 = 12k\Omega, \quad R_2 = 16k\Omega, \quad R_3 = 8k\Omega, \quad R_f = 108k\Omega$$

Determine the output voltage V_o .

(8 marks)

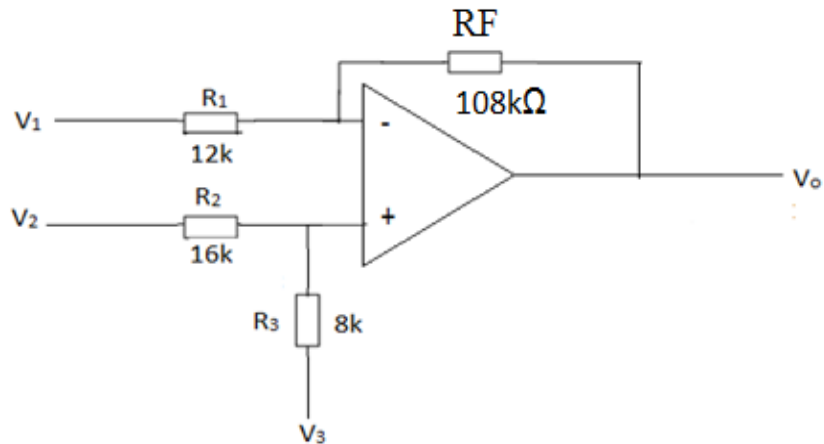


Fig. Q5(a)

(b) Design an amplifier to carry out the following operation:

$$f = 3x + 4y - 5z$$

(7 marks)

(c) Using appropriate diagrams derive an expression for the common-mode rejection ratio for an op-amp.

(5 marks)