



TECHNICAL UNIVERSITY OF MOMBASA

FACULTY OF ENGINEERING AND TECHNOLOGY

ELECTRICAL ENGINEERING DEPARTMENT

UNIVERSITY EXAMINATION FOR:

BACHELOR OF SCIENCE IN ELECTRICAL ENGINEERING

EEE2513: ELECTRICAL MACHINE DRIVES

SPECIAL/SUPPLEMENTARY EXAMINATION

SERIES: SEPTEMBER 2018

TIME: 2 HOURS

DATE: SEPTEMBER 2018

Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of **five** Questions; Question ONE is compulsory. In addition attempt any Other TWO Questions.

Do not write on the question paper.

Question ONE (Compulsory 30 marks)

- a)
- i. Explain the main purpose of an electrical drive
 - ii. Explain the significance of rectification and inversion in electrical drives
 - iii. State any THREE roles of an instrumentation circuit in an electrical drive
- (6 Marks)**
- b) Sketch block diagram showing Field Oriented Control(FOC) technique for electrical drives and explain how it works
- (9 Marks)**
- c)
- i. State TWO advantages and TWO disadvantage of cyclo-converter drives over inverter drives
 - ii. Explain unique applications for DC and AC drives respectively
- (6 Marks)**

- d) Sketch the equivalent circuit of an Induction motor and show that in variable voltage constant frequency drives the torque output is given by:

$$T_0 = [kV]^2$$

Hence

- i. determine the torque output for 15hp, 415V, 730rpm, 50Hz induction motor when the control signal $k=0.25, 0.5$ and when $k=0.65$ and 1 respectively:
- ii. Sketch the Torque speed characteristic above assuming the motor was of NEMA class D

(9 Marks)

Question TWO

- a) Highlight any SIX factors to consider while selecting an electric drive for a certain application
(6 Marks)
- b) Sketch a Current Source Inverter Circuit (VSI) for a 3- ϕ synchronous motor, and explain the function of each section
(6 Marks)
- c) A 150V_{L-n}, 10A, 40Hz, 1- ϕ , 0.85pf motor is fed via a four step inverter circuit from a 3- ϕ , 240 V_{L-n} supply. Assuming modulating index m_a of 0.7, calculate:
 - i. The DC section voltage and current
 - ii. The source side fundamental current and power factor
 - iii. The source side fundamental current and power factor if source is replaced by 415V_L, 3- ϕ supply(8 Marks)

Question THREE

- a) Describe scalar and vector modelling of electrical drives
(4 Marks)
- b)
 - i. List any FOUR parameters considered in a dynamic model for electrical drives
 - ii. State TWO advantages of space phasor models over dynamic models in electrical drives
(6 Marks)
- a) Two phase quadrature currents displaced from fixed reference frame by $\theta=30^\circ$ and each having peak value of 200 A are fed to a three phase machine with balanced supply. Sketch the layout of such a drive system and determine:
 - i. $\alpha\beta$ component output with dqo input
 - ii. abc component output from $\alpha\beta$ block
 - iii. the layout sketch corresponding to drive in b(i) and b(ii) above
(10 Marks)

Question FOUR

- a) State THREE:
 - i. Advantages of DC Chopper drives over DC Silicon Controlled Rectifier (SCR)
 - ii. Problems of SCR drives
(6 Marks)
- b) Sketch block diagram of DC SCR drive system and explain how it functions
(6 Marks)

- c) A 220V, 20A, 500r.p.m. armature current controlled separately excited DC motor having armature resistance of 0.5Ω is to be connected to a 3- ϕ 415V mains through a Δ - Δ step down transformer and a SCR drive. Determine transformer ratio applied and the firing angle required for:
- forward motoring operation at 500rpm
 - forward braking at 300rpm

(8 Marks)

Question FIVE

- a) Using sketches distinguish between unipolar and bi-polar wave drives for stepper motors
(4 Marks)
- b) Estimate the number of pulses and pulse frequency per phase output by a 6-phase wave drive supplying a stepper motor having 12 stator poles and 10 rotor poles, and is required to rotate a 21cm diameter wheel through a distance of 6.6m in 5 seconds.

(6 Marks)

- c) i. Show that the transfer function of a Field Controlled Servo Motor is given by:

$$\frac{\theta_o(s)}{V_F(s)} = \frac{K_F K_m / L_F J_m}{s(s + D_m / J_m)(s + R_f / L_f)}$$

- ii. Determine the steady state angular displacement for the motor in b(i) above when supplied with a 100V 25ms pulse input. The parameters of the machine are:
 $L_f = 100\text{H}$, $R_f = 0.5\text{k}\Omega$, $K_f = 10$, $J_m = 0.01\text{Kgm}^2\text{s}^{-2}$, $D_m = 0.04\text{N/ms}^{-1}$, $K_m = 50$

(10 Marks)