



TECHNICAL UNIVERSITY OF MOMBASA

FACULTY OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF MEDICAL ENGINEERING

UNIVERSITY EXAMINATION FOR:

BACHELOR OF SCIENCE IN MEDICAL ENGINEERING

SECOND YEAR SEMESTER ONE

EEE 4232: CIRCUIT AND NETWORK ANALYSIS

SPECIAL/SUPPLEMENTARY EXAMINATION

SERIES: SEP 2017

TIME: 2 HOURS

DATE: SEP 2018

Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of **FIVE** questions. Question **ONE** is **COMPULSORY**. Attempt any other two questions.

Do not write on the question paper.

Question ONE (COMPULSORY)

a) i) State Thevenin's theorem.

ii) Fig Q1(a) represents a resistive network. Use Thevenin's theorem determine the:

- I. Current I along the 4Ω resistor
- II. The power dissipated on the 4Ω resistor (10mks)

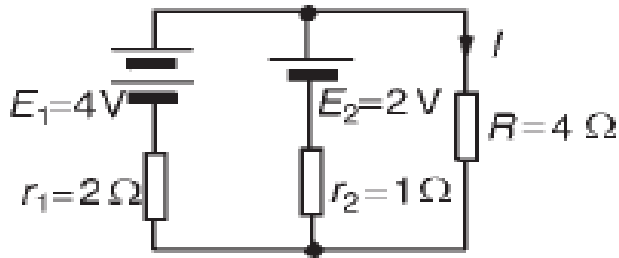


Fig Q1(a).

b) In the network of Fig Q1(b), use nodal analysis theorem to determine the voltage V_{xy} .

(12mks)

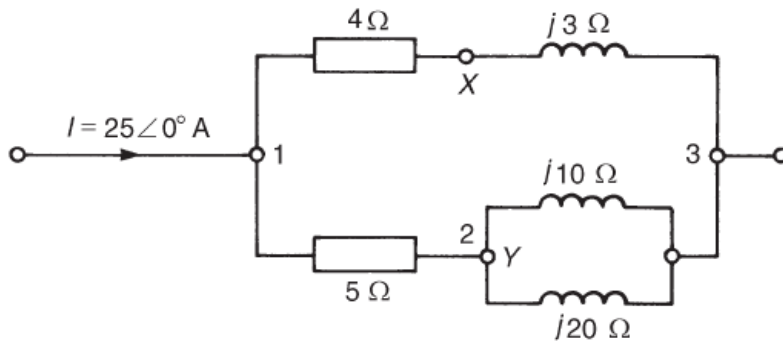


Fig Q1(b)

c) With an aid of waveforms show that the mean value of a symmetrical alternating quantity is given by:

$$V_{mean} = \frac{2 V_{max}}{\pi} \quad (8mks)$$

Question TWO

a) With an aid of a current, voltage and power wave forms show that the mean power in a purely resistive network is given by:

$$\text{Mean power} = \frac{V_{max} I_{max}}{2} \quad (10mks)$$

b) A coil of inductance 159.2mH and resistance 40Ω is connected in parallel with a

30 μ capacitor across a 240V, 50HZ supply. Determine the:

- (i) Current in the coil and its phase angle
- (ii) Current in the capacitor and its phase angle
- (iii) Supply current and its phase angle
- (iv) Circuit impedance

(10mks)

Question THREE

- a) (i) State Kirchoff's current and voltage laws.
- (ii) Determine using Kirchoff's laws each branch current for the network shown in

Fig Q3(a)

(8mks)

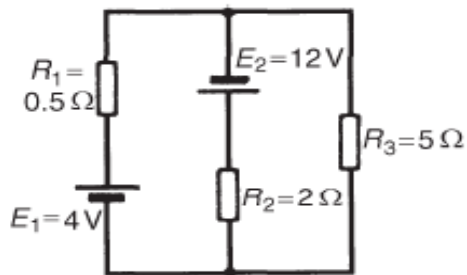


Fig Q3(a)

- b) In the network of Fig Q3(b), use Delta-star transformation to determine:

- (i) The current flowing in the $(0 + j10)\Omega$ impedance
- (ii) The power dissipated on $(20 + j0)\Omega$ impedance

(12mks)

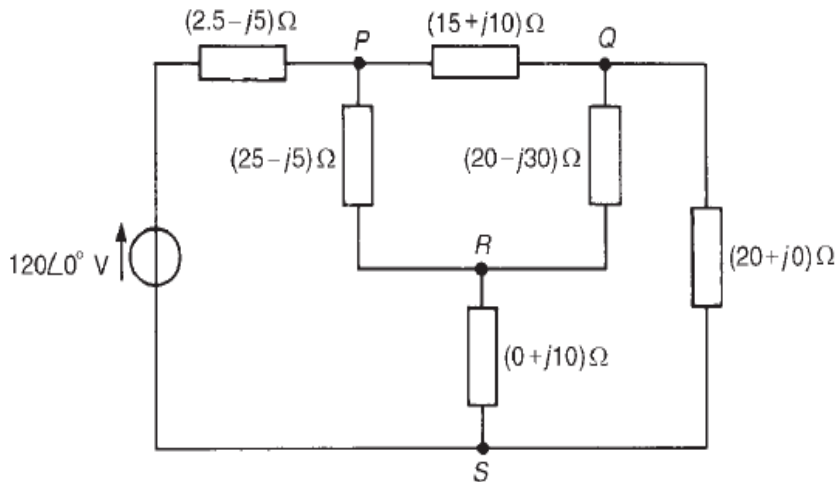


Fig Q3(b)

Question FOUR

a) Design a T-section Band pass filter to pass all frequencies between 300HZ and 1KHZ.

The load impedance is 600Ω . Draw the filter network. (8mks)

b) With an aid of T-section low pass filter network, show that the cut-off frequency

$$f_c = \frac{1}{\pi\sqrt{LC}} \quad (12\text{mks})$$

Question FIVE

a) The current in A.C circuit at any given time t seconds is given by:

$$I = 75 \sin(200\pi t - 0.25) \text{ Amperes. Determine:}$$

- (i) Peak value
- (ii) Mean value
- (iii) Rms value
- (iv) Periodic time
- (v) Frequency and phase angle (10mks)

b) A coil of negligible resistance and inductance of 100mH is connected in series with a capacitance of $2\mu\text{F}$ and a resistance of 10Ω across a 50V variable frequency supply.

Determine the;

- (i) Resonant frequency
- (ii) Current at resonant
- (iii) Voltage across the coil at resonance
- (iv) Q-factor of the circuit (10mks)