



TECHNICAL UNIVERSITY OF MOMBASA

FACULTY OF ENGINEERING AND TECHNOLOGY
DEPARTMENT OF MEDICAL ENGINEERING
UNIVERSITY EXAMINATION FOR:
BACHELOR OF SCIENCE IN MEDICAL ENGINEERING
THIRD YEAR SEMESTER ONE
EEE 4331: ANALOGUE ELECTRONICS III
SPECIAL/SUPPLEMENTARY EXAMINATION

SERIES: SEP 2018

TIME: 2 HOURS

DATE: SEP 2018

Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of **FOUR** questions. **Question ONE is COMPULSORY**. Attempt any other two questions.

Do not write on the question paper.

Question ONE (COMPULSORY)

- a) (i). State the four characteristics of an ideal operational amplifier.
- ii) With a aid of Fig Q1(a) show that if the loop gain ($A\beta$) of a non ideal non inverting amplifier is very large then it's finite open loop gain is given by

$$A_V = 1 + \frac{R_2}{R_1} \quad (14\text{mks})$$

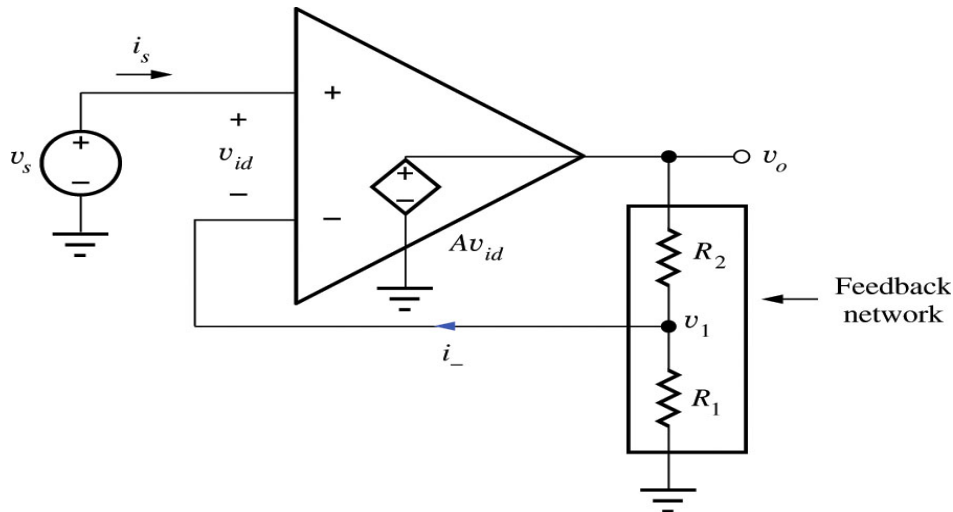


Fig Q1(a)

b) (i) State any three sources of power loss in silicon controlled rectifiers

(ii) The SCR of Fig Q1(b) has a gate trigger voltage $V_T = 0.7V$, gate trigger current

$I_T = 7mA$ and holding current $I_H = 6mA$. Determine the:

- I. output voltage when SCR is off
- II. input voltage that triggers the SCR
- III. minimum anode voltage that can sustain conduction of SCR (11mks)

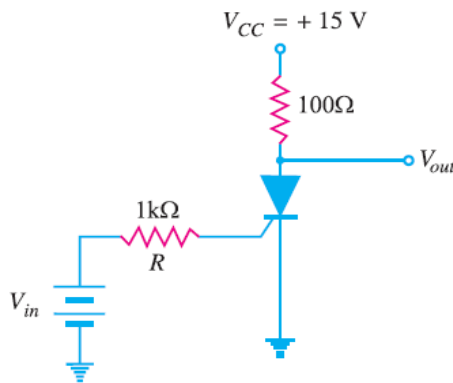


Fig Q1(b)

c) A non inverting amplifier is constructed with $R_1 = 1k\Omega$, $R_f = 39k\Omega$. If the op-amp has an open loop gain of 80dB and internal output resistance $R_o = 50\Omega$. Determine the output resistance of the non inverting amplifier. (5mks)

Question TWO

- a) Design an op-amp circuit that will produce an output voltage equal to $-(3V_1 + 2V_2 + 0.1V_3)$ if its feedback resistance is $100k\Omega$. Draw the amplifier circuit.

(7mks)

- b) (i) A differential amplifier with common mode input of $500mV$ and a difference mode input $30mV$ has an output of $5mV$ due to common mode input and $3V$ due to difference input.

Determine the:

- I. difference mode gain
- II. common mode gain
- III. common mode rejection ratio

- (ii) With an aid of a diagram derive the expression of the output voltage of an instrumentation amplifier.

(13mks)

Question THREE

- a) With an aid of a circuit diagram of a phase shift Oscillator and considering Barkhausen Criterion, show that oscillations are realized if the transfer function of the oscillator

$$T_{(j\omega 0)} = \frac{R_1}{12R} \text{ at the point when } R_1 = 12R \quad (14mks)$$

- b) Draw an equivalent circuit diagram of silicon bilateral switch hence describe its operation.

(6mks)

Question FOUR

- (a) With an aid of a diagram and waveforms show that the mean voltage of a half wave controlled rectifier with resistive load is given by:

$$V_{dc} = \frac{V_{max}}{2\pi} (1 + \cos\theta) \quad (8mks)$$

(b) With an aid of Fig 4Q(b) show that the input resistance of a non ideal inverting amplifier

is given by $R_{in} = R_1 + \frac{R_2}{1+A}$ (12mks)

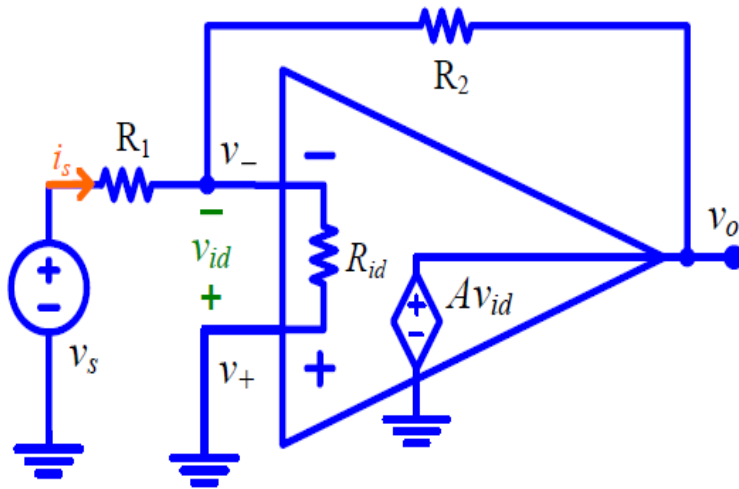


Fig Q4(b)