



# TECHNICAL UNIVERSITY OF MOMBASA

---

FACULTY OF ENGINEERING & TECHNOLOGY

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

## UNIVERSITY EXAMINATION FOR:

DIPLOMA IN TECHNOLOGY (ELECTRICAL & ELECTRONICS ENGINEERING) (DEEE3)

EEE 2202: DIGITAL ELECTRONICS II

## SPECIAL/SUPPLEMENTARY EXAMINATION

**SERIES: SEPTEMBER 2018**

**TIME: 2 HOURS**

**DATE: SEPTEMBER 2018**

### Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of FIVE questions. Attempt ANYTHREE Questions

**Do not write on the question paper.**

---

### Question ONE

(a)(i) Explain the THREE types of triggering signals used in flip flops

(ii) With the aid of block diagrams, describe the FOUR modes of operation of shift registers **(11marks)**

(b)(i) Explain any TWO applications of shift registers

(ii) Explain the term “Multiplexer” in digital circuits.

(iii) With the aid of a diagram explain the operation of a 4-input multiplexer. **(9marks)**

### Question TWO

(a)(i) With the aid of a diagram explain how a shift register can be modified to form a ring counter

(ii) Draw a decade counter and explain its operation **(10marks)**

(b) Figure 1 shows a block diagram of a counter.

(i) Name the type of counter implemented

(ii) Draw the complete timing diagram for eight clock pulses, showing the clock,  $Q_0$ , and  $Q_1$  waveforms

(iii) Determine the count at each clock pulse **(10marks)**

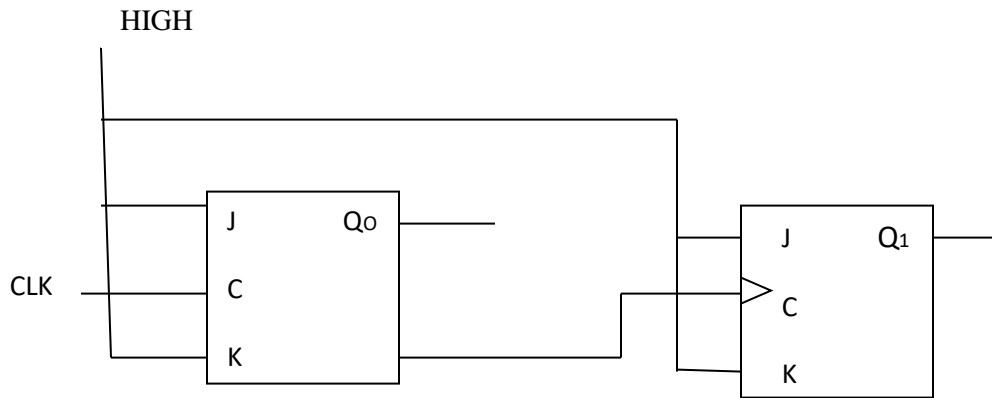


Figure 1

### Question THREE

- (a) Draw the clocked RS flip-flop and by use of state table explain its operation **(8marks)**
- (b) (i) Explain how “RACE AROUND condition occurs in flip flops.  
(ii) Explain how the condition in b(i) above is overcome **(6marks)**
- (c) Draw a simplified block diagram of a digital clock and explain its operation. **(6marks)**

### Question FOUR

- a)(i) List the FOUR main types of flip-flops used in digital circuits.  
(ii) With the aid of a diagram and state table explain the operation of master slave flip-flop. **(11marks)**
- (b) Explain with the aid of a diagram and truth table why the T-type flip-flop was developed. **(5marks)**
- (c) Describe by use of sketches and truth table the basic concept of “bits” storage in digital circuits **(4marks)**

### Question FIVE

- (a) Define the following terms as applied to semiconductor memory:
- (i) EEPROM
- (ii) RAM **(2marks)**
- (b) Draw a Bipolar memory cell and describe its reading and writing process **(8marks)**
- (c)(i) Explain the steps followed in designing a sequential logic circuit.

( ii) Design a relay switching network with FOUR relay coils and associated contacts to provide a closed path through the contacts when at least TWO coils are energized. **(10marks).**