



TECHNICAL UNIVERSITY OF MOMBASA

FACULTY OF ENGINEERING AND TECHNOLOGY
DEPARTMENT OF MEDICAL ENGINEERING

UNIVERSITY EXAMINATION FOR:
DIPLOMA IN MEDICAL ENGINEERING

EEP 2251: ELECTRICAL MACHINES & UTILIZATION II
END OF SEMESTER EXAMINATION

SERIES: AUGUST 2019

TIME: 2 HOURS

DATE: Pick Date Aug 2019

Instructions to Candidates

You should have the following for this examination

-Examination pass and student ID

This paper consists of **FIVE** questions. Attempt any **THREE** questions.

Do not write on the question paper.

QUESTION ONE

- a) Distinguish between **apparent power** and reactive **power**. (2marks)
- b) Describe the 4-wire electricity distribution system. (2marks)
- c) Compare and contrast the **2-wattmeter** and **3-wattmeter** methods of measuring electrical power in 3-phase systems. (3marks)
- d) A balanced load consists of three coils, each of resistance 6Ω and inductive reactance of 8Ω , connected first in star and then in delta across a 400V, 3-phase supply. Calculate
 - i) the line current
 - ii) the power absorbed by the coils (13marks)

QUESTION TWO

- a) Distinguish between **salient-pole rotor** and **squirrel –cage rotor** (2marks)
- b) Compare and contrast induction motor and synchronous motor. (3marks)
- c) Explain how the speed of 3-phase induction motor varies with load. (5marks)
- d) A 3-phase induction motor is wound for 4-poles and is supplied from a 50Hz system.
Calculate.
 - i) the synchronous speed
 - ii) the speed of the motor when slip is 4%
 - iii) the rotor current frequency when the motor runs at 600 r.p.m (10marks)

QUESTION THREE

- a) Explain how the 3-phase synchronous motor is affected by
 - i) loading
 - ii) excitation (10marks)

- b) A 3-phase synchronous motor has 12 poles and operates from a 415V, 50Hz supply.
If it takes a line current of 100A at 0.8 power-factor lead, calculate
 - i) the motor speed
 - ii) the torque developed by the motor, neglecting losses. (10marks)

QUESTION FOUR

- a) With the aid of a labeled diagram, explain the principle of operation of a star- star, 3-phase transformer. (6marks)

- b) A 3-phase, 50Hz transformer has a delta- connected primary and star- connected secondary, the line voltage being 25,000V and 415V, respectively. The secondary has a star- connected balanced load at 0.8 power-factor lagging. The line current on the primary side is 5A.
Calculate
 - i) the current in the primary winding
 - ii) the current in the secondary winding
 - iii) the true power output of the transformer. (14marks)

QUESTION FIVE

A machine, which is driven by an electric motor, has stopped running.

- i) state **FIVE** likely causes for this failure, if the coupling between machine and motor is gear drive.
- ii) Explain the remedial action to be taken to solve this problem. (20marks)