



TECHNICAL UNIVERSITY OF MOMBASA

Faculty of Engineering and Technology

Department of Electrical and Electronic engineering

UNIVERSITY EXAMINATION:

Diploma in Electrical Power Engineering

Electric circuit theory I

EEP 2102

SPECIAL/SUPPLEMENTARY EXAMINATION

SERIES: SEPTEMBER 2018

TIME: 2 HOURS

Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of **five** Questions;. Attempt any **THREE** Questions.

Do not write on the question paper.

Question ONE

(a) State:

- (i) Three effects of an electric current
- (ii) Four factors affecting the resistance of a conductor

(7 marks)

(b) For the series-parallel arrangement shown below.

Determine

- (i) the supply current,
- (ii) the current flowing through each resistor
- (iii) the p.d. across each resistor.

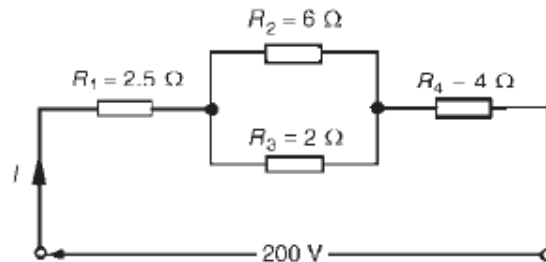


Fig 1

(6 marks)

(c) A coil of copper wire has a resistance of 100 when its temperature is 0°C.

Determine its resistance at 70°C if the temperature coefficient of resistance of copper at 0°C is 0.0043/°C

(7 marks)

Question TWO

(a) By reference to an atom explain

- (i) Flow of current
- (ii) Conductors
- (iii) Insulators

(6 marks)

(b) Explain the following

- (i) Electric cell
- (ii) Polarization
- (iii) Local action

(6marks)

(c) (i) Distinguish between primary and secondary cells

(ii) Four cells, each with an internal resistance of 0.40Ω and an e.m.f. of 2.5V are connected in series to a load of 38.40Ω.

(a) Determine the current flowing in the circuit and the p.d. at the battery terminals.

b) If the cells are connected in parallel instead of in series, determine the current flowing and the p.d. at the battery terminals.

(8 marks)


Question THREE

(a) State:

- (i) Three effects of an electric current
- (ii) Four factors affecting the resistance of a conductor

(7 marks)

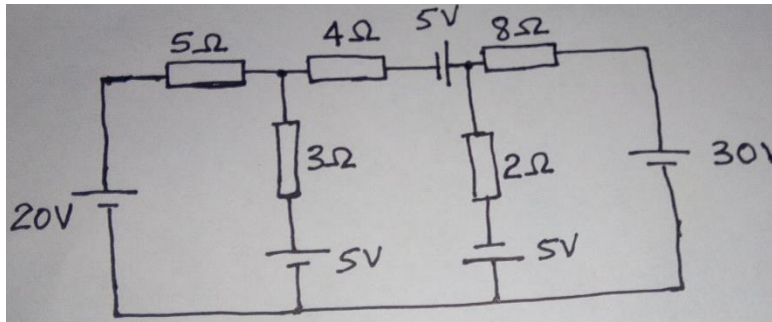(b) Using kirchoffs laws determine the current flowing inn all parts of the circuit



(13 marks)

Question FOUR

(a) State

- (i) Superposition theorem
- (ii) Thevenin's theorem

(5 marks)

(b) Determinet the current in the 3Ω resistor using thevenins theorem in fig 3

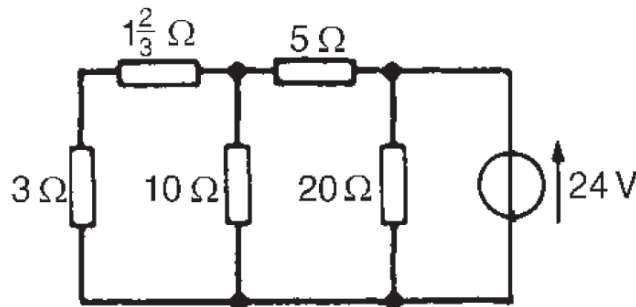


Fig 3

(15 marks)

Question FIVE

- (a) State Norton's theorem (3 marks)
(b) Using Norton's theorem determine the current flowing through the 8Ω resistor of Fig 4


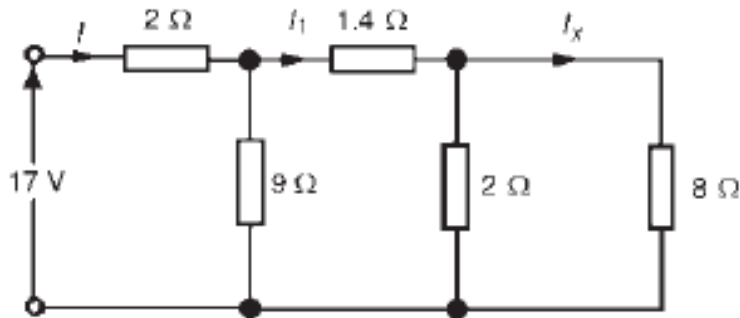


Fig 4

(10

marks)

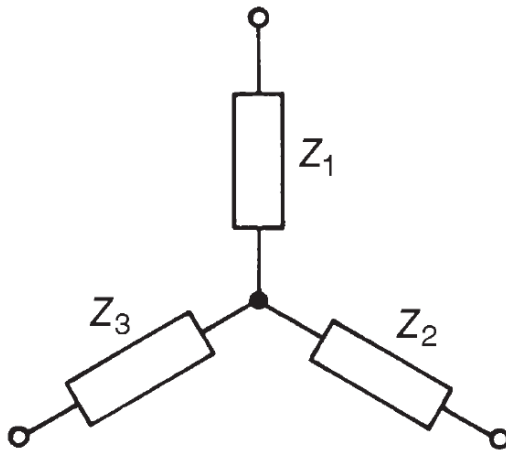- (c) Convert the circuit network below into an equivalent delta given $Z_1 = 0.6\Omega$
 $Z_2 = 1.5\Omega$ $Z_3 = 1\Omega$



(7

marks)