



TECHNICAL UNIVERSITY OF MOMBASA

Faculty of Engineering and Technology
Department of Mechanical & Automotive Engineering
UNIVERSITY EXAMINATION FOR:
BSc. Mechanical Engineering
EMG 2505 : Measurement and Instrumentation
SUPPLEMENTARY EXAMINATION
SERIES: SEPTEMBER 2018
TIME: 2 HOURS

Instruction to Candidates:

You should have the following for this examination

- Answer booklet
- Non-Programmable scientific calculator

This paper consists of FIVE questions. Attempt question ONE and any other TWO questions.

Maximum marks for each part of a question are as shown.

Do not write on the question paper.

Question ONE (Compulsory)

- a. An instrumentation system is usually an assemblage of physical quantities. Using a block diagram identify and explain the main elements of an instrumentation system. (6 marks)
- b. A single strain gauge having resistance of 120 Ohm is mounted on a steel cantilever beam at a distance of 0.15 m from the free end. An unknown force F applied at the free end produces a deflection of 12.7 mm of the free end. The change in gauge resistance is found to be 0.152 Ohm. The beam is 0.25 m long with a width of 20 mm and a depth of 3 mm. The Young's modulus for steel is 200 GN/m². Calculate the gauge factor, G_f . (10 Marks)

Given,

Moment of inertia of beam,

$$I = \frac{1}{12} (bd^3)$$

Deflection of a cantilever beam,

$$F = \frac{3EIx}{l^3}$$

- c. Consider a resistance Wheatstone bridge circuit made up of four resistors as shown in Figure Q1. If two resistor values change from balance condition to the following values $(R_1 + \Delta R_1)$ and $(R_2 + \Delta R_2)$. Determine the expression for the output voltage v_o in terms of the excitation voltage v_i and resistance values. (4 marks)

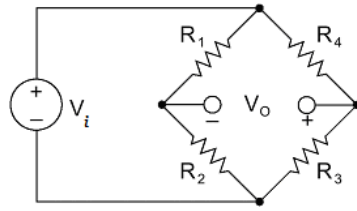


Figure Q1

- d. A single 100 Ohm resistance strain gauge, having a gauge factor of 2 is mounted on a steel bar and is connected into a symmetrical bridge circuit as shown in Figure Q1. When the steel bar is subjected to a tensile force, the output voltage of the unloaded bridge is 5mV. If the recommended operating current of the gauge is 15mA, determine:
- The mathematical expression showing the relationship between the detector current and the strain.
 - The value of the mechanical strain. (6 marks)

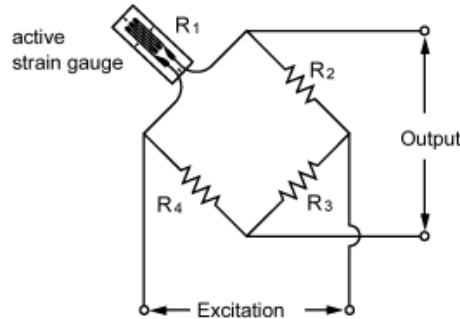


Figure Q1.

- e. Define calibration and explain its importance in a measurement system. (4 marks)

QUESTION TWO

- Briefly explain what a signal conditioning circuit is and state its importance in measurement systems. (6 marks)
- Define the following terms as used in instrumentation amplifiers and identify their causes:
 - Drift
 - Offset voltages (4 marks)
- Derive the expression for the output voltage of the amplifier shown in figure 1.

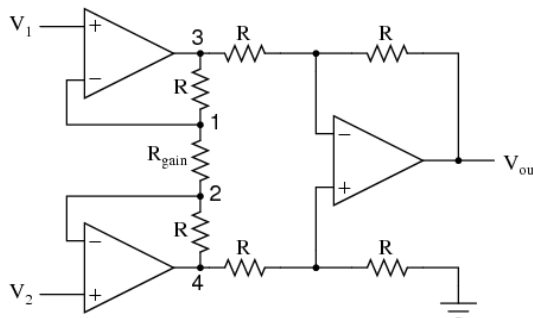


Figure 1

- (ii) For the amplifier in (i), a common mode input signal of 0.5mV gives a common mode output of 0.05mV . Given that $R = 10\text{M}\Omega$ and R_{gain} is adjusted to 10Ω . A right input from a transducer is $10\mu\text{V}$. Determine:
- The CMRR of the amplifier in dB.
 - The measured signal at the output. (10 marks)

QUESTION THREE

- a. A thermistor of resistance $1\text{ k}\Omega$, temperature co-efficient of resistance $4.5\text{ per cent}/^\circ\text{C}$ and an internal temperature rise of $0.2^\circ\text{C}/\text{mW}$ around 27°C is included in a d.c. bridge with three fixed resistors each of value of $1\text{ k}\Omega$. A d.c. amplifier of high input impedance is connected across the bridge output and an indicating device connected to the amplifier output.
- Calculate the maximum voltage sensitivity of the bridge if the internal temperature rise is not to exceed 0.1°C
 - Calculate the maximum amplifier drift, referred to the input that can be tolerated if the overall system accuracy is to be within $\pm 2^\circ\text{C}$. (12 marks)
- b. With the aid of a diagram explain the principles of operation of a cathode ray oscilloscope. (8 marks)

QUESTION FOUR

- a. With the aid of constructional diagram, explain the principles of operation of the following transducers:
- Resistive transducer (potentiometric type)
 - Linear variable differential transformer (LVDT)
 - Variable capacitance displacement transducer (12 marks)
- b. Consider the Maxwell bridge shown in Figure Q4, let the fixed-value bridge components have the following values: $R_3 = 5\Omega$; $C = 1\text{mF}$. Obtain the following:
- Derive the expression used to find the unknown inductive impedance Z_u (L_u and R_u)
 - The value of the unknown impedance (L_u , R_u) if $R_1 = 159\Omega$ and $R_2 = 10\Omega$ at balance.
 - The Q factor for the unknown impedance at a supply frequency of 50 Hz . (8 marks)

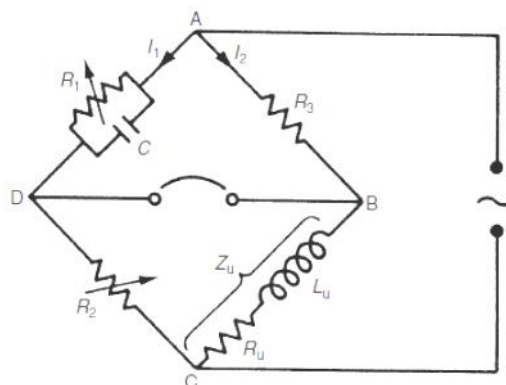


Figure Q4

QUESTION FIVE

- a. Briefly explain what a signal conditioning circuit is and state its importance in measurement systems. (4 marks)
- b. With reference to operational amplifier define the following terms:
- Slew rate
 - Common mode rejection ratio
 - Offset voltage. (6 marks)
- c. Figure Q 5 shows a non-inverting voltage feedback circuit configuration, given $A_o = 100000$, $r_i = 2M\Omega$, $r_o = 75\Omega$, $R_1 = 100\Omega$ and $R_F = 100k\Omega$, determine the:
- Feedback fraction
 - Desensitivity
 - Overall gain
 - Closed loop input impedance
 - Closed loop output impedance. (10 marks)

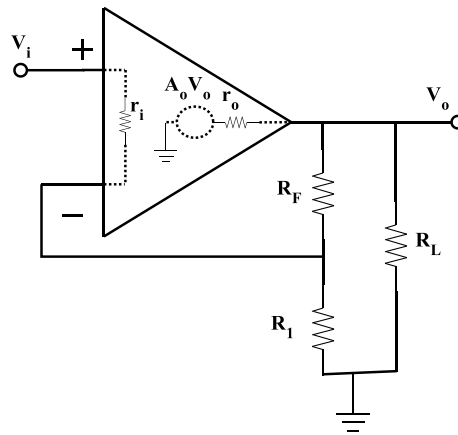


Figure Q 5