



**TECHNICAL UNIVERSITY OF MOMBASA**

*Faculty of Engineering and Technology*

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

**UNIVERSITY EXAMINATION FOR:**

THE DEGREE OF BACHELOR OF TECHNOLOGY IN ELECTRICAL & ELECTRONIC  
ENGINEERING

**TEE 4201: ELECTRICAL CIRCUIT THEORY 1**

SPECIAL/SUPPLEMENTARY EXAMINATION

SERIES: SEPTEMBER 2018

**TIME 2 HOURS**

**DATE: Sep 2018**

**INSTRUCTIONS TO CANDIDATES**

You should have the following for this examination

*-Answer Booklet, examination pass and student ID*

This paper consists of FIVE questions; Question ONE is compulsory. In addition attempt any other TWO questions.

**Do not write on the question paper**

**QUESTION ONE. (Compulsory 30 marks)**

- a. An alternating current is represented by  $i=141.4\sin 377t$ . Determine the:
- Maximum value
  - Frequency
  - Time period
  - Instantaneous value of voltage when  $t=3\text{ms}$  (4marks)
- b. Two currents represented by  $50\sin 314t$  and  $30\sin (314t-\pi/6)$  are fed to a common conductor. Determine the expression for the resultant in the form  $i=I\sin(314t+\phi)$  (4marks)
- c. Express these sinusoids as phasors
- i)  $-7\cos(2t+40^\circ)$  ii)  $i=4\sin(10t+10^\circ)$  (4marks)
- d. Given  $\mathbf{V}=j8e^{-j20}$  and  $\mathbf{I}=-3+j4$ , find the sinusoids represented by these phasors (4marks)
- e. Find the voltage  $v(t)$  in a circuit described by the integro-differential equation

$$2\frac{dv}{dt} + 5v + 10 \int v dt = 20\cos(5t - 30^\circ) \text{ using the phasor method} \quad (5\text{marks})$$

f. Draw ac waveforms showing the phase relations between voltage and current for i) Resistor ii) Inductor iii) Capacitor (3marks)

g. A voltage  $v(t) = 141.4\sin(314t + 10)$  is applied to a circuit and the steady current given by  $i(t) = 14.14\sin(314t - 20)$  is found to flow through it

Determine:

- i. The power factor of the circuit
- ii. The power delivered to the circuit
- iii. Draw the phasor diagram (6marks)

### QUESTION TWO

- a. A voltage is applied to a series R-L circuit. Obtain the phasor representing the voltage across L and explain how the magnitude of this voltage varies with frequency (5marks)
- b. A two element series circuit carries a current  $v(t) = 141.4\sin(314t + 10)$ , exciting voltage being  $v(t) = 141.4\sin(314t + 10)$ . Determine:
  - i. Circuit element values
  - ii. Average and reactive powers
  - iii. Peak value of the instantaneous dissipated power (8marks)
- c. In the circuit of Fig. Q(2) determine the:
  - i. Rms current I
  - ii. Rms voltages  $V_R, V_C, V_E$
  - iii. Capacitance C
  - iv. Draw the the phasor diagram phase angle I and  $V_x, I$  and  $V_E$  between and phase angle (7marks)

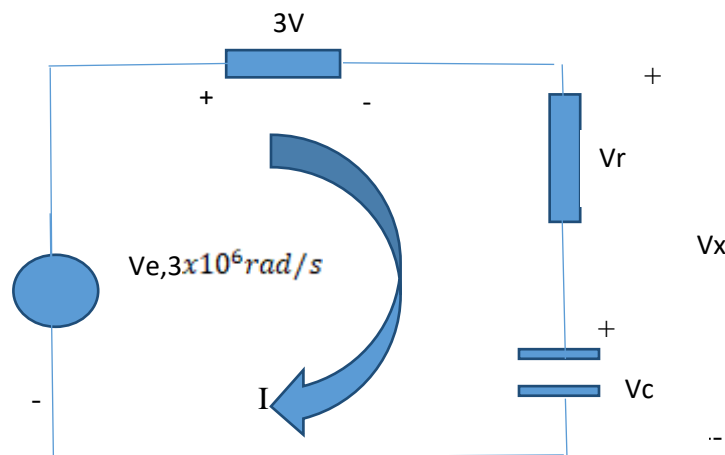


Fig.Q(2)

### QUESTION THREE

- a. Explain with aid of sketches the meaning of the following terms
  - i. Step response
  - ii. Impulse response (4marks)

- b. Consider the circuit of Fig and determine the expression and sketch for  $V_c$  (7marks)
- c. Given that the voltage across a  $5\mu\text{F}$  capacitor is  $V=20 \text{ v}(t)=141.4\sin(314t+10)$ ,.Determine the:
- phasor current
  - Steady state sinusoidal current (4marks)
- d. A coil of inductance of  $0.5\text{H}$  and resistance  $90$  is connected in parallel with a capacitor of value  $20\text{F}$ . The circuit is connected to an a.c. source voltage of  $230\text{V}$ ,  $50\text{Hz}$ . Determine the:
- Current drawn from the source
  - Power factor of the circuit (5marks)

#### QUESTION FOUR

- I.State Nortons theorem as applied to any ac two terminal active linear network
- . Determine the current which will flow through an impedance of  $(10 - j20)$  across terminals A and B of the circuit shown fig(4a).


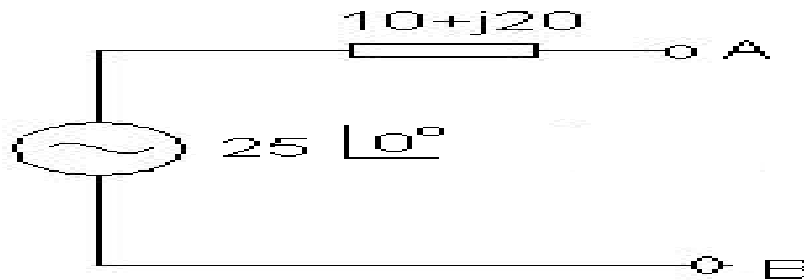


Fig Q(4a)

(8marks)

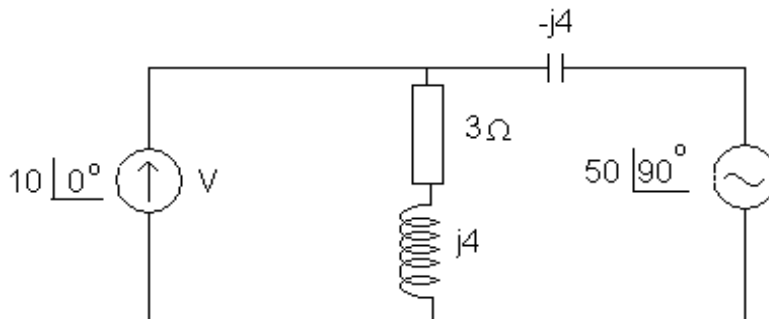- Use superposition theorem to determine the voltage  $V$  in the network shown fig(4b)



Fig(4b)

(5marks)

- In the network shown Fig 4(c) find the current through the load  $Z_L$  using Thevenin's theorem

$$Z_1 = (8 + j8)\Omega; \quad Z_2 = (8 - j8); \quad Z_3 = (2 + j20); \quad Z_L = -j10$$

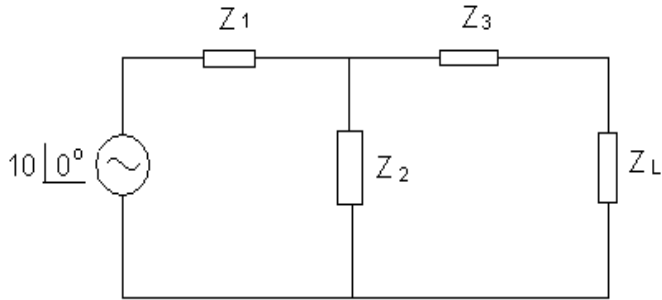


Fig.(4c)

(5marks)

d) State the condition of duality of a circuit and give TWO examples dual quantities

(2marks)

**QUESTION FIVE.**

a (i) With the aid of a diagram and waveforms describe how three phase supply a.c. voltages are generated

(ii) Describe two possible connections of three phase circuits and draw the phasor for each case (7marks)

b. A balanced star connected load is supplied from a symmetrical three phase 400V system. The current in each phase is 30A and lags 30 behind the phase voltage. Determine the:

- i. Phase voltages
- ii. Total voltage
- iii. Draw the phasor diagram showing current and voltages (6marks)

c. Each phase of a star connected load consists of a resistance of  $100\ \Omega$  in parallel with a capacitance of  $31\ \mu\text{F}$ . Determine:

- i. Line current
- ii. Power absorbed
- iii. Total KVA
- iv. Power factor of the load when the load is connected to 415, 4wire, 50Hz supply (7marks)