



# TECHNICAL UNIVERSITY OF MOMBASA

---

FACULTY OF ENGINEERING & TECHNOLOGY

DEPARTMENT OF MEDICAL ENGINEERING

## UNIVERSITY EXAMINATION 2017/2018

BACHELOR OF TECHNOLOGY IN MEDICAL ENGINEERING

TEE 4231: ANALOGUE ELECTRONICS I (PAPER 2)

SPECIAL/SUPPLEMENTARY EXAMINATION

**SERIES:** SEPTEMBER 2018

**TIME:** 2 HOURS

**DATE:** SEPTEMBER 2018

### Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of FIVE questions. Attempt **Question ONE (Compulsory)** and any other **TWO Questions**

**Do not write on the question paper.**

---

### **QUESTION 1 (compulsory-30 marks)**

- (a) Describe the THREE major differences between BJT and FET amplifiers. **(6 marks)**
- (b) Describe the characteristics and application of a zener diode. **(6 marks)**
- (c) Describe with the help of suitable diagram and waveforms, the operation of a half-wave rectifier hence derive the expression for its average d.c voltage. **(10 marks)**
- (d) A half-wave rectifier connected to transformer produces d.c voltage of 9 V. Determine the secondary voltage of the transformer. *(Take  $V_d$  for the diode = 0.7 V)* **(8 marks)**

### **QUESTION 2**

- (a) Describe and sketch the following bipolar junction transistor characteristics
- Input characteristics
  - Output characteristics

**(6 marks)**


(b) Briefly describe the properties of the following components and in each case draw its symbol and state its main application in electronics circuits.

- i. Varactor diode
- ii. Light emitting diode
- iii. Photo diode

(6 marks)

(c) Determine the d.c collector-emitter voltage  $V_{CE}$  for the circuit of **Fig. Q2** given that:

$$R_B = 240 \text{ k}\Omega, R_C = 2.2 \text{ k}\Omega, \beta = 50, V_{CC} = 12 \text{ V. (Take } V_{BE} = 0.7\text{V).}$$

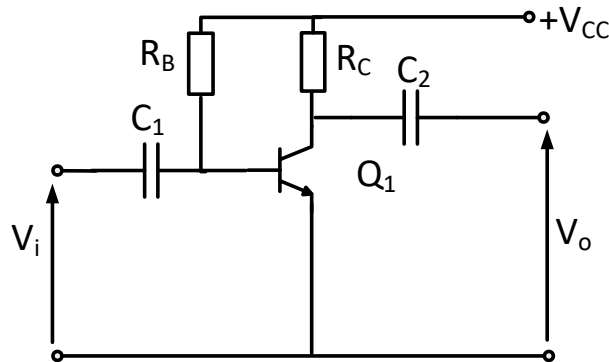

**Fig. Q2**

(8 marks)


### QUESTION 3

(a) Describe using suitable circuit and waveforms the filtering process in a half-wave rectifier. (6 marks)

(b) Describe the advantages of bridge rectifier over full-wave centre rectifier. (6 marks)

(c) Determine in Fig Q3 the current through  $R_1$ ,  $D_1$  and  $R_L$  given that  $V_i = 12 \text{ V}$ ,  $R_L = 2 \text{ k}\Omega$ ,

$R_1 = 0.5 \text{ k}\Omega$  and the diode's zener breakdown voltage  $V_Z = 9\text{V}$ .

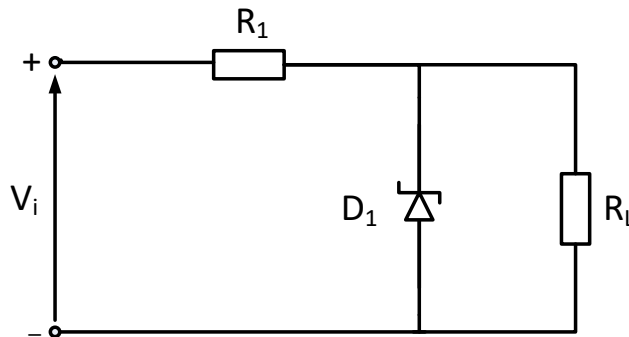


**Fig. Q3**

(8 marks)

**QUESTION 4**

(a) State the type of feedback represented in Fig Q.4. Give reasons for your answer.

**(6 marks)**

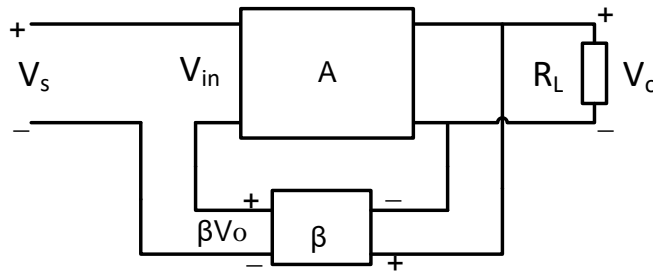

**Fig. Q4.**

(b) Explain the effect of the feedback in (a) on the amplifier's voltage gain, input impedance and output impedance.

**(8 marks)**

(c) Calculate the output signal voltage  $V_o$  if the signal voltage  $V_s = 100 \text{ mV}$  and open-loop voltage gain  $A = -100$  and feedback factor  $\beta = 25\%$ .

**(6 marks)**

**QUESTION 5**

(a) Describe using suitable block diagram the principle of operation of MOSFET.

**(6 marks)**


(b) State the FOUR major requirements of a small signal amplifier.

**(4 marks)**

(c) Draw the a.c equivalent circuit for FET amplifier of **Fig.Q5**. Determine its a.c voltage gain given that:  $I_{DSS} = 12 \text{ mA}$ ,  $V_P = -6\text{V}$ ,  $R_G = 10 \text{ M}\Omega$ ,  $R_D = 4 \text{ k}\Omega$  and the operating point is defined by  $V_{GS} = -2\text{V}$

**NB:** mutual conductance  $g_m$  is given by:  $g_m = g_{m0} \left( 1 - \frac{V_{GS}}{V_P} \right)$  where  $g_{m0} = \frac{2I_{DSS}}{|V_P|}$

**(10 marks)**

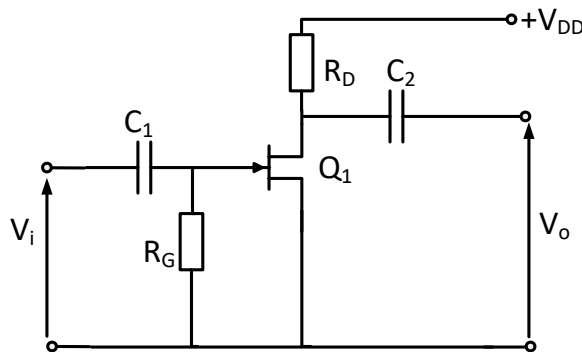

**Fig. Q5.**