



TECHNICAL UNIVERSITY OF MOMBASA

SCHOOL OF ENGINEERING AND TECHNOLOGY
ELECTRICAL AND ELECTRONICS ENGINEERING DEPARTMENT

UNIVERSITY EXAMINATION FOR:

CERTIFICATE IN ELECTRICAL ENGINEERING

EEE1101: ANALOGUE ELECTRONICS .

END OF SEMESTER EXAMINATION

SERIES: APRIL 2025

TIME: 2 HOURS

DATE: Pick Date Select Month Pick Year

Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of FIVE questions. Attempt ANY THREE.

Do not write on the question paper.

Question ONE

- a) Explain with diagrams the term thermionic emission (3marks)
- b) Define the following with respect to semiconductors.
- i. Ionization potential
 - ii. Covalent bonding
 - iii. Doping (3marks)
- c) Plot the I-V characteristics of the diode shown in table and fig.1 (7marks)

Table 1.

Forward voltage(v)	0	0.2	0.4	0.6	0.8
Forward Current	0	0	0.02	1	100

(mA)					
------	--	--	--	--	--

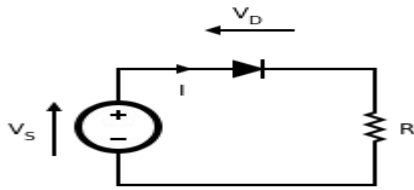


Fig. 1

- ii. From the characteristics determine the value of the load voltage across R if the diode starts conducting fully at forward voltage of 0.6V and R is $2K\Omega$ (4marks)
- iii. Explain why there is no current till almost 0.6V (3mark)

Question TWO

- a) Explain why silicon material is preferred in semiconductors. (2marks)
- b) Using appropriate diagrams describe the formation of N and P semiconductor materials (8marks)
- c) Describe the effect of connecting an external source to a P-N junction.(illustrate with diagrams. (6marks)
- d) State any two applications of the LED and varactor diodes (4marks)

Question THREE

- a. Draw a well labelled block diagram of a regulated DC power supply (4marks)
- b. Draw a circuit diagram of a single phase full wave bridge rectifier and explain its operation. (6marks)
- c. Sketch the input and output voltage waveform of the rectifier circuit in c above (4marks)
- d. List one advantages and two application of power diodes (3marks)
- e. Explain the importance of incorporating a Zener diode in a rectified power supply (3marks)

Question FOUR

- a) i. With the aid of sketches explain the operation of any three classes of amplifiers (9marks)
- ii. Using first principles, show that $\beta = \frac{\alpha}{1-\alpha}$ (4 marks)

- b) i. With the aid of the appropriate diagrams describe the construction and operation of a J FET
- (ii) Compare and contrast between FET and BJT (7marks)

Question FIVE

- a) With the aid of sketches explain the four regions of the Bipolar Junction Transistor. (6marks)
- b) Describe how the biasing and stabilization is achieved in the collector bias network. (6marks)
- c) For the circuit in Figure 1. $V_{CC} = 15V$, $\beta = 100$ and $V_{BE} = 0.7V$ determine the value of
- The base supply voltage (V_{BB})
 - The bias resistor (R_B)
 - The emitter current (I_E)
 - State the function of R_E mentioning any modification that can be introduced to improve on the stability of the circuit. (8marks)

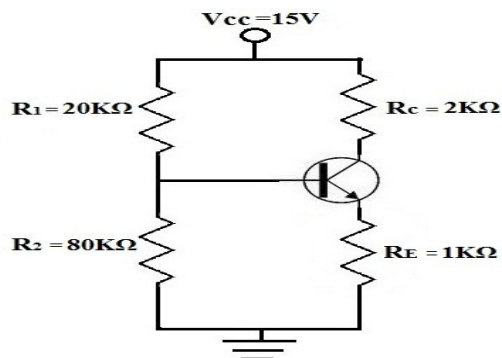


Fig. 1