



TECHNICAL UNIVERSITY OF MOMBASA

TECHNICAL UNIVERSITY OF MOMBASA

School of Engineering and Technology

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

UNIVERSITY EXAMINATION FOR:

THE DEGREE OF BACHELOR OF TECHNOLOGY IN ELECTRICAL & ELECTRONIC
ENGINEERING.

TEE 4210: CIRCUIT AND NETWORK THEORY II

END OF SEMESTER EXAMINATIONS

SERIES: AUGUST 2024

TIME: 2 HOURS

DATE: AUGUST 2024

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of FIVE questions; Question ONE is compulsory. In addition attempt any other TWO questions.

Refer to the last page for selected Laplace transform pairs

Do not write on the question paper

QUESTION 1 [Compulsory 20 marks]

- (a) Describe the major steps in analyzing a circuit using Laplace transform **(8 marks)**
- (b) In the RL circuit in Fig. Q1, the switch is in position 1 long enough to establish steady state conditions, and at $t=0$ it is switched to position 2. By applying Laplace Transform, find the resulting circuit current i . **(12 marks)**

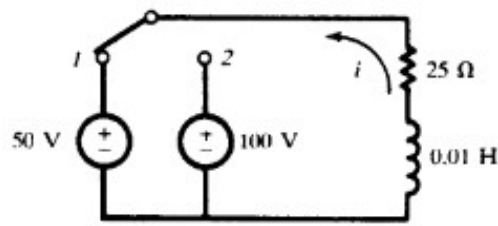


Fig. Q1

QUESTION 2 [20 marks]

(a) Determine the number of octaves and decades between the following pairs of frequencies.

- (i) 10 Hz, 1000 Hz
- (ii) 1700 rad/s, 4200 rad/s

(4 marks)

(b) Draw the asymptotic Bode Magnitude Plot for the transfer function.

$$H(s) = \frac{4(s+2)}{(s+1)(s+4)}$$

(8 marks)

(c) The asymptotic Bode plot of a minimum phase linear system is shown in Fig.Q2

Determine its transfer function.

(8 marks)

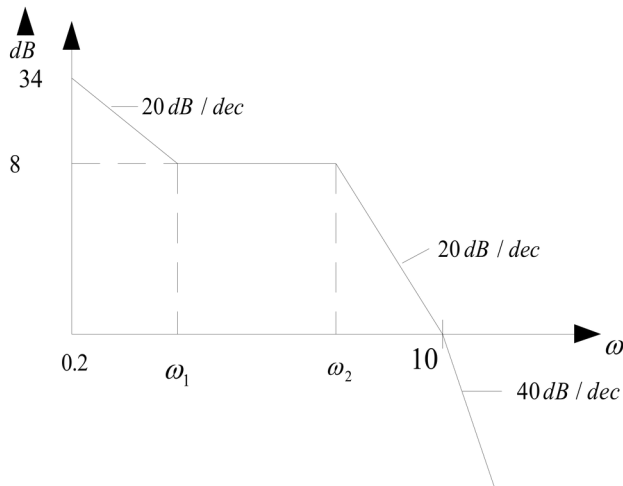


Fig.Q2

QUESTION 3 [20marks]

(a) Define the following terms in reference to analogue filters

- i. Magnitude scaling
- ii. Frequency scaling
- iii. Robustness
- iv. Bode sensitivity

(6 marks)

(b) filter has a transfer function

$$H(s) = \frac{5}{s^2 + ks + 5}$$

Given that the nominal value of k is 2, obtain the poles sensitivity and hence their location after a 10% increase in k

(9 marks)

(b) Determine the frequency ω_{max} that gives maximum $|T(j\omega)|$ for the function.

(5 marks)

QUESTION 4 [20 marks]

For the circuit of Fig. Q4, assuming $v_s(t) = V_m \cos \omega t$

(a) Obtain the voltage gain transfer function $H(j\omega)$.

(4 marks)

(b) Evaluate the magnitude of the transfer function hence sketch the Magnitude plot.

(10 marks)

(c) Evaluate the Phase of the transfer function hence sketch the Phase plot

(6 marks)

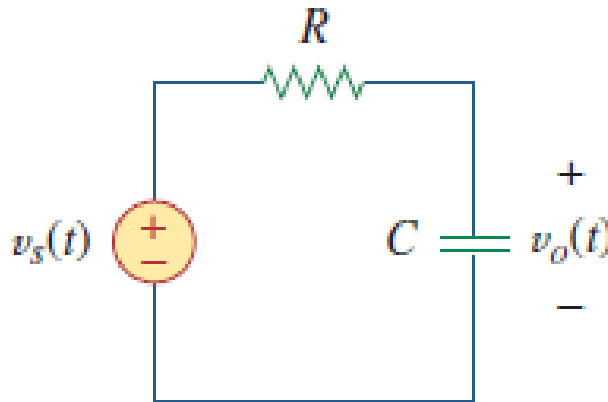


Fig.Q.4

QUESTION 5 [20 marks]

(a) With reference to transfer function, determine the type of filter in Fig. Q5.

$$v_i(t) = V_m \cos \omega t.$$

(8 marks)

(b) Calculate the corner or cut-off frequency given that $R = 2 \Omega$, $L = 2 \text{ H}$, $C = 2 \mu\text{F}$.

(12 marks)

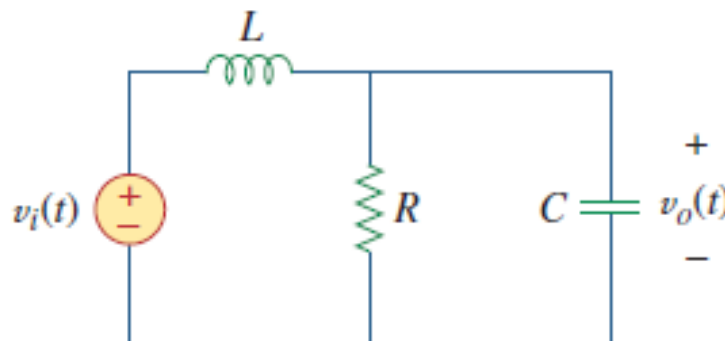


Fig. Q5

	<i>Laplace transform pairs</i>	
1	$f(t)$	$F(s)$
2	1	$\frac{1}{s}$
3	t	$\frac{1}{s^2}$
4	$e^{-\alpha t}$	$\frac{1}{s+a}$
5	$te^{-\alpha t}$	$\frac{1}{(s+a)^2}$
6	$\frac{df}{dt}$	$sF(s) - f(0)$
7	$\int f(t)$	$\frac{F(s)}{s}$
8	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
9	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
10	$\sin (\omega t + \theta)$	$\frac{s \sin \theta + \omega \cos \theta}{s^2 + \omega^2}$
11	$\cos (\omega t + \theta)$	$\frac{s \cos \theta - \omega \sin \theta}{s^2 + \omega^2}$