



TECHNICAL UNIVERSITY OF MOMBASA

School of Engineering and Technology

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

UNIVERSITY EXAMINATION FOR:

THE DEGREE OF BACHELOR OF TECHNOLOGY IN ELECTRICAL & ELECTRONIC ENGINEERING.

TEE 4210: CIRCUIT AND NETWORK THEORY II

END OF SEMESTER EXAMINATIONS

SERIES: MARCH 2025

TIME: 2 HOURS

DATE: MARCH 2025

INSTRUCTIONS TO CANDIDATES

You should have the following for this examination

-Answer Booklet, examination pass and student ID

-Refer to the selected Laplace transform pair at the last page

This paper consists of FIVE questions; attempt any THREE questions.

Do not write on the question paper

QUESTION 1 | 20 marks|

- (a) Find the voltage $v(t)$ in a circuit described by integro-differential equation

$$-50 \cos(5t + 30^\circ) + 2 \frac{dv}{dt} + 5v + 10 \int v dt = 0$$

(10 marks)

- (b) Determine I_1 and I_2 in Fig. Q1 given that $V_1 = 100 \angle 0^\circ \text{ mV}$.



Fig. Q1

(10 marks)

QUESTION 2 [20 marks]

- (a) Describe the major steps in analyzing a circuit using Laplace transform (5 marks)
- (b) In the RC circuit in Fig. Q2, the switch is in position 1 long enough to establish steady state conditions, and at $t=0$. By applying Laplace Transform, find the resulting v_c voltage across the capacitor. (10 marks)

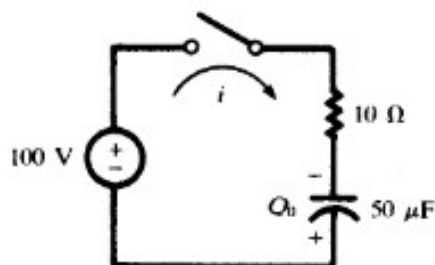


Fig. Q2

- (c) Describe with the help of suitable equations, the state variable model and its general representation. (5 Marks)

QUESTION 3 [20 marks]

For the circuit of Fig. Q3, assuming $v_s(t) = V_m \cos \omega t$

- (a) Obtain the voltage gain transfer function $H(j\omega)$. (4 marks)
- (b) Evaluate the magnitude of the transfer function hence sketch the Magnitude plot. (10 marks)
- (c) Evaluate the Phase of the transfer function hence sketch the Phase plot (6 marks)

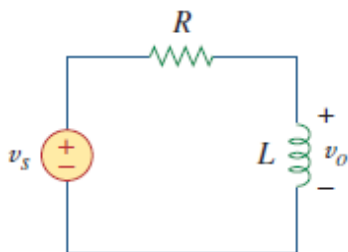


Fig.Q.3

QUESTION 4 [20 marks]

- (a) With reference to transfer function, determine the type of filter in Fig. Q4. $v_i(t) = V_m \cos \omega t$. (8 marks)
- (b) Calculate the corner or cut-off frequency given that $R = 2 \Omega$, $L = 2 \text{ H}$, $C = 2 \mu\text{F}$. (12 marks)

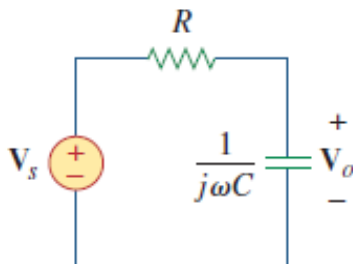



Fig. Q4

QUESTION 5 [20 marks]

(a) Describe the procedures in nodal analysis

(6 marks)(b) For Fig. Q.5, given that $E = 50 \angle 0^\circ \text{ V}$

- i. Find the total impedance Z_T
- ii. Determine the branch currents I_1 , I_2 and I_3
- iii. Determine the power dissipated by each of branch of the circuit.

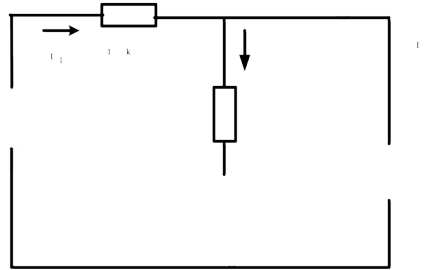**Fig. Q5.**

	<i>Laplace transform pairs</i>	
1	$f(t)$	$F(s)$
2	1	$\frac{1}{s}$
3	t	$\frac{1}{s^2}$
4	e^{-at}	$\frac{1}{s+a}$
5	te^{-at}	$\frac{1}{(s+a)^2}$
6	$\frac{df}{dt}$	$sF(s) - f(0)$
7	$\int f(t)$	$\frac{F(s)}{s}$
8	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
9	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
10	$\sin (\omega t + \theta)$	$\frac{s \sin \theta + \omega \cos \theta}{s^2 + \omega^2}$
11	$\cos (\omega t + \theta)$	$\frac{s \cos \theta - \omega \sin \theta}{s^2 + \omega^2}$