



TECHNICAL UNIVERSITY OF MOMBASA
School of Engineering and Technology
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING
UNIVERSITY EXAMINATION 2024/2025
BACHELOR OF TECHNOLOGY IN ELECTRICAL AND ELECTRONIC
ENGINEERING

TEE 4312:

DIGITAL SYSTEMS DESIGN

TIME: 2 HOURS

SERIES: April, 2025

INSTRUCTIONS TO CANDIDATES

1. You are required to have the following for this examination;
 - Answer Booklet
 - A non Programmable Calculator
2. This paper consists of **FIVE** Questions.
3. Answer **ANY THREE** Questions.

Question ONE

- (a)
 - (i) State the design procedures for a combinational logic circuit.
 - (ii) Using a 4 - to - 1 multiplexer, implement the function
$$f(A, B, C, D) = \sum_m (1, 2, 4, 5, 9, 12, 13, 14)$$
(8 marks)
- (b) Design a logic circuit that has an enable input 'E' such that it converts a 3-bit Binary value to its equivalent Gray code when E = 1 and when E = 0, it converts a 3-bit Gray code to its Binary equivalent. Implement using Encoder and Decoder.**(12 marks)**

Question TWO

- a) Explain the functions of the following digital devices:
 - (i) Binary comparator
 - (ii) Multiplexer
 - (iii) Logic analyser**(6 marks)**
- b) With aid of a transition table, design a modulo-6 J-K flip-flop synchronous counter to repetitively count in the sequence 5, 4, 3, 2, 1, 0, 5 Any illegal state will assume a value represented by 3 after a trigger pulse.**(14 marks)**

Question THREE

- a) Obtain a minimum SOP expression for the function below using the abbreviated binary method of tabular minimization. (10 marks)

$$F(A, B, C, D, E) = \sum_m (3, 4, 7, 9, 11, 12, 15, 16, 18, 19, 20, 23, 24, 26, 27, 28, 31)$$

- b) State the design procedures for a Finite State Machine. (5 marks)
- c) Determine the size of the PROM required for implementing the following logic circuits:
- a binary multiplier that multiplies two four-bit numbers;
 - a dual 8-to-1 multiplexer with common selection inputs;
- (5 marks)

Question FOUR

- a) Develop a full ADDER using NAND gates. (10 marks)
- b) Derive the state table and state diagram of the sequential circuit shown in Figure Q4. (10 marks)

 


Figure Q4

Question FIVE

- a) An electronic thermometer, designed for greenhouse use, has a 5-bit binary output representing a temperature range from 0°C to 31°C. A plug-in logic module is to be designed to output logic 1 when the temperature is even above 16°C. Design NOR-to-NAND gate combinational network to implement this specification. (10 marks)
- b) Obtain realizable logic diagram for a 4-to-2 priority encoder if the available signals are $\sim F_1[NL]$, F_0 , $\sim I_2[NL]$, I_3 , I_1 , I_0 . (5 marks)
- c) Design a PLA device that implements a 3-bit odd parity generation. (5 marks)