



TECHNICAL UNIVERSITY OF MOMBASA

SCHOOL OF ENGINEERING & TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

UNIVERSITY EXAMINATION

BACHELOR OF SCIENCE IN ELECTRICAL AND ELECTRONIC ENGINEERING

EEE 4205: ANALOGUE ELECTRONICS I

END OF SEMESTER EXAMINATION

SERIES: JULY 2025

TIME: 2 HOURS

DATE: Pick DateSelect MonthPick Year

Instructions to Candidates

You should have the following for this examination

-Answer Booklet, examination pass and student ID

This paper consists of FIVE questions. Attempt any other **THREE** Questions

Each question carries 20 marks

Do not write on the question paper.

QUESTION 1

- (a) Differentiate between degenerative and regenerative feedback. (4 marks)
- (b) State FOUR major merits of negative feedback in amplifiers (4 marks)
- (c) With the help of a suitable block diagram, show that the feedback voltage gain A_f for an amplifier with Negative feedback is given by: $A_f = \frac{A}{1 + A\beta}$ where A is the open loop voltage gain and β the feedback ratio. (6 marks)
- (d) An amplifier has an open loop voltage gain of 60 dB. When negative feedback is applied the gain reduces to 40 dB. Determine the feedback ratio, β in percentage. (6 marks)

QUESTION 2

- (a) With the help of well a labeled diagram, describe the construction of n-channel MOSFET. Draw its schematic symbol. (6 marks)
- (b) Describe and sketch the following characteristics of Bipolar Junction transistors
 - i. Input characteristics
 - ii. Transfer characteristics(4 marks)

(c) For the BJT amplifier in Fig. Q2 given that: $R_1 = 82 \text{ k}\Omega$, $R_2 = 15 \text{ k}\Omega$, $R_C = 3.3 \text{ k}\Omega$, $R_E = 1 \text{ k}\Omega$, $\beta = 100$ and $V_{CC} = 18 \text{ V}$,

- derive the expression for the d.c base current I_B
- Calculate the dc, collector-emitter voltage V_{CE}

(10 marks)

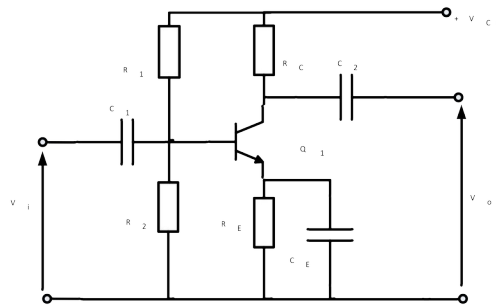


Fig. Q2.

QUESTION 3 (20 marks)

(a) Describe the properties and applications of the following semiconductor devices. In each case draw its schematic symbol.

- Light emitting diode
- Varactor diode

(4 marks)

(b) Describe with the help of suitable diagram and waveforms, the operation of a full-wave centre-tap rectifier hence derive the expression for its average d.c voltage.

(8 marks)

(c) Calculate the average d.c voltage of a *full-wave* rectifier if it is connected to the U.S domestic socket (120 V, 60 Hz) via a stepdown transformer with turns-ratio of 1:10.

(Assume the diode barrier voltage $V_d = 0.7 \text{ V}$)

(8 marks)

QUESTION 4

(a) Describe using suitable circuit and waveforms the filtering process in a half-wave rectifier.

(8 marks)

(b) State THREE advantages of bridge rectifier over full-wave centre-tap rectifier.

(3 marks)

(c) Determine in Fig Q4 the current through R_1 , D_1 and R_L given that $V_i = 12 \text{ V}$, $R_L = 2 \text{ k}\Omega$, $R_1 = 0.5 \text{ k}\Omega$ and the diode's Zener breakdown voltage $V_Z = 9 \text{ V}$.

(9 marks)

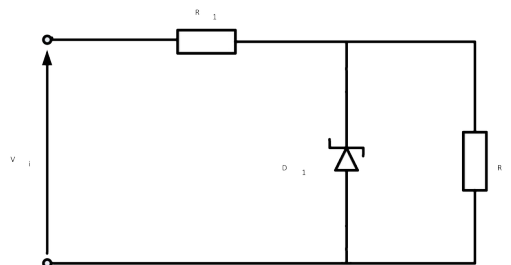


Fig. Q4

QUESTION 5

(a) Describe with the help of suitable diagrams THREE bipolar junction transistor amplifier configurations stating TWO major properties of each configuration.

(9 marks)

(b) State the THREE major requirements of a small signal amplifier.

(3 marks)

(c) For Fig.Q5, given $I_{DSS} = 10 \text{ mA}$, $V_P = -2 \text{ V}$, $R_G = 10 \text{ M}\Omega$, $R_S = 0.5 \text{ k}\Omega$, $R_D = 2 \text{ k}\Omega$, $V_{DD} = 20 \text{ V}$

- i. Determine using graphical method the gate-source voltage V_{GS}
- ii. Calculate the d.c drain-source voltage V_{DS} .

(8 marks)

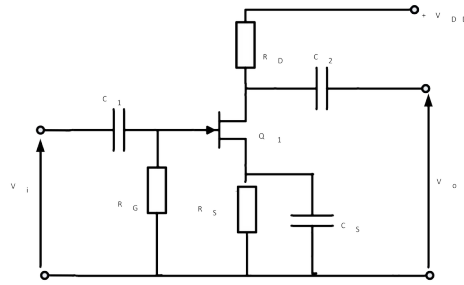


Fig. Q5