



TECHNICAL UNIVERSITY OF MOMBASA

School of Engineering and Technology

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

UNIVERSITY EXAMINATION 2024/2025

BACHELOR OF SCIENCE IN ELECTRICAL AND ELECTRONIC ENGINEERING

EEE 4409: DIGITAL SYSTEMS DESIGN I

TIME: 2 HOURS

SERIES: March, 2025

INSTRUCTIONS TO CANDIDATES

1. You are required to have the following for this examination;
 - Answer Booklet
 - A non- Programmable Calculator
2. Answer **ANY THREE** Questions.

Question ONE

- (a)
 - (i) State the design procedures for a combinational logic circuit.
 - (ii) Design a logic circuit that takes a 2-bit number and obtains its square. Implement using NOR gates **(8 marks)**
- (b) Design a logic circuit that has an enable input 'E' such that it converts a 3-bit gray code to its equivalent 3-bit binary value when $E = 0$ and when $E = 1$, it converts a 3-bit binary value to its gray code equivalent. Implement using appropriate encoder and decoder with minimum external IC package. **(12 marks)**

Question TWO

- a) Obtain a minimum SOP expression for the function below using the abbreviated binary method of tabular minimization. **(10 marks)**
$$F(A,B,C,D,E) = \sum_m(1, 5, 9, 10, 11, 12, 13, 14, 17, 21, 25, 26, 27, 28, 29, 30)$$
- b) Design a code converter that translates Excess-3 BCD to 8421BCD. Implement using PLA. **(10 marks)**

QUESTION THREE

- a) Develop a full ADDER using NAND gates. (11 marks)
- b) An electronic thermometer, designed for greenhouse use, has a 5-bit binary output representing a temperature range from 0°C to 31°C. A plug-in logic module is to be designed to output logic 1 when the temperature is even below and odd above 7°C. Design the following gate combinational networks to implement this specification:
- OR-to-NAND and
 - NOR-to-NOR. Comment on the two designs. (9 marks)

QUESTION FOUR

- a) Obtain logic diagram for a 4-to-2 priority encoder for the following available signals $\sim F_1[NL]$, F_0 , I_3 , $\sim I_2[NL]$, I_1 , I_0 . (5 marks)
- b) Given the state diagram in Figure Q4, generate the state table and design a sequence circuit using T-flip flops. (10marks)

 


Figure Q4

- c) Using a 4 – to – 1 multiplexer, implement the function

$$\mu f(A,B,C,D) = \sum_m (0, 2, 4, 7, 8, 10, 11, 12, 14, 15). \quad (5 \text{ marks})$$

QUESTION FIVE

- a) Explain the general technique to design a divide by N ripple counter, assuming J-K flip-flops with preset available. (5 marks)
- b) With aid of a transition table, design a modulo-6 T flip-flop based synchronous counter to repetitively count in the sequence 0, 1, 2, 3, 4, 5, 0.... The unused states will assume a value represented by 3. Other than the flip-flop IC packages, determine the minimum number of IC packages. (15marks)