

MOMBASA POLYTECHNIC UNIVERSITY COLLEGE

FACULTY OF ENGINEERING

DEPARTMENT OF COMPUTER SCIENCE AND INFORMATION TECHNOLOGY

EXAMINATION FOR

CERTIFICATE IN COMPUTER MAINTENANCE & INFORMATION COMMUNICATION TECHNOLOGY-  
CMNT2K 11M

FUNDAMENTALS OF PHYSICS (APS 1103)

Answer question One and any other Two questions.

**QUESTION 1**

a) Explain the OHMS law using graphical illustrations.

(4marks)

b) Three resistors of  $20\text{K}\Omega$ ,  $10\text{K}\Omega$  and  $80\text{K}\Omega$  are connected in parallel. They are then connected in series to  $50\text{K}\Omega$  and  $70\text{K}\Omega$  resistors. The network is then supplied with 24V d.c. Calculate:

- i. total resistance in the circuit
- ii. voltage drop in the parallel circuit
- iii. total current in the circuit
- iv. current through  $2\text{K}\Omega$ ,  $10\text{K}\Omega$  and  $80\text{K}\Omega$  resistors
- v. total power in the circuit

( 9marks)

c) Determine the colour codes for the following resistors:

- i.  $1.9\text{M}\Omega \pm 20\%$
- ii.  $330\text{K}\Omega \pm 10\%$
- iii.  $470\Omega \pm 5\%$
- iv.  $4.7\text{M}\Omega \pm 2\%$

(8marks)

e) With the aid of a circuit diagram explain the operation of a full wave bridge rectifier.

(9marks)

**QUESTION 2**

a) Calculate the maximum and the minimum values of the following resistors given the colour codes. (All answers in  $\text{K}\Omega$ )

- i. violet, green, yellow
- ii. Blue, black, purple, silver
- iii. green, red, yellow, gold

(10marks)

b) Differentiate between step-up and step-down transformers.

(4 marks)

c) Briefly explain the following:

- i. Intrinsic semiconductor
- ii. Extrinsic semiconductor

iii. Doping (6 marks)

### **QUESTION 3**

a) Define the following terms:

- i. Capacitance
- ii. Time constant
- iii. Transmission ratio
- iv. Self inductance
- v. Mutual inductance

( 10 marks)

c) With the aid of circuit diagrams explain the following with regard to diodes:

- i. Forward biasing
- ii. Reverse biasing

( 6 marks)

c) Differentiate between rectification and voltage regulation.

(4 marks)

### **QUESTION 4**

a) Three capacitors of  $300\mu\text{F}$ ,  $200\mu\text{F}$  and  $400\mu\text{F}$  are connected in series and then connected to  $3600\mu\text{F}$  capacitor in parallel. The network is then supplied with 12V D.C.

- i. Draw the circuit diagram
- ii. Calculate the capacitance in the circuit
- iii. Charge across the  $3600\mu\text{F}$  capacitor
- iv. Energy in the circuit

(10 marks)

b) Describe two applications of P-N junction diodes. (4 marks)

c) Explain the kirchoffs law on:

- i. Current
- ii. Voltage

(6 marks)

### **QUESTION 5**

a) Using circuit diagram show the following transistors configurations:

- i. Common base
- ii. Common collector
- iii. Common emitter

(9 marks)

b) Explain the following:

- i. Resistance
- ii. Reactance
- iii. Impedance

(6 marks)

c) With the aid of diagrams differentiate between N-P-N and P-N-P transistors.

(5 marks)