



TECHNICAL UNIVERSITY OF MOMBASA

Faculty of Engineering and Technology
DEPARTMENT OF MEDICAL ENGINEERING

DIPLOMA IN MEDICAL ENGINEERING
(DME 213 Y2 S2)

EHL 2204
DIGITAL ELECTRONICS

SPECIAL/SUPPLEMENTARY EXAMINATIONS

SERIES: JULY, 2014

TIME: 2 HOURS

INSTRUCTIONS TO CANDIDATES:

- Answer any **THREE** questions
 - You are required to carry a scientific calculator for this paper.
- This paper consists of **3 PRINTED** pages

QUESTION ONE

- (a) (i) Convert the decimal number 23 to Binary. (4 marks)
- (ii) Perform $(1-3)_{10}$ by 1's complement (4 marks)
- (b) (i) Define the term decoder
- (ii) Design a Binary-to-octal decoder and implement it using gates. (10 marks)

Convert the decimal number 17 to excess-3 BCD (2 marks)

QUESTION TWO

- (i) Convert the decimal number 17 to octal. (3 marks)
- (ii) Perform $(7-9)_{10}$ by 2's complement (8 marks)
- (b) Illustrate using a schematic diagram and truth table how a RS latch can be converted into a JK flip flop. (6 marks)

$$F = AB + \bar{B}C\bar{D}$$

Find the minterms of (6 marks)

QUESTION THREE

- (a) (i) Convert 27_{10} to Hexadecimal (3 marks)
- (ii) Explain, giving **TWO** reasons, why BCD is not used in digital computers. (4 marks)
- (b) (i) Design a FULL adder circuit and implement it using the minimum number of gates. (12 marks)
- (ii) Define the term conjunctive normal form as used in Boolean equations. (1 marks)

QUESTION FOUR

(a) (i) Convert $9B4_{16}$ into decimal (3 marks)

(ii) Add $275_{10} + 241_{10}$ using the 8421 BCD (4 marks)

$$F = A + B\bar{C}$$

(b) (i) Find the max-term of (10 marks)

(ii) Perform $(2345 - 6879)_{10}$ by 10s complement (3 marks)

QUESTION FIVE

(a) (i) Convert 124.35_8 into hexadecimal. (3 marks)

(ii) Convert 101_{10} to Cray code (3 marks)

(b) Sensor D is a daytime sensor while sensor E is the timetable sensor for digital electronics lessons. DME 213 class occupies lab 6 or med 5 for electronic lessons. Sensors L and M detect their presence in Lab 6 and in Med 5 respectively.

Design a logic circuit which will round an alarm whenever the students are absent and light lamps they are present at right. Implement the circuit. (14 marks)