



# **Technical University of Mombasa**

## **Faculty of Engineering and Technology**

### **DEPARTMENT OF MECHANICAL AND AUTOMOTIVE ENGINEERING DIPLOMA IN MECHANICAL ENGINEERING (PLANT)**

## **EEE 2140: ELECTRICAL ENGINEERING SCIENCE I**

YEAR I SEMESTER I

SPECIAL/SUPPLEMENTARY EXAMINATION

February 2013 SERIES

TIME: 2 HOURS

### ***INSTRUCTIONS TO CANDIDATES:***

You should have the following for this examination:

- Answer booklet
- Non-programmable scientific calculator

This paper consists of **FIVE** questions

Attempt any **THREE** questions. Maximum marks for each part of a question are as shown.

***This paper consists of 3 printed Pages***



### Question ONE

- a) I. Define the following terms in relation to magnetic circuits
- Reluctance
  - Magnetic permeance
- II. With reference to electromagnetic induction state the two laws advanced by Michael Faraday. **(8marks)**

- b) I. Explain any FOUR characteristics of magnetic flux line all magnetic materials.
- II. A coil of 200 turns is wound uniformly over a wooden ring having a mean circumference of 600mm and a uniform cross-sectional area of  $500\text{mm}^2$  if the current through the coil is 4A,

Calculate:

- The magnetic field strength
- The flux density
- The total flux

- III. Explain any FOUR characteristics of magnetic flux lines in all magnetic materials.


**(12marks)**

### Question TWO

- a) I. State the TWO laws of Kirchoffs as used in electrical engineering science.
- II. State the superposition Theorem as applied in electrical engineering science.

**(6marks)**


- b) I.

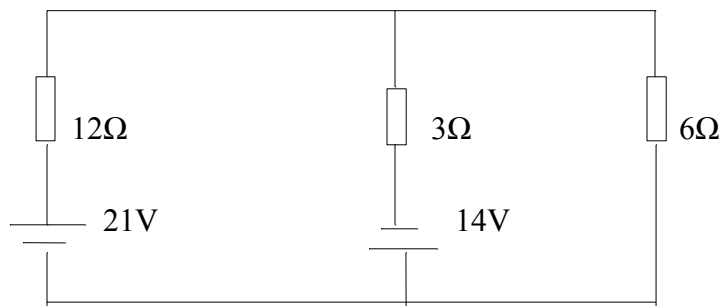


The circuit shown above was used in automobile system; by using superposition Theorem Calculate the magnitude and the direction of the current flowing through  $6\Omega$  resistor. Assume the internal resistances of the batteries to be zero. (8marks)

- II. The electrical d.c network shown below was used in an engineering works; calculate the current flowing through resistor  $10\Omega$  using Kirchhoff's laws.

**(6marks)**

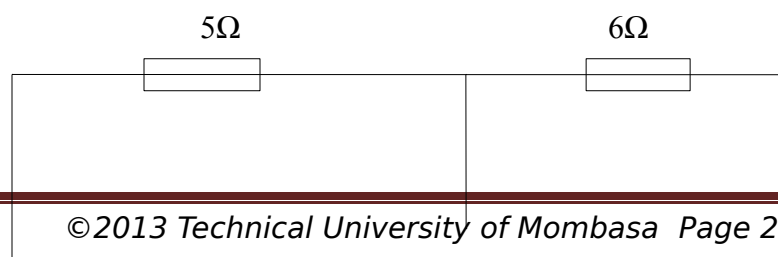



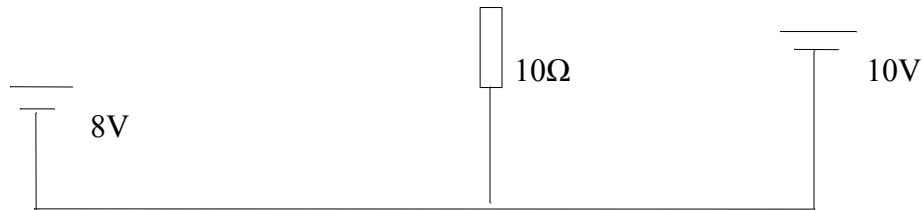


### Question THREE

- a) I. state any THREE methods used in battery charging  
 II. Explain the following terms as used in batteries and cells. **(7marks)**
- b) I. Ten cells of 1.5 volts each were connected in series to a load of  $0.2\Omega$ , the internal resistance of each battery was  $0.2\Omega$ .

Calculate:

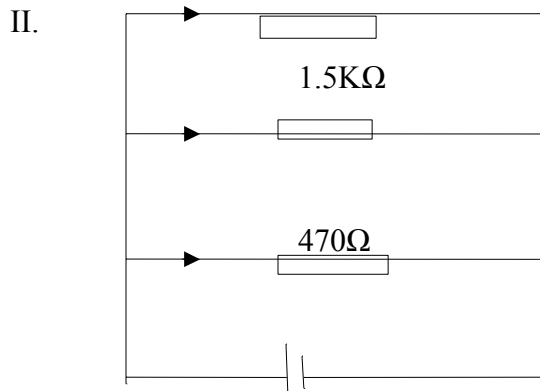- i) The current flowing in the circuit  
 ii) The p.d at each battery terminal  
 $330\Omega$



The circuit shown above was used instrumentation engineering circuit determine:

- i) The total resistance of the network  
 ii) The total current of the network  
 iii) The current flowing in each resistor **(13marks)**

### Question FOUR

- a) i. Define the following units in engineering:  
 i) Ohms  
 ii) Newtons  
 iii) Watts  
 iv) Coulomb  
 v) Volts  
 ii. State any TWO fundamental quantities and THREE derived. **(10marks)**
- b) I. An hydro-electric station has a turbine of efficiency of 86% and a generator of efficiency of 92%. The effective head of the water is 150m. Calculate the volume



of water used when delivering a load of 40Mw for 6 hours the water weighs  $1000\text{Kg/m}^3$ .

- II. In an electrical industry a motor was used to drive a load of 20KN for a distance of 30metre, what is the work done by the motor? If the motor was operated for 10hours what is the power of the motor in doing the work.

**(10marks)**

### Question FIVE

- a) I. State the coulombs laws electrostatics. **(2marks)**  
II. Explain the following terms as used in electrostatics

- i) Electric field strength
- ii) Electric field density
- iii) Permittivity


**(6marks)**

- b) I. A ceramic capacitor has an effective plate area of  $4\text{cm}^2$  separated by 0.1mm of ceramic of a relative permittivity of 100.

(a) Calculate the capacitance of the capacitor in PICO farads. If the capacitor in part (a) is given a change of  $1.2\mu\text{C}$  what will be the pd between the plates.

**(4marks)**

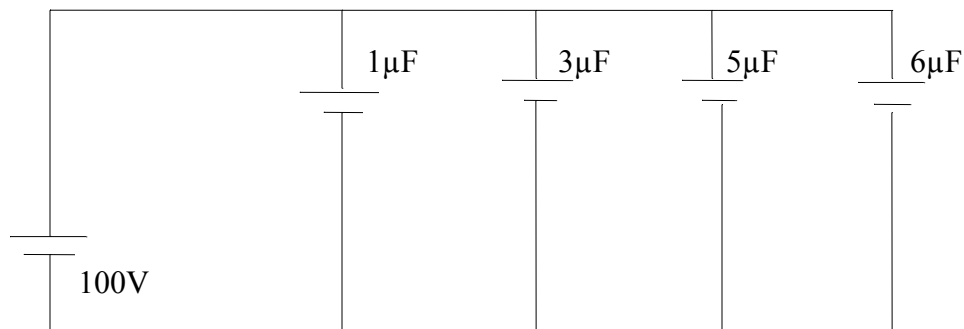- II. The following capacitors were used to construct a telecommunication circuit, they were all connected in parallel as shown below.



- i. The equivalent circuit capacitance of the circuit
- ii. The total charge of the circuit
- iii. The total change of the circuit
- iv. The change for each capacitor
- v. The energy stored in the whole circuit

**(8marks)**