



TECHNICAL UNIVERSITY OF MOMBASA

# Faculty of Applied & Health Sciences

DEPARTMENT OF MATHEMATICS & PHYSICS

CERTIFICATE IN BUILDING & CIVIL ENGINEERING (CBCE 13M)

**APS 1150: PHYSICAL SCIENCE FOR ENGINEERS**

SPECIAL/SUPPLEMENTARY EXAMINATION

**SERIES: AUGUST 2016**

**TIME: 2 HOURS**

**Instructions to Candidates:**

You should have the following for this examination

- *Answer Booklet*

This paper consist of **FIVE** questions

Answer question **ONE (COMPULSORY)** and any other **TWO** questions

Maximum marks for each part of a question are as shown

This paper consists of **THREE** printed pages

**Mobile phones are not allowed inside the examination room  
Do NOT write on the question paper**

**Question One (Compulsory)**

- a) State the following:  
(i) Kirchhoff Law on current  
(ii) Kirchhoff Law on voltage **(4 marks)**
- b) Describe the factors that affect resistance of a wire. **(4 marks)**
- c) Define the following terms stating their SI units:  
(i) Charge  
(ii) Electromotive force  
(iii) Capacitance  
(iv) Resistivity **(4 marks)**
- d) Calculate the resistance of a copper wire of 240m with a cross-section area of  $1.5\text{mm}^2$  ( $\rho$  for copper =  $0.0175 \times 10^{-6} \Omega \text{ m}$ ) **(8 marks)**

**Question Two**

- a) Using graphical illustrations, state and explain the Ohm's Law **(6 marks)**
- b) Two resistors of  $100 \Omega$  and  $150 \Omega$  are connected in series and the connected in parallel to a  $130 \Omega$  resistor. The circuit is supplied with 15v D.C.. Determine:  
(i) Total current in the circuit  
(ii) Current through  $130 \Omega$  resistor  
(iii) Voltage drop across  $150 \Omega$  resistor  
(iv) Total power in the circuit **(8 marks)**
- c) With the aid of a circuit diagram, explain the operation of a half-wave rectifier circuit. **(6 marks)**

**Question Three**

- a) Explain the following:  
(i) Rectification  
(ii) Voltage regulation **(4 marks)**
- b) With the aid of symbolic diagrams. Explain the following with regard to diodes:  
(i) Forward Biasing  
(ii) Reverse Biasing **(6 marks)**
- c) Three capacitors of  $470 \mu\text{F}$ ,  $300 \mu\text{F}$  and  $150 \mu\text{F}$  are connected in series and then connected in parallel

to a  $100 \mu F$  capacitor. The circuit is supplied with 12V D.C. Determine:

- (i) Total capacitance in the circuit
- (ii) Charge across the circuit
- (iii) Current through  $100 \mu F$  capacitor
- (iv) Total energy in the circuit **(10 marks)**

#### Question Four

- a) With the aid of symbolic diagrams, describe:
  - (i) Step-up transformer
  - (ii) Step-down transformer **(4 marks)**
  
- b) Explain the following
  - (i) Frequency
  - (ii) Period
  - (iii) Amplitude **(6 marks)**
  
- c) A transformer of 8:1 turns ratio is supplied with 110v, produces 200w at the output. Calculate:
  - (i) Primary current
  - (ii) Secondary current
  - (iii) Secondary voltage **(6 marks)**
  
- d) Using symbols differentiate between, P-N-P and N-P-N transistors **(4 marks)**

#### Question Five

- a) Explain the factors which affect the capacitance of a capacitor. **(4 marks)**
  
- b) Describe the following terms:
  - (i) Mutual induction
  - (ii) Self induction **(6 marks)**
  
- c) With the aid of a circuit diagram. Explain the operation of a temperature stabilized single transistor amplifier. Show that 
$$U_{CC} = I_C R_C + U_{CE} + I_E R_E$$
 **(10 marks)**