



# TECHNICAL UNIVERSITY OF MOMBASA

## Faculty of Applied & Health Sciences

DEPARTMENT OF MATHEMATICS & PHYSICS

UNIVERSITY EXAMINATION FOR:

**BACHELOR OF SCIENCE IN MATHEMATICS & COMPUTER SCIENCE**

APS 4112: PHYSICS ELECTRONICS

**SPECIAL/SUPPLEMENTARY EXAMINATION**

SERIES: JULY 2014

**TIME ALLOWED: 2 HOURS**

**Instructions to Candidates:**

You should have the following for this examination

- *Mathematical tables*
- *Scientific Calculator*

This paper consist of **FOUR** questions

Answer question **ONE (COMPULSORY)** and any other **TWO** questions

Maximum marks for each part of a question are as shown

This paper consists of **FOUR** printed pages

---

**Question One (Compulsory)**

a) Define the following terms:

- |                                   |           |
|-----------------------------------|-----------|
| (i) Donor and acceptor impurities | (2 marks) |
| (ii) Rectification                | (1 mark)  |
| (iii) Peak inverse voltage        | (1 mark)  |
| (iv) Pn junction                  | (1 mark)  |
| (v) Zener diode                   | (1 mark)  |

b) Distinguish between conductors, semiconductors and insulators. (3 marks)

c) Find the current flowing through the resistors and the corresponding voltage drops in the resistors in the figure below (assume the diodes are ideal) (3 marks)

- d) A half wave crystal diode rectifier is transformer fed from a 240V line. Calculate:
- (i) Turn ratio (4 marks)
  - (ii) Diode Piv rating if the circuit provides an output of 24Vdc. (2 marks)
- e) Explain THREE types of filter circuits. (3 marks)
- f) Explain how a Zener diode acts as a voltage regulator. (3 marks)
- g) (i) In a common base connection, the emitter current is 2mA. If the emitter circuit is open, the collector current is  $40 \mu A$ . Find the term collector current given that  $\alpha = 0.92$  (3 marks)
- (ii) Draw circuit diagrams to distinguish between npn and pnp transistors. (2 marks)

### Question Two

- a) Explain the working of a npn and pnp transistors. (5 marks)
- b) Find the value of B if (i)  $\alpha = 0.9$  and (ii)  $0.94$  and (iii) 0.97. (3 marks)
- c) Explain the operation of a transistor as:
- (i) An amplifier (3 marks)
  - (ii) A switch (3 marks)
- d) The base current in a transistor is 0.02mA and emitter current is 1.0mA. Calculate the values of  $\alpha$  and  $\beta$ . (4 marks)
- e) Define the following:
- (i) Tished Amplifiers (2 marks)

### Question Three

- a) Explain transistor biasing by:
- (i) Base resistor method (3 marks)
  - (ii) Biasing with feedback resistor (3 marks)

- b) The figure below shows a Silicon transistor with  $\beta = 120$  biased by base resistor method. Draw the d.c. load line and determine the operating point. **(7 marks)**

- c) The figure below shows a two stage transistor amplifier biased by base resistor method. What are collector-emitter voltages? Assume  $\beta = 110$  and  $V_{BE} = 0.77V$  **(7 marks)**

#### Question Four

- a) Define the following terms in relation to transistor amplifier circuit. **(8 marks)**  
(i) Input resistance

- (ii) Output resistance
- (iii) d.c. load
- (iv) a.c load

b) In the figure below the transistor has  $\beta = 80$ . Find the voltage gain if input resistance  $R_{in} = 0.4 \text{ K}\Omega$ . (6 marks)

c) State THREE features incorporated into voltage amplifier and power amplifier so as to achieve high amplification. (6 marks)

**Question Five**

- a) Define the following terms:
  - (i) Frequency response (1 mark)
  - (ii) Band width (1 mark)
  - (iii) Decibel gain (1 mark)
- b) Express the following gains as a number:
  - (i) Power gain of 40db (2 marks)
  - (ii) Power gain of 53db (2 marks)
- c) A three stage amplifier has the first stage voltage gain of 200, second stage voltage gain of 300 and third stage of 500. Find the total voltage gain in db. (7 marks)
- d) A class A power amplifier has zero signal collector current of 40mA. If the collector supply voltage is 4v find:
  - (i) Maximum a.c. power output (2 marks)
  - (ii) Power rating of transistor (2 marks)

(iii) Maximum collector efficiency

**(2 marks)**