



TECHNICAL UNIVERSITY OF MOMBASA

Faculty of Applied & Health Sciences

DEPARTMENT OF MATHEMATICS & PHYSICS

UNIVERSITY EXAMINATION FOR DEGREE OF:

BACHELOR OF TECHNOLOGY IN ANALYTICAL CHEMISTRY

APS 4103: PHYSICS FOR CHEMISTS

END OF SEMESTER EXAMINATION

SERIES: APRIL 2015

TIME ALLOWED: 2 HOURS

Instructions to Candidates:

You should have the following for this examination

- *Mathematical tables*
- *Scientific Calculator*

This paper consist of **FOUR** questions

Answer question **ONE (COMPULSORY)** and any other **TWO** questions

Maximum marks for each part of a question are as shown

This paper consists of **THREE** printed pages

Take

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ Fm}^{-1}$$

$$K = \frac{1}{4\pi\epsilon_0} = 9 \times 10^9 \text{ Nm}^2\text{C}^{-2}$$

$$g = 9.8 \text{ ms}^{-2}$$

Mass of electron = $1.6 \times 10^{-19} \text{ C}$

Permeability of free space, $\mu_0 = 4\pi \times 10^{-7} \text{ Hm}^{-1}$

Universal gravitational constant $G = 6.63 \times 10^{-11} \text{ Nm}^2\text{g}^{-2}$

Question One (Compulsory)

a) Use dimensional analysis to check if the following equation is valid:

$$V^2 = 2ax$$

where V is the velocity , a is the acceleration and x is the displacement

(3 marks)

- b) (i) Differentiate between velocity and speed (1 mark)
- (ii) An object is dropped into a well and hits the water 2 seconds after being released. How deep is the well (3 marks)
- (iii) If the velocity of a particle changes by the same amount for each similar time interval what can you say about the acceleration (1 mark)
- c) Find the equivalent resistance of the following combinations of resistors:
- (i) Parallel arrangement of 3Ω, 2Ω and 5Ω resistor (2 marks)
- (ii) Series combination of 3 Ω and 4 Ω resistor in parallel with a 5 Ω resistor (2 marks)
- d) Explain the term half life as used in discharging of a capacitor (1 mark)
- e) (i) Show that for a linear conductor or electric current, resistivity j , is given by:
- $$\tau = \frac{RA}{L}$$
- where R is the resistance and L is the length of the conductor (3 marks)
- (iii) Distinguish between ohmic and non-ohmic conductors (1 mark)
- f) A 2.00μF and a 4.00μF capacitors are connected to a 60.0v battery. How much charge is supplied by the battery in charging the capacitors when the wiring is in series (3 marks)
- g) (i) State Ohm's Law (1 mark)
- (ii) Show that the effective resistance R of three resistors connected in parallel is given as:
- $$R_T = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$
- (4 marks)
- h) The charges in figure 1 below are placed at the corners of an equilateral triangle of side a
- Figure 1**

Show that the force experienced by charge Q1 is given by:

$$F = \frac{a^3 kQ^3}{a^2}$$

if all the charges are identical (6 marks)

Question Two

- a) What do you understand by the term capacitance? (2 marks)

$$C_1 = 2\mu F, C_2 = C_3 = 0.5\mu F$$

- b) In the circuit below, and v = 6v

Figure 2

- (i) Determine the charge in each capacitor (3 marks)
(ii) Calculate the potential difference across each capacitor (4 marks)
- c) A steady uniform current of 5mA flows axially along a metal cylinder of cross sectional area 0.02mm^2 , length 5m and resistivity $3 \times 10^{-5}\Omega\text{m}$. Calculate:
- (i) The potential difference across the ends of the cylinder (4 marks)
(ii) The rate of heat production (3 marks)
- d) State the TWO Kirchhoff's Laws (4 marks)

Question Three

- a) Define the following terms and give the dimensions:
- (i) Distance
(ii) Displacement
(iii) Acceleration
(iv) Friction (8 marks)
- b) Derive Newton's second law (3 marks)
- c) A 600N object is to be given an acceleration of 0.7ms^{-2} . How large an unbalanced force must act upon it? (3 marks)
- d) Two masses of 0.5kg and 0.25kg are connected by a light inextensible string, which passes over a smooth light pulley. If the system is released from rest with the string taut, find the acceleration of each mass and distance travelled in 1 second from rest (6 marks)

Question Four

- a) (i) State Coulomb's Law for the electrostatic force between two point charges (2 marks)
- (ii) Three positive charges lie along the same line as shown in figure 2. Derive an expression for the force acting on Q_2 (2 marks)

+

- b) A $10\mu\text{F}$ capacitor is charged for a 30V supply and then connected across an uncharged $50\mu\text{F}$ capacitor. Calculate the:
- (i) Final potential difference across the combination **(4marks)**
 - (ii) Initial and final energies **(4 marks)**

- c) Consider two charges Q_1 and Q_2 separated initially by a distance r . If the charge Q_2 is moved towards Q_1 such that the new separation distance is r_1 , show that the work done in moving the charge Q_2 is

$$W = \frac{Q_1 Q_2}{4\pi\epsilon_0} \left(\frac{1}{r} - \frac{1}{r_1} \right)$$

given by:

(6 marks)