



TECHNICAL UNIVERSITY OF MOMBASA
Faculty of Applied & Health
Sciences

DEPARTMENT OF MATHEMATICS & PHYSICS
DIPLOMA IN ARCHITECTURE (DARCH 14S)

APS 2102: PHYSICS II

END OF SEMESTER EXAMINATION
SERIES: APRIL 2015
TIME ALLOWED: 2 HOURS

Instructions to Candidates:

You should have the following for this examination

- *Answer Booklet*
- *Mathematical Table*

This paper consist of **FIVE** questions

Answer question **ONE (COMPULSORY)** and any other **TWO** questions

Maximum marks for each part of a question are as shown

This paper consists of **THREE** printed pages

Question One (Compulsory)

- a) For an inverting amplifier using an OP.AMP $R_{in} = 100K\Omega$ and $R_f = 500K\Omega$. Calculate the output voltage if the input voltage is $-2V$ **(5 marks)**
- b) Calculate the output voltage of a non-inverting constant gain multiplier for value of $V_{in} = 2V$, $R_f = 500K\Omega$ and $R_{in} = 100K\Omega$ **(5 marks)**
- c) What is the output voltage of a OP-AMP summing amplifier for the following sets of input voltages and resistors ($R_f = 1M\Omega$ for all cases)
- $V_1 = 1V, V_2 = +2V, V_3 = +3V, R_1 = 500K\Omega$
 $R_2 = 1M\Omega$ and $R_3 = 1M\Omega$ **(5 marks)**
- (i)
- $V_1 = -2V, V_2 = 3V, V_3 = +1V, R_1 = 200K\Omega$
 $R_2 = 500K\Omega$ and $R_3 = 1M\Omega$ **(5 marks)**
- (ii)

Question Two

- a) A comparator is a circuit which can compare signals and give an output with aid of an OP-AMP. Show how a comparator can be configured and how it operates **(10 marks)**
- b) A non-inverting using an OP-AMP is supplied with a signal $0.08 \cos wt$ in the input. The amplifier has an amplification (G) of 100.
- (i) Determine the expression of the output of the amplifier **(2 marks)**
- (ii) Draw the sketch of the output signal **(2 marks)**
- (iii) Determine the value of the External resistors which will give the amplifier the respective gain **(6 marks)**

Question Three

- a) Briefly explain the following:
- (i) Voltage rectification **(2 marks)**
- (ii) Voltage regulation **(2 marks)**
- b) Draw the symbols of the following Thyristors:
- (i) SCR
- (ii) TRIAC
- (iii) DIAC **(3 marks)**
- c) (I) With the aid of a graph show the characteristics and ratings of an SCR (Silicon controlled Rectifier) **(5 marks)**
- (II) Explain the following parameters with regard to the characteristic of SCR
- (i) Forward break over voltage **(2 marks)**
- (ii) Holding current **(2 marks)**
- (iii) Forward blocking region **(2 marks)**

(iv) Reverse break down voltage

(2 marks)

Question Four

a) State the FIVE ideal properties of operational amplifier

(5 marks)

b) State the least FIVE application of OP-AMP's

(5 marks)

c) With the aid of a circuit diagram, show that the gains of inverting and non-inverting amplifiers are

given by $G = -R_f / R_2$ and $G = \frac{R_1 + R_f}{R_1}$ respectively

(10 marks)

Question Five

a) Design an inverting and non-inverting amplifier which will give a gain of -100 and 100 respectively.

(10 marks)

b) With the aid of two transistor equivalent circuit show the operation of a latch

(5 marks)

c) State at least FIVE application of SCR's

(5 marks)