



TECHNICAL UNIVERISTRY OF MOMBASA

Faculty of Engineering & Technology

DEPARTMENT OF COMPUTER SCIENCE & INFORMATION TECHNOLOGY

DIPLOMA IN INFORMATION COMMUNICATION TECHNOLOGY (DICT 14S)

EEE 2135: ELECTRONICS

END OF SEMESTER EXAMINATION

SERIES: APRIL 2015

TIME: 2 HOURS

Instructions to Candidates:

You should have the following for this examination

- *Answer Booklet*

This paper consists of **FIVE** questions.

Attempt question **ONE (Compulsory)** and any other **TWO** questions

Maximum marks for each part of a question are as shown

This paper consists of **FOUR** printed pages

Question One (Compulsory)

- a) Given the colour codes of the following resistors, find the value of each resistor:-
- (i) Yellow, purple, Red, Silver (2 marks)
 - (ii) Brown, Orange, Brown, Gold (2 marks)
 - (iii) Orange, Orange, Orange, Red (2 marks)
 - (iv) Yellow, Orange, Red (2 marks)
- b) Calculate the total Resistance R_T of figure 1 (4 marks)
- 5K
- c) Use nodal analysis to calculate V_x in the following circuit. (8 marks)
- 2

Question Two

- a) Design rectifier with given specification. Specification = $V_{dc} = 12V$, $V_r < 0.12V$, $I_{dc} = 3A$
Assumption $V_{ou} = 1V$ input frequency = 60Hz. Use full-wave bridge rectifier.
- b) Find dc output voltage, output current, ripple voltage, conduction interval conduction angle of RC loaded half-wave rectifier. GIVEN DATA:
- Secondary voltage $V_{rms} = 13.4$ (50Hz), $R = 12\Omega$, $C = 50,000\mu F$, $V_{ou} = 1V$

Question Three

- a) Find the therein equivalent of the circuit between node A and B by performing a sequence of Norton \leftrightarrow therein transformations.

Figure 5

- b) Calculate the therein and Norton equivalent network at the terminal A and B in figure below in two ways a) by combining resistors to simplify the circuit and b) by using nodal analysis.

Figure 4

- c) Draw the thevenin equivalent circuit network below and find the value of its components of figure 5 below **(6 marks)**

9K

Question Four

- a) (I) The SCR shown has a gate trigger voltage $V_T = 1V$. gate trigger current $I_T = 5mA$ and $I_H = 3mA$

Z

- (i) What is the V_{out} when SCR is OFF?
(ii) What is V_{in} that trigger the SCR?
(iii) If V_{CC} is decreased until the SCR open, what is the value of V_{CC} ? **(9 marks)**

- (II) Draw and explain the V-I characteristic of SCR? **(6 marks)**

Question Five

- a) Design a common emitter BJT circuit such that $V_{CE} = 1.8V$ take $\beta = 40$ **(6 marks)**

Figure 7

- b) Calculate the value of I_C , I_B , I_E , V_C , V_B of the following 'UPU' circuit mode of transistor $\beta = 120$. Also state the mode of transistor (8 marks)
- n