



TECHNICAL UNIVERISTRY OF MOMBASA

Faculty of Engineering & Technology

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

DIPLOMA IN ELECTRICAL ELECTRONIC ENGINEERING (DEEE 2)

EEE 2101: ANALOGUE ELECTRONICS

END OF SEMESTER EXAMINATION

SERIES: DECEMBER 2014

TIME: 2 HOURS

Instructions to Candidates:

You should have the following for this examination

- *Answer Booklet*

This paper consists of **FIVE** questions. Answer any **THREE** questions

Maximum marks for each part of a question are as shown

This paper consists of **THREE** printed pages

Question One (Compulsory)

- a) Define the following terms as applied to atomic theory:
(i) Element
(ii) Atom
(iii) Compound (3 marks)
- b) With the aid of appropriate sketches, explain the formation of a P and N extrinsic semiconductor material (6 marks)
- c) (i) Draw the characteristics of the P-N junction diode and explain its shape. (6 marks)
(ii) Explain how the diode can be used to protect the measuring instrument (5 marks)

Question Two

- a) Define the following terms as applied in diodes:
(i) Peak inverse voltage
(ii) Junction capacitance
(iii) Maximum operating temperature
- b) With the aid of a circuit diagram, explain the operation of a bridge rectifier with a capacitive filter.
- c) (I) Draw a voltage tripler circuit and outline the cycles of operation (4 marks)
(II) A 4.7v Zener diode is to be used in power a stabilizing circuit. If 60mA is required at the output and the supply voltage is 8V, determine:
(i) The power rating of the diode
(ii) The series resistor to be connected to the circuit
(iii) The rating of the series resistor (5 marks)


Question Three

- a) With the aid of a diagram, describe the operation of an NPN transistor (4 marks)
- b) Use a circuit diagram to explain how biasing and stabilization is achieved in a collector biased network. (6 marks)
- c) (I) For the circuit of figure 1, $V_{ce} = 0$, $V_{\epsilon} = IV$ $IC = 9.2mA$ and $\beta = 100$. Determine:
(i) The value of I_B
(ii) The values of R_1 and R_2 assuming that the current through R_2 is 10 x the basic current.
- (II) State the function of the capacitors in the circuit (10 marks)

Question Four

- a) Using sketches, explain the operation of the following classes of amplifiers:
Class A
Class B
Class C (9 marks)

 - b) State any THREE comparisons between BJT and FET **(3 marks)**
- c) (i) With the aid of diagrams describe the construction of an enhancement mode MOSFET.
- (ii) For the circuit of figure 2, show that $AV = g_m R_L$ stating any assumptions made. **(8 marks)**



Question Five

- a) Define the following terms:
- (i) Sensitivity
 - (ii) Aquadag
 - (iii) Thermionic emission **(3 marks)**
- b) Draw the cathode Ray Oscilloscope (CRO) block diagram and state the functions of each **(10 marks)**
- c) (i) Explain how a CRO can be used to measure voltages
- (ii) Determine the value of the unknown frequency for figure 3 if the known frequency is 15KHZ **(7 marks)**

Figure 3