



THE MOMBASA POLYTECHNIC UNIVERSITY COLLEGE

(A Constituent College of Jkuat)

Faculty of Engineering and Technology

DEPARTMENT OF COMPUTER SCIENCE & INFORMATION TECHNOLOGY

DIPLOMA IN INFORMATION & COMMUNICATION TECHNOLOGY –
DICT2K11/DICT11M

APS 2103: PHYSICS

END OF SEMESTER EXAMINATIONS

SERIES: AUGUST/SEPTEMBER 2011

TIME: 2 HOURS

Instructions to Candidates:

You should have the following for this examination

- *Answer booklet*

Answer question **ONE (COMPULSORY)** and any other **TWO** questions

This paper consists of **THREE** printed pages

Question 1 (Compulsory)

- a) State the Kirchhoff Law on
i) Current
ii) Voltage (4 marks)
- b) Calculate the maximum and the minimum values of the following resistors given the colour codes (all answers in $K \Omega$)
i) Red, green, yellow
ii) Blue, black, purple, silver
iii) Yellow, red, yellow, gold (9 marks)
- c) Determine the colour codes for the following resistors:
i) $1.9M \Omega \pm 20\%$
ii) $330K \Omega \pm 10\%$
iii) $470 \Omega \pm 5\%$
iv) $4.7M \Omega \pm 2\%$ (8 marks)
- d) Differentiate between alternating current (A.C) and direct current (D.C) citing application for each (9 marks)

Question 2

- a) Three resistors of $2K \Omega$, $10K \Omega$ and $80K \Omega$ are connected in parallel. They are then connected in series to $5K \Omega$ and $7K \Omega$ resistors. The network is then supplied with 12V d.c. Calculate:
i) Total resistance in the circuit
ii) Voltage drop in the parallel circuit
iii) Total current in the circuit
iv) Current through $2K \Omega$, $10K \Omega$ and $80K \Omega$ resistors
v) Total power in the circuit (10 marks)
- b) Differentiate between step-up and step-down transformers (4 marks)
- c) With the aid of circuit diagrams, explain the following with regard to diodes
i) Forward biasing
ii) Reverse biasing (6 marks)

Question 3

- a) Define the following terms:

- i) Capacitance
 - ii) Time constant
 - iii) Transmission ratio
 - iv) Self inductance
 - v) Mutual inductance
- (10 marks)

- b) Briefly explain the following
- i) Intrinsic semiconductor
 - ii) Extrinsic semiconductor
 - iii) Doping
- (6 marks)
- c) Differentiate between rectification and voltage regulation
- (4 marks)

Question 4

- a) Three capacitors of $300\ \mu\text{F}$ and $400\ \mu\text{F}$ are connected in series and then connected to $3600\ \mu\text{F}$ capacitor in parallel. The network is then supplied with 12V D.C.
- i) Draw the circuit diagram
 - ii) Calculate the capacitance in the circuit
 - iii) Charge across the $3600\ \mu\text{F}$ capacitor
 - iv) Energy in the circuit
- (10 marks)
- b) State **FOUR** applications for transformers
- (4 marks)
- c) With the aid of graphs explain the ohms law on:
- i) Current
 - ii) Voltage
- (6 marks)

Question 5

- a) Using circuit diagram show the following transistors configurations:
- i) Common base
 - ii) Common collector
 - iii) Common emitter
- (9 marks)
- b) Explain the following:
- i) Resistance
 - ii) Reactance
 - iii) Impedance
- (6 marks)

$$Z^2 = \sqrt{R^2 + (X_L^2 - X_C^2)}$$

- c) With the aid of phasor diagram show that
- (5 marks)