



**TECHNICAL UNIVERSITY OF MOMBASA**  
**Faculty of Applied & Health**  
**Sciences**

DEPARTMENT OF MATHEMATICS & PHYSICS

APS 2301: PHYSICS TECHNIQUES III

**END OF SEMESTER EXAMINATION**

**SERIES: APRIL 2013**

**TIME: 2 HOURS**

**Instructions to Candidates:**

You should have the following for this examination

- *Answer Booklet*

This paper consist of **FIVE** questions in **TWO** sections **A & B**

Answer question **ONE (COMPULSORY)** and any other **TWO** questions

Maximum marks for each part of a question are as shown  
This paper consists of **THREE** printed pages

## SECTION A (COMPULSORY)

### Question One

- a) Define the following terms:
- (i) Doping
  - (ii) Intrinsic semiconductors
  - (iii) Extrinsic semiconductors
  - (iv) N-type and p-type semiconductors
- (8 marks)**

- b) State **FIVE** ideal properties of operational Amplifiers. **(5 marks)**

- c) Given the following Boolean Expressions:

$$Y = (\overline{A \cdot B}) (\overline{A \cdot B}) (\overline{A \cdot B \cdot C + D})$$

(i)

$$y = A \cdot \overline{B} \cdot C + (\overline{A + B \cdot C}) \cdot B$$

(ii)

Draw their general logic gates arrangement. **(7 marks)**

## SECTION B (Answer any TWO questions from this section)

### Question Two

- a) Define the following terms:
- (i) Logic gate
  - (ii) Truth table
  - (iii) Flip-flop
- (6 marks)**

- b) With the aid of circuit diagrams, show that the gains of an inverting amplifier and a non-inverting amplifier using OP-AMPS, are given by  $-R_f/R_{in}$  and  $1 + R_f/R_1$  respectively. **(10 marks)**

- c) Using symbols differentiate between:
- (i) N-P-N and P-N-D Transistors
  - (ii) Crystal diode and zener diode
- (4 marks)**

### Question Three

- a) Explain the following concepts:
- (i) Rectification
  - (ii) Voltage regulation
- (4 marks)**

- b) With the aid of a circuit diagram and wave form diagrams, explain the operation of a full-wave bridge rectifier. **(10 marks)**

- c) With the aid of a diagram show how a multimeter can be used to measure current and voltage in a circuit. **(6 marks)**

#### Question Four

- a) Describe the operations of the following flip-flops, showing their logic gates arrangement and truth tables:
- (i) J-K flip-flop
  - (ii) R-S flip flop **(10 marks)**
- b) Convert the following decimal numbers to binary numbers:
- (i) 197
  - (ii) 56 **(4 marks)**
- c) With the aid of a circuit diagram, show how a N-P-N transistors can be used as a single stage voltage amplifier. **(6 marks)**

#### Question Five

- a) Using symbolic diagrams, explain:
- (i) Forward biasing and
  - (ii) Reverse biasing of P-N function diodes **(8 marks)**
- b) With the aid of a graph, describe the following parameters of silicon controlled Rectifier (SCR)
- (i) Forward break over voltage
  - (ii) Holding current
  - (iii) Forward and reverse blocking regions
  - (iv) Reverse breakdown voltage **(12 marks)**