



# THE MOMBASA POLYTECHNIC UNIVERSITY COLLEGE

(A Constituent College of JKUAT)

## **Ukunda Campus**

*Faculty of Engineering and Technology*

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

**CERTIFICATE IN TECHNOLOGY –ELECTRICAL POWER ENGINEERING**

EEE 1105: DIGITAL ELECTRONICS

**END OF SEMESTER EXAMINATION**

SERIES: APRIL 2012

TIME: 2 HOURS

### **Instructions to Candidates:**

This paper consists of **FIVE** questions

- *Answer Booklet*

Answer question **ONE (COMPULSORY)** and any other **TWO** questions

Marks are indicated for each part of the question

This paper consists of **THREE** printed pages

### Question One

- a) Differentiate between the following terms
- (i) Analogue and digital representation (2 marks)
  - (ii) Primary and secondary logic gates (2 marks)
  - (iii) Weighted and Non weighted binary codes (2 marks)
  - (iv) Min terms and Max terms (2 marks)
- b) Define the term binary code as used in digital electronics (1 mark)
- c) With the aid of a logic circuit show how a NAND gate can be used as an OR gate (3 marks)
- d) Convert the following numbers into the specified equivalents
- (i)  $93.625_{10}$  into its binary equivalent (4 marks)
  - (ii)  $206.104_8$  into its decimal equivalent (4 marks)
- e) Construct a logic circuit whose output is  $Y = \overline{AC} + \overline{BC} + ABC$  (5 marks)
- f) Determine the logic level Y for a logic circuit with the output  $Y = (\overline{A+B})BC$  where A = 0, B = 1 and C = 1 (4 marks)
- g) State **ONE** major drawback of digital over analogue techniques (1 mark)

### Question Two

- a) Define the following terms
- (i) Number system (1 mark)
  - (ii) Radix (1 mark)
- b) Mention **FOUR** number systems that are commonly used in digital electronics (4 marks)
- c) Convert the following Decimal numbers to their Hexadecimal equivalent
- (i)  $650_{10}$  (4 marks)
  - (ii)  $4019.345_{10}$  (4 marks)
- d) Subtract  $1101_2$  from  $1010_2$  using
- (i) 1's complement representation (2 marks)
  - (ii) 2's complement representation (2 marks)
- e) State **TWO** applications of number systems in digital electronics (2 marks)

### Question Three

- a) Briefly describe **FOUR** types of binary codes (8 marks)
- b) State **TWO** applications of binary codes (2 marks)

c) Convert the following numbers into Binary Coded Decimals (BCD)

- (i)  $79_{10}$  (3 marks)  
(ii)  $93_{10}$  (3 marks)

d) Perform the following binary calculations

- (i)  $100101 + 100101$  (2 marks)  
(ii)  $110.01 - 100.1$  (2marks)

#### Question Four

a) Citing examples differentiate between basic and secondary logic gates (3 marks)

b) Define the term universality as used with NAND and NOR gates (1 mark)

$$Y = \bar{A} + B + C + \overline{\overline{AD}}$$

c) For the output

- (i) Implement the logic circuit (5 marks)  
(ii) Determine the truth table for the circuit (5 marks)  
(iii) Determine the logic level Y given A = 1, B = 0, C = 1 and D = 0 (4 marks)

d) With the aid of a diagram show how a NAND gate can be implemented as an OR gate (2 marks)

#### Question Five

a) Describe the **TWO** standard forms of Boolean expressions (4 marks)

b) Simply the following the following Boolean expression

$$X = AB(\overline{\overline{A + BC}})$$

Hence draw the simplified logic circuit (10 marks)

c) Construct a truth table for the simplified expression in (b) above and obtain the value of X

(6marks)