



THE MOMBASA POLYTECHNIC UNIVERSITY COLLEGE

(A Constituent College of Jkuat)

Faculty of Engineering and Technology

**DEPARTMENT OF COMPUTER SCIENCE & INFORMATION
TECHNOLOGY**

DIPLOMA IN INFORMATION COMMUNICATION
TECHNOLOGY – DICT 10A
(YR 2 SEM 1)

EEE 2120: ANALOGUE ELECTRONICS

END OF SEMESTER EXAMINATIONS

SERIES: AUGUST/SEPTEMBER 2011

TIME: 2 HOURS

Instructions to Candidates:

You should have the following for this examination

- *Answer booklet*

Answer question **ONE (COMPULSORY)** and any other **TWO** questions

This paper consists of **THREE** printed pages

Question 1 (Compulsory)

- a) Outline **FIVE** ideal properties of an Operational Amplifier (5 marks)
- b) With the aid of circuit diagrams derive the gains of inverting and non-inverting amplifiers using Operational Amplifier (10 marks)
- c) Calculate the output voltage of a summing amplifier, for the following sets of input voltages and resistors ($R_f = 0.1M\ \Omega$ in all cases)
- i) $V_1 = +1V, V_2 = +2V, V_3 = +3V$
 $R_1 = 50K\ \Omega, R_2 = 0.1M\ \Omega, R_3 = 0.1M\ \Omega$
- ii) $V_1 = -2V, V_2 = +3V, V_3 = +3V$
 $R_1 = 20K\ \Omega, R_2 = 50K\ \Omega, R_3 = 0.1M\ \Omega$ (10 marks)
- d) Derive from the first principles the equation of the output voltage of differentiator and integrator using OP –AMP (5 marks)

Question 2

- a) With the aid of a diagram show how a Zener diode can be used to provide reference voltage to the output load. (4 marks)
- b) State any **FOUR** advantages and **FOUR** disadvantages of using Zener diode as a voltage regulator (8 marks)
- c) Explain any **FOUR** applications of thyristors (8 marks)

Question 3

- a) With the aid of PNP and NPN transistors show how a latch can be formed. (4 marks)
- b) A Zener diode connected as a voltage regulator; has $V_Z = 12V$ and $I_{ZM} = 30mA$, is used to supply a variable load. A current limiting resistor of $1K\ \Omega$ is connected in series to the diode a fixed D.C voltage of 40V is used to supply the regulator.
- (i) Draw the circuit diagram of the regulator
- (ii) Determine the range of R_L and I_L that will result in V_L being maintained at $12V$.
- (iii) Sketch the graphs of V_L versus R_L and V_L versus I_L
- (iv) Determine the maximum wattage rating of the diode as a regulator (16 marks)

Question 4

- a) Describe **THREE** methods of triggering ON thyristors (6 marks)
- b) With the aid of symbolic diagrams, briefly explain the operations of the following thyristors: SCR, DIAC and TRIAC (14 marks)

Question 5

- a) With the aid of a graph describe the following parameters of the silicon controlled rectifier (SCR)
- i) Forward breakover voltage
 - ii) Holding current
 - iii) Forward and reverse blocking regions
 - iv) Reverse breakdown voltage (12 marks)
- b) Explain the following terms:
- i) Doping
 - ii) Intrinsic semiconductor
 - iii) Extrinsic semiconductor
 - iv) P-type and N-type semiconductors (8 marks)