



THE MOMBASA POLYTECHNIC UNIVERSITY COLLEGE

(A Constituent College of JKUAT)

Faculty of Engineering & Technology

DEPARTMENT COMPUTER SCIENCE & INFORMATION TECHNOLOGY

DIPLOMA IN INFORMATION COMMUNICATION TECHNOLOGY - DICT 2K11M

EEE 2120: ELECTRONICS

SPECIAL/SUPPLEMENTARY EXAMINATION

SERIES: FEBRUARY/MARCH 2012

TIME: 2 HOURS

Instructions to Candidates:

You should have the following for this examination

- *Answer Booklet*

This paper consist of **FIVE** questions in **TWO** sections **A & B**

Answer question **ONE (COMPULSORY)** and any other **TWO** questions

Maximum marks for each part of a question are as shown

This paper consists of **THREE** printed pages

SECTION A (COMPULSORY)

QUESTION 1 (30 MARKS)

- a) Outline five ideal properties of an Operational Amplifier. (5 marks)
- b) With the aid of circuit diagrams derive the gains of inverting and non-inverting amplifiers using Operational Amplifier. (10 marks)
- c) Calculate the output voltage of a summing amplifier, for the following sets of input voltages and resistors ($R_f=0.1M\Omega$ in all cases)
- i) $V_1=+1V, V_2=+2V, V_3=+3V$
 $R_1=50K\Omega, R_2=0.1M\Omega, R_3=0.1M\Omega$
- ii) $V_1= -2V, V_2= +3V, V_3= +3V$
 $R_1= 20K\Omega, R_2= 50K\Omega, R_3= 0.1M\Omega$ (10 marks)
- d) Derive from the first principles the equation of the output voltage of differentiator and integrator using OP-AMP. (5 marks)

SECTION B (Answer any two questions)

QUESTION 2 (20 MARKS)

- a) With the aid of a diagram show how a Zener diode can be used to provide reference voltage to the output load. (4 marks)
- b) State any four advantages and four disadvantages of using Zener diode as a voltage regulator. (8 marks)
- c) Explain any **four** applications of thyristors. (8 marks)

QUESTION 3 (20 MARKS)

- a) With the aid of PNP and NPN transistors show how a latch can be formed. (4 marks)
- b) A Zener diode connected as a voltage regulator; has $V_Z=12V$ and $I_{ZM}=30mA$, is used to supply a variable load. A current limiting resistor of $1K\Omega$ is connected in series to the diode. A fixed D.C voltage of $40V$ is used to supply the regulator.
- i. Draw the circuit diagram of the regulator
- ii. Determine the range of R_L and I_L that will result in V_L being maintained at $12V$.
- iii. Sketch the graphs of V_L versus R_L and V_L versus I_L .
- iv. Determine the maximum wattage rating of the diode as a regulator. (16 marks)

QUESTION 4 (20 MARKS)

- a) Describe three methods of triggering ON thyristors. (6 marks)

- b) With the aid of symbolic diagrams briefly explain the operations of the following thyristors: SCR, DIAC and TRIAC. (14 marks)

QUESTION 5 (20 MARKS)

- a) With the aid of a graph describe the following parameters of the silicon controlled rectifier (SCR)

- i. forward break over voltage
- ii. holding current
- iii. forward and reverse blocking regions
- iv. reverse breakdown voltage (12 marks)

- b) Explain the following terms:

- i. Doping
- ii. Intrinsic semiconductor
- iii. Extrinsic semiconductor
- iv. P-type and N-type semiconductors (8 marks)